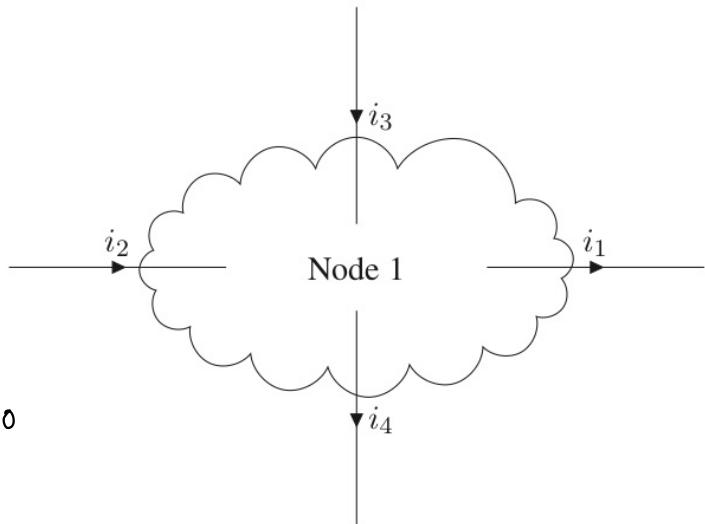



## 1.1 Kirchhoff's Laws

- a) Formulate the Kirchhoff's current law for the depicted node.




- b) Give the Kirchhoff's current law in general form.  $\sum_{\substack{j \in \text{branches} \\ \text{connected to node}}} i_j(t) = 0$
- c) Formulate the Kirchhoff's voltage law for the depicted network.

$$U_F + U_G - U_J - U_H = 0$$

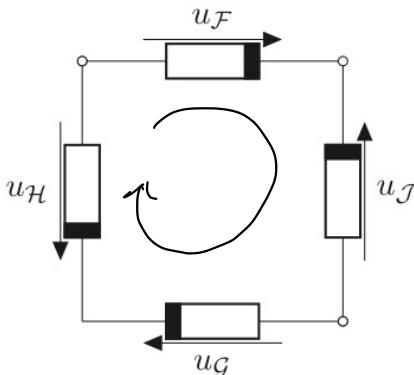

- d) Give the Kirchhoff's voltage law in general form.  $\sum_{\substack{j \in \text{branches} \\ \text{of loops}}} u_j(t) = 0$

1.2

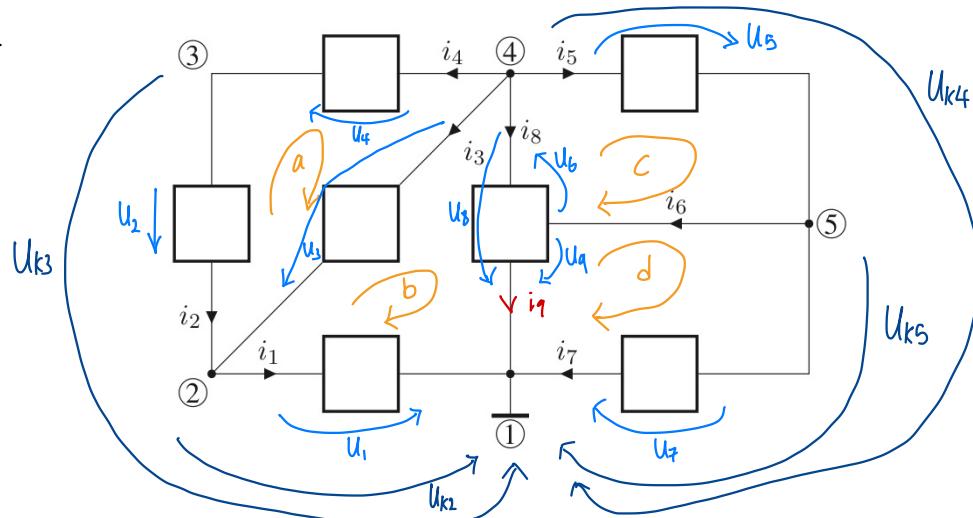

- Formulate Kirchhoff's current law (KCL) for all nodes.
- Find the Kirchhoff's voltage law (KVL) equations for some loops.
- Give the alternative form of KVL by expressing all branch voltages depending on the node voltages.

$$a) \text{ KCL(1)} : i_1 + i_7 + i_9 = 0$$

$$\text{KCL(2)} : i_1 - i_2 - i_3 = 0$$

$$\text{KCL(3)} : i_2 - i_4 = 0$$

$$\text{KCL(4)} : i_3 + i_4 + i_5 + i_8 = 0$$

$$(5) : -i_5 + i_6 + i_7 = 0$$

$$c) U_1 = U_{k2} - U_{k1} = U_{k2}$$

$$U_2 = U_{k3} - U_{k2}$$

$$U_3 = U_{k4} - U_{k2}$$

$$U_4 = U_{k4} - U_{k3}$$

$$U_5 = U_{k4} - U_{k5}$$

$$b) \text{ KVL(1)} : -U_2 - U_4 + U_3 = 0$$

$$(b) : -U_3 + U_8 - U_1 = 0$$

$$(c) : U_5 + U_6 = 0$$

$$(d) : -U_9 + U_7 = 0$$

$$U_6 = U_{k5} - \underset{0}{U_{k4}}$$

$$U_7 = U_{k5} - \cancel{U_{k4}} = U_{k5}$$

$$U_8 = U_{k4}$$


$$U_9 = U_{k5}$$

## 2.1 Linear Sources and Source Transform


- What is the difference between general linear sources and independent sources? Depict the difference graphically.
- How are the *internal resistance* and *internal conductance* of linear sources defined?

By source transform, a linear voltage source combined with an internal resistance can be equivalently transformed to a current source combined with an internal conductance.

Hence, consider the following circuit.

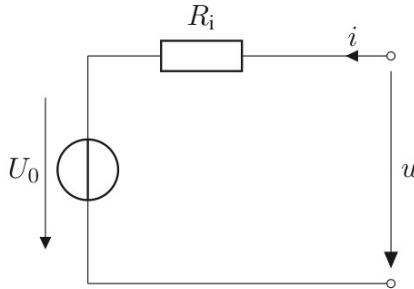

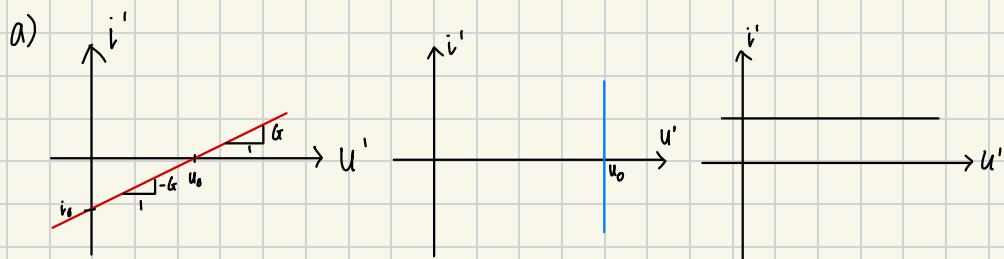
- Draw the equivalent circuit with a current source and internal conductance. Give all parameters depending on  $U_0$  and  $R_i$ .



$$b) R = \frac{U_0}{i_0}$$

$$G = \frac{1}{R} = \frac{i_0}{U_0}$$


c)

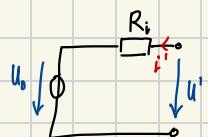

$$KVL: R_i i' + U_0 - U' = 0$$

$$U' = R_i i' + U_0$$
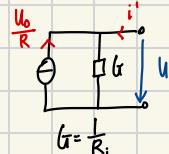
$$i' = \frac{1}{R_i} U - \frac{U_0}{R_i}$$



## 2.2 Resistive Circuits and Duality

- a) Apply the duality transform to an independent current source  $I_0 = 1 \text{ A}$  with the duality constant  $R_d = 2 \Omega$ .

Let the duality constant  $R_d$  be given.

- b) Find the element dual to a strictly linear resistor with conductance  $G$  depending on  $G$  and  $R_d$ .

a)

$$R_d = 2 \Omega$$

$$i' = I_0 \rightarrow \frac{1}{R_d} U^d = I_0$$

$$U^d = R_d I_0$$

$$R_d I_0 = 2V$$

b)

$$\text{Ohm: } i = Gu$$


$$\frac{1}{R_d} U^d = G R_d i^d$$

$$U^d = R_d^2 i^d$$

$$i^d = R_d^2 i^d$$
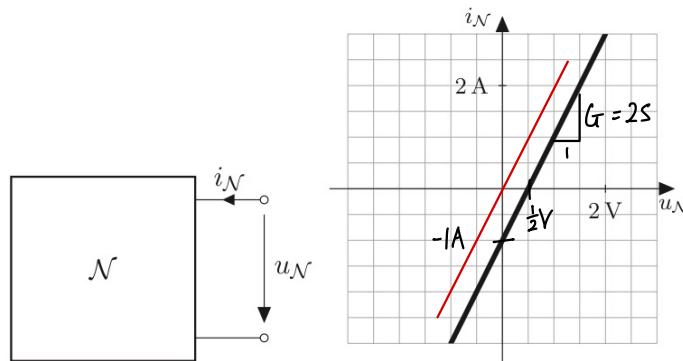
## 2.7 Source Transform

Given is the linear one-port  $\mathcal{N}$  whose characteristic is depicted in the following diagram.



- a) The circuit can be represented by two different equivalent circuit diagrams which only contain two network elements. Give the two equivalent circuit diagrams with the element values.

Now the following internal structure of  $\mathcal{N}$  is given.



13


$$G = \frac{1A}{0.5V} = 2S$$

$$R = \frac{1}{G} = 0.5\Omega$$

$$i_N = 2S u_N - 1A$$

$$u_N = 0.5\Omega i_N + 0.5V$$

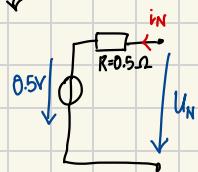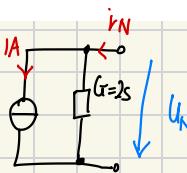

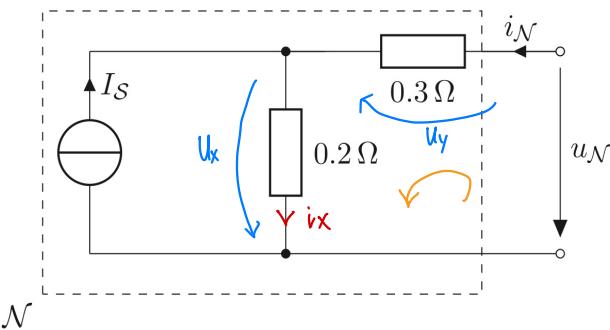


- b) Determine the source current  $I_S$ . (Hint: With the help of the characteristic, find out the behaviour of the circuit if it is connected to an open circuit.)

$$\left\{
 \begin{array}{l}
 \text{KCL : } I_S + i_N - i_x = 0 \\
 \text{KVL : } -U_N + U_y + U_x = 0 \\
 U_y = i_x \cdot 0.3 \Omega, \quad U_x = i_x \cdot 0.2 \Omega \\
 \\ 
 i_x = I_S + i_N \\
 U_x = 0.2 \Omega (I_S + i_N) \\
 \rightarrow U_N = U_y + U_x \\
 = 0.3 \Omega i_N + 0.2 \cdot 2 I_S + 0.2 i_N \\
 = 0.5 \Omega i_N + 0.2 \Omega I_S
 \end{array}
 \right.$$

$$0.5Y = 0.2 \Omega \cdot I_S \rightarrow I_S = 2.5A$$
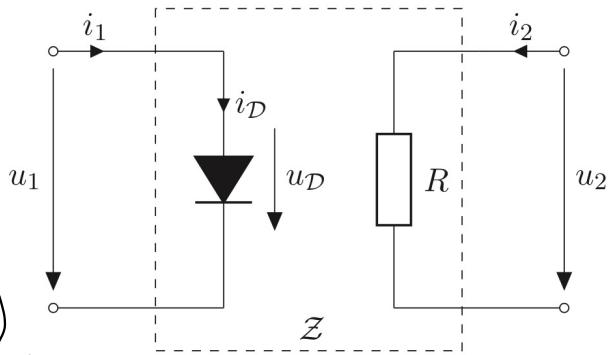
### 3.2 Representation of a Non-Linear Two-Port

Consider the following two-port  $\mathcal{Z}$ .



$$i_D = I_s \left( e^{\frac{u_D}{U_T}} - 1 \right)$$

- a) Can the two-port  $\mathcal{Z}$  be represented by a matrix?

non-linear two port  $\Rightarrow$  no matrix represent

- b) Give the current-controlled representation of  $\mathcal{Z}$ .

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = L \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Ohm:  $U_2 = R i_2$

$$\frac{i_D}{I_s} = e^{\frac{U_D}{U_T}} - 1$$

$$U_D = U_T \ln \left( \frac{i_D}{I_s} + 1 \right)$$

Kirchhoff:

$$U_D = U_1, \quad i_D = i_1$$

$$U_1 = U_T \ln \left( \frac{i_1}{I_s} + 1 \right)$$

$$\begin{aligned} U_1 &= r_1(i_1, i_2) \\ &= U_T \ln\left(\frac{i_1}{I_S} + 1\right) \\ U_2 &= R_{i_2}(i_1, i_2) = R_{i_2} \end{aligned}$$

c) Determine the hybrid representation of  $\mathcal{Z}$ .

hybrid repr.:

$$\begin{bmatrix} U_1 \\ i_2 \end{bmatrix} = h\left(\begin{bmatrix} i_1 \\ U_2 \end{bmatrix}\right)$$

$$\begin{aligned} U_1 &= h_1(i_1, U_2) \\ &= U_T \ln\left(\frac{i_1}{I_S} + 1\right) \end{aligned}$$

$$i_2 = h_2(i_1, U_2) = \frac{1}{R} U_2$$

d) Find the inverse hybrid representation of  $\mathcal{Z}$ .

$$\begin{bmatrix} i_1 \\ U_2 \end{bmatrix} = h'( \begin{bmatrix} U_1 \\ i_2 \end{bmatrix})$$

$$i_1 = h_1'(U_1, i_2)$$

$$= I_S \left( e^{\frac{U_1}{U_T}} - 1 \right)$$

$$U_2 = h_2'(U_1, i_2)$$

$$= R_{i_2}$$


e) Determine the transmission representation of  $\mathcal{Z}$ .

$$\begin{bmatrix} U_1 \\ i_1 \end{bmatrix} = a \left( \begin{bmatrix} U_2 \\ -i_2 \end{bmatrix} \right)$$

transmission representation does not exist, since  $U_2 = R_{i_2}$  is independent of  $U_1$  &  $i_1$ .
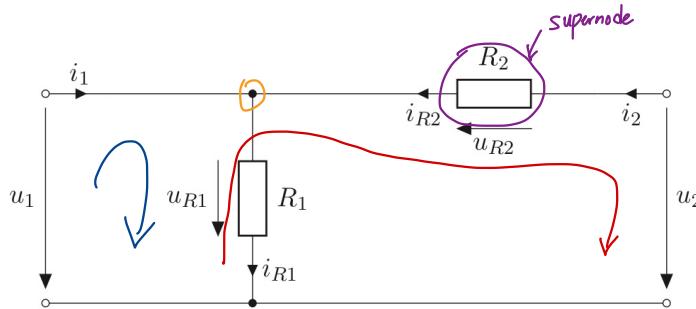
### 3.3 Two-Port Matrices

Given is the following strictly linear two-port comprising two Ohmic resistors.



Use in all calculations the conductances  $G_1 = \frac{1}{R_1}$  and  $G_2 = \frac{1}{R_2}$  if it allows simpler formulas and results.

- a) Formulate all elementary relations for the interior of the two-port.

Now determine the six two-port matrices of the two-port.

$$\text{KCL: } i_1 + i_{R2} - i_{R1} = 0$$

$$\text{KCL: } i_{R2} - i_2 = 0$$

$$\text{KVL: } -U_{R1} - U_{R2} + U_1 = 0$$

$$\text{KVL: } -U_1 + U_{R1} = 0$$

$$\text{Ohm: } U_{R1} = R_1 \cdot i_{R1}$$

$$U_{R2} = R_2 \cdot i_{R2}$$

- b) conductance matrix  $\tilde{G}$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \tilde{G} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$

$$\tilde{G} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$$

$$i_1 = g_{11} U_1 + g_{12} U_2$$

$$i_2 = g_{21} U_1 + g_{22} U_2$$

$$\text{Ohm: } i_{R1} = G_1 \cdot U_{R1}$$

$$i_{R2} = G_2 \cdot U_{R2}$$

$$\text{KCL: } i_{R2} = i_2$$

$$\text{KVL: } U_{R1} = U_1$$

$$i_{R1} = G_1 \cdot U_1$$

$$i_2 = G_2 \cdot U_{R2}$$

$$\text{From KCL: } i_{R1} = i_1 + i_{R2}$$
$$= i_1 + i_2$$

$$i_1 + i_2 = G_1 \cdot U_1$$

$$\text{From KVL: } U_{R2} = U_2 - U_{R1}$$
$$= U_2 - U_1$$

$$i_2 = \underline{\underline{G_2}} (U_2 - U_1)$$

$$i_1 + \underline{\underline{G_2}} (U_2 - U_1) = G_1 \cdot U_1$$

$$i_1 = \underline{\underline{(G_1 + G_2)U_1}} - \underline{\underline{G_2U_2}}$$

$$\underline{\underline{G}} = \begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 \end{bmatrix}$$

c) resistance matrix  $\underline{\underline{R}}$

$$\underline{\underline{U}} = \underline{\underline{R}} \underline{\underline{i}} \quad \longrightarrow \quad \underline{\underline{i}} = \underline{\underline{R}}^{-1} \underline{\underline{U}} = \underline{\underline{G}} \underline{\underline{U}}$$

$$U_1 = R_{11} i_1 + R_{12} i_2$$

$$U_2 = R_{21} i_1 + R_{22} i_2$$

$$U_1 = R_1 i_{R1}$$

$$= R_1 i_1 + R_1 i_2$$

$$\underline{\underline{R}}^{-1} = \begin{bmatrix} R_1 & R_1 \\ R_1 & R_1 + R_2 \end{bmatrix}^{-1}$$

$$= \frac{1}{\det \underline{\underline{R}}} \begin{bmatrix} R_1 + R_2 & -R_1 \\ -R_1 & R_1 \end{bmatrix}$$

$$= \frac{1}{R_1(R_1 + R_2) - R_1^2} \begin{bmatrix} R_1 + R_2 & -R_1 \\ -R_1 & R_1 \end{bmatrix}$$

$R_1 R_2$

$$U_2 = U_1 + U_{R2}$$

$$= U_1 + R_2 i_2$$

$$= R_1 i_1 + (R_1 + R_2) i_2$$

$$= \left[ \frac{R_1}{R_1 R_2 + R_2 R_1} + \frac{R_2}{R_1 R_2} i_1 - \frac{R_1}{R_1 R_2} i_2 \right]$$

$$\tilde{R} = \begin{bmatrix} R_1 & R_1 \\ R_1 & R_1 + R_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_2} + \frac{1}{R_1} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} \end{bmatrix} = \tilde{G}$$

d) hybrid matrix  $H$

$$\begin{bmatrix} U_1 \\ i_2 \end{bmatrix} = \tilde{H} \begin{bmatrix} i_1 \\ U_2 \end{bmatrix}$$

$$U_1 = h_{11} i_1 + h_{21} U_2$$

$$i_2 = h_{21} i_1 + h_{22} U_2$$

$$\begin{cases} i_1 + i_2 = G_1 U_1 \\ i_2 = G_2 (U_2 - U_1) \\ i_2 = G_1 U_1 - i_1 \end{cases}$$

$$(G_1 U_1 - i_1) = (G_2 U_2 - G_2 U_1)$$

$$(G_1 + G_2) U_1 = i_1 + G_2 U_2$$

$$U_1 = \frac{1}{G_1 + G_2} i_1 + \frac{G_2}{G_1 + G_2} U_2$$

$$i_2 = G_2 \left( U_2 - \frac{1}{G_1 + G_2} i_1 - \frac{G_2}{G_1 + G_2} U_1 \right)$$

$$\frac{G_1 + G_2}{G_1 + G_2}$$

$$= \boxed{\frac{G_1 G_2}{G_1 + G_2}} U_2 - \frac{G_2}{G_1 + G_2} i_1$$

$$G_1 || G_2 = \left( \frac{1}{G_1} + \frac{1}{G_2} \right)^{-1}$$

$$\tilde{H} = \begin{bmatrix} \frac{1}{G_1 + G_2} & \frac{G_2}{G_1 + G_2} \\ \frac{G_1 G_2}{G_1 + G_2} & -\frac{G_2}{G_1 + G_2} \end{bmatrix}$$

e) inverse hybrid matrix  $\tilde{H}'$ .

$$\tilde{H}' = \frac{1}{R_{11}} \begin{bmatrix} 1 & -R_{12} \\ R_{21} & \det \tilde{R} \end{bmatrix} \quad \text{Pg 142}$$

$$\det \tilde{R} = R_1 R_2$$

$$\tilde{R} = \begin{bmatrix} R_1 & R_1 \\ R_1 & R_1 + R_2 \end{bmatrix}$$

$$\tilde{H}' = \frac{1}{R_1} \begin{bmatrix} 1 & -R_1 \\ R_1 & R_1 R_2 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{R_1} & -1 \\ 1 & R_2 \end{bmatrix}$$

f) transmission matrix  $A$ .

$$\tilde{A} = \frac{1}{g_{21}} \begin{bmatrix} -g_{22} & -1 \\ -\det \tilde{G} & -g_{11} \end{bmatrix}$$

$$\tilde{G} = \begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 \end{bmatrix}$$

$$\det \tilde{G} = G_2(G_1 + G_2) - G_2^2$$

$$= G_1 G_2$$

$$\tilde{A} = \frac{1}{-G_2} \begin{bmatrix} -G_2 & -1 \\ -G_1 G_2 & -G_1 - G_2 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & \frac{1}{G_2} \\ G_1 & 1 + \frac{G_1}{G_2} \end{bmatrix}$$

g) inverse transmission matrix  $A'$ .

$$\tilde{A}' = \frac{1}{\det \tilde{A}} \begin{bmatrix} a_{22} & a_{12} \\ a_{21} & a_{11} \end{bmatrix}$$

$$\det \tilde{A} = \left( 1 + \frac{G_1}{G_2} \right) - \frac{G_1}{G_2} = 1$$

$$\tilde{A}' = \begin{bmatrix} 1 + \frac{G_1}{G_2} & \frac{1}{G_2} \\ G_1 & 1 \end{bmatrix}$$

For strictly linear two-ports, the different elements of the two-port matrices can be measured with the help of a particular connection of the two-port. Compare the results with those of above method.

- h) Derive the necessary connection to measure the different elements of the hybrid matrix of a strictly linear two-port. Find the hybrid matrix  $H$ .


$$\begin{bmatrix} U_1 \\ i_L \end{bmatrix} = \tilde{H} \begin{bmatrix} i_1 \\ U_2 \end{bmatrix}$$


$$U_1 = h_{11} i_1 + h_{12} U_2$$

$$i_L = h_{21} i_1 + h_{22} U_2$$

for  $h_{12}$ :  $i_1 = 0 \rightarrow$  Open circuit

define  $U_2$  by voltage source

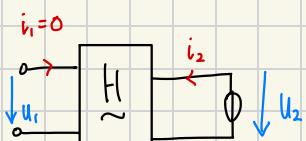

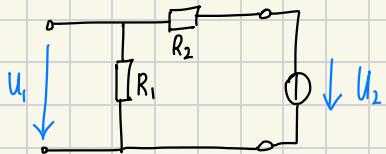


Voltage divider rule

$$\frac{U_1}{U_2} = \frac{R_1}{R_1 + R_2}$$

$$= \frac{\frac{1}{G_1}}{\frac{1}{G_1} + \frac{1}{G_2}} = \frac{G_2}{G_1 + G_2}$$

for  $h_{11}$ :  $U_2 = 0$ , short circuit

define  $i_1$  by current source

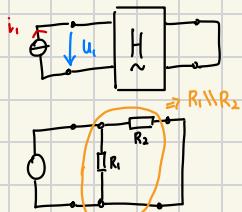

Ohm:  $U_1 = \underbrace{(R_2 || R_2)}_{h_{11}} i_1$

$$\begin{aligned} R_1 || R_2 &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{1}{\frac{1}{R_2} + \frac{1}{R_1}} \end{aligned}$$


- i) Derive the connections such that the different elements of the transmission matrix of a strictly linear two-port can be measured. Determine the transmission matrix  $A$ .

$$\begin{bmatrix} U_1 \\ i_1 \end{bmatrix} = A \begin{bmatrix} U_2 \\ -i_2 \end{bmatrix}$$


$$U_1 = a_{11} U_2 + a_{12} (-i_2)$$

$$i_1 = a_{21} U_2 + a_{22} (-i_2)$$

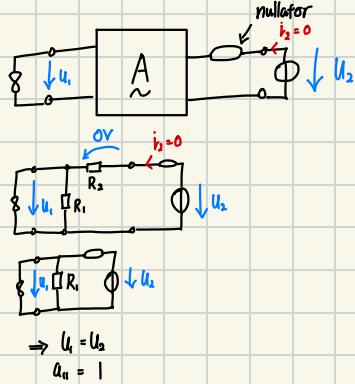for  $a_{11}$ :  $i_2 = 0 \rightarrow$  Open circuit



for  $a_{12}$ :  $U_2 = 0$

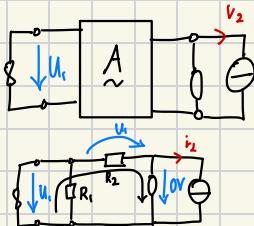

$$KVL: -U_1 + U_{R2} + 0V = 0$$

$$\rightarrow U_{R2} = U_1 = R_2 i_{R2}$$

$$= R_2 \cdot -i_2$$


$$U_1 = R_2 \cdot -i_2$$

$$\Rightarrow a_{12} = R_2$$

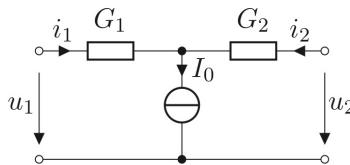
### 3.4 Linear Two-Port

not strictly linear

We consider the following two-port  $\mathcal{T}$  with  $G_1 = 1 \text{ S}$ ,  $G_2 = 2 \text{ S}$ , and  $I_0 = 4 \text{ A}$ .



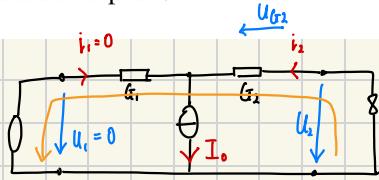- a) Perform the necessary number of measurements to be able to formulate the parametric representation of the two-port  $\mathcal{T}$ .




$$\text{due to nullator: } i_2 = I_0$$

$$\text{Ohm: } U_{G2} = \frac{i_2}{G_2}$$

$$\text{KVL: } -U_2 + U_{G2} + \text{OV} + \text{OV} = 0$$

$$U_2 = U_{G2} = \frac{I_0}{G_2}$$

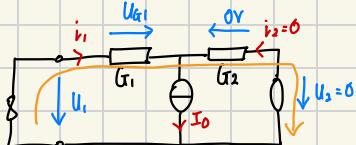


$$i_1 = I_0$$

$$U_{G1} = \frac{i_1}{G_1} = \frac{I_0}{G_1}$$

$$\text{KVL: } -U_1 + U_{G1} - \text{OV} - \text{OV} = 0$$

$$U_1 = U_{G1} = \frac{I_0}{G_1}$$
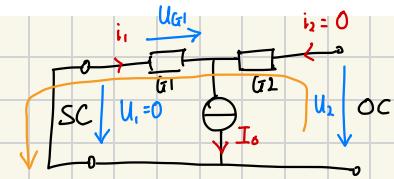
$$\begin{bmatrix} U_1^{(1)} \\ U_2^{(1)} \\ i_1^{(1)} \\ i_2^{(1)} \end{bmatrix} = \begin{bmatrix} \text{OV} \\ \text{OV} \\ 4\text{A} \\ \text{OA} \end{bmatrix}$$



$$i_1 = I_0 \text{ (due to } i_2 = 0)$$

$$U_{G1} = \frac{I_0}{G_1}$$

$$\text{KVL: } -U_2 + \text{OV} - U_{G1} + \text{OV} = 0$$

$$U_2 = -U_{G1} = -\frac{I_0}{G_1}$$

3 measurements

$$\begin{bmatrix} U_1^{(1)} \\ U_2^{(1)} \\ i_1^{(1)} \\ i_2^{(1)} \end{bmatrix} = \begin{bmatrix} \text{OV} \\ \text{OV} \\ I_0/G_2 \\ \text{OA} \end{bmatrix}$$

$$= \begin{bmatrix} \text{OV} \\ 2\text{V} \\ \text{OA} \\ 4\text{A} \end{bmatrix}$$

$$\begin{bmatrix} U_1^{(2)} \\ U_2^{(2)} \\ i_1^{(2)} \\ i_2^{(2)} \end{bmatrix} = \begin{bmatrix} 4\text{V} \\ \text{OV} \\ 4\text{A} \\ \text{OA} \end{bmatrix}$$

$$\begin{bmatrix} U_1^{(3)} \\ U_2^{(3)} \\ i_1^{(3)} \\ i_2^{(3)} \end{bmatrix} = \begin{bmatrix} \text{OV} \\ -4\text{V} \\ 4\text{A} \\ \text{OA} \end{bmatrix} - \begin{bmatrix} U_1^{(2)} \\ U_2^{(2)} \\ i_1^{(2)} \\ i_2^{(2)} \end{bmatrix}$$

$$\underline{u} \sim = \left[ \underline{u}^{(1)} - \underline{u}^{(3)}, \quad \underline{u}^{(2)} - \underline{u}^{(3)} \right]$$

$$= \begin{bmatrix} 0V & 4V \\ 6V & 4V \end{bmatrix}$$

$$\underline{i} \sim = \left[ \underline{i}^{(1)} - \underline{i}^{(3)}, \quad \underline{i}^{(2)} - \underline{i}^{(3)} \right]$$

$$= \begin{bmatrix} -4A & 0A \\ 4A & 0A \end{bmatrix}$$

$$\begin{bmatrix} \underline{u} \\ \underline{i} \end{bmatrix} = \begin{bmatrix} \underline{u} \sim \\ \underline{i} \sim \end{bmatrix} \subseteq + \begin{bmatrix} \underline{u}^{(3)} \\ \underline{i}^{(3)} \end{bmatrix}$$

- b) Rearrange the parametric representation such that you obtain the explicit representation of the form  $\underline{i} = G\underline{u} + i_G$ .

$$\begin{aligned} \underline{u} &= \underline{u} \sim + \underline{u}^{(3)} \\ \underline{i} &= \underline{i} \sim + \underline{i}^{(3)} \end{aligned}$$

$$\underline{\subseteq} = \underline{u}^{-1} (\underline{u} - \underline{u}^{(2)})$$

$$= \begin{bmatrix} 0V & 4V \\ 6V & 4V \end{bmatrix}^{-1} \left( \underline{u} - \begin{bmatrix} 0V \\ -4V \end{bmatrix} \right)$$

$$= \frac{1}{-24V^2} \begin{bmatrix} 4V & -4V \\ -6 & 0V \end{bmatrix} \left( \underline{u} - \begin{bmatrix} 0V \\ -4V \end{bmatrix} \right)$$

$$= \begin{bmatrix} -\frac{1}{6}\frac{1}{V} & \frac{1}{6}\frac{1}{V} \\ \frac{1}{4}\frac{1}{V} & 0\frac{1}{V} \end{bmatrix} \left( \underline{U} - \begin{bmatrix} 0V \\ -4V \end{bmatrix} \right)$$

$$\underline{i} = \underline{\underline{I}} \underline{U}^{-1} (\underline{U} - \underline{U}^{(s)}) + \underline{i}^{(s)}$$

$$= \begin{bmatrix} -4A & OA \\ 4A & OA \end{bmatrix} \cdot \begin{bmatrix} -\frac{1}{6}\frac{1}{V} & \frac{1}{6}\frac{1}{V} \\ \frac{1}{4}\frac{1}{V} & 0\frac{1}{V} \end{bmatrix} \cdot \left( \underline{U} - \begin{bmatrix} 0V \\ -4V \end{bmatrix} \right) + \begin{bmatrix} 4A \\ OA \end{bmatrix}$$


$$= \begin{bmatrix} \frac{2}{3}S & -\frac{2}{3}S \\ -\frac{2}{3}S & \frac{2}{3}S \end{bmatrix} \underline{U} - \underbrace{\begin{bmatrix} \frac{8}{3}A \\ -\frac{8}{3}A \end{bmatrix}}_{\begin{bmatrix} \frac{4}{3}A \\ \frac{8}{3}A \end{bmatrix}} + \begin{bmatrix} 4A \\ OA \end{bmatrix}$$

$$\underline{i} = \underline{\underline{G}} \underline{U} + \underline{i}_G$$

$$\underline{\underline{G}} = \frac{1}{3}S \begin{bmatrix} 2 & -2 \\ -2 & 2 \end{bmatrix}$$

$$\underline{i}_G = \frac{1}{3}A \begin{bmatrix} 4 \\ 8 \end{bmatrix}$$

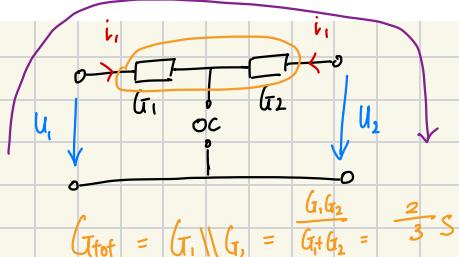- c) Find the conductance matrix  $G_0$  for the case that  $I_0 = 0$  A. What do you observe?



$$KVL: -U_1 + U_{tot} + U_2 = 0$$

$$U_{tot} = U_1 - U_2$$



$$\text{Ohm: } i_1 = G_{tot} U_{tot}$$

$$= \frac{2}{3}S(U_1 - U_2)$$

$$i_2 = -i_1 = -\frac{2}{3}s(u_1 - u_2)$$

$$\tilde{G}_0 = \begin{bmatrix} \frac{2}{3}s & -\frac{2}{3}s \\ -\frac{2}{3}s & \frac{2}{3}s \end{bmatrix} = \tilde{G}$$

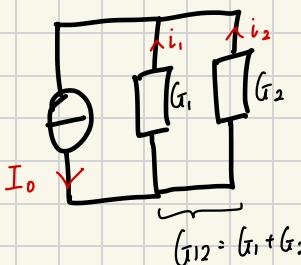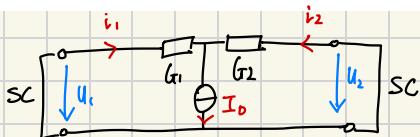- d) Determine the currents  $i_1$  and  $i_2$  for  $I_0 = 4 \text{ A}$  if the two ports are connected to short circuits.  
What do you observe?



$$\frac{i_1}{I_0} = \frac{G_1}{G_{12}} = \frac{G_1}{G_1 + G_2} = \frac{1}{3}$$


$$I_0 = 4 \text{ A}$$

$$i_1 = \left(\frac{4}{3}\right) \text{ A}$$

$$\frac{i_2}{I_0} = \frac{G_2}{G_1 + G_2} = \frac{2}{3}$$


$$i_2 = \frac{2}{3} \cdot 4 \text{ A} = \left(\frac{8}{3}\right) \text{ A}$$

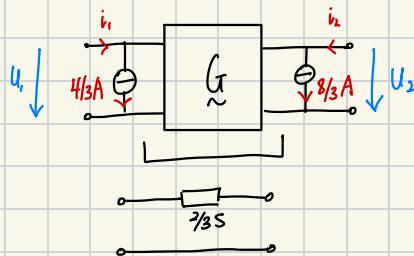- e) Draw the equivalent circuit diagram of the circuit.


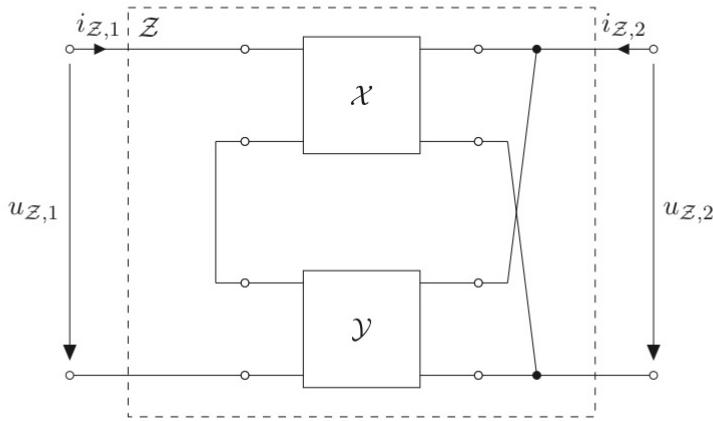
### 3.5 Series-Parallel Connection

Consider the following connection of two two-ports.



The two-ports  $\mathcal{X}$  and  $\mathcal{Y}$  are strictly linear two-ports with the hybrid matrices

$$H_{\mathcal{X}} = \begin{bmatrix} 1\Omega & 0 \\ 0.5 & 1S \end{bmatrix} \quad H_{\mathcal{Y}} = \begin{bmatrix} -1\Omega & 0.5 \\ -1.0 & -1S \end{bmatrix}$$

- a) What conditions must be fulfilled such that it is possible to obtain the hybrid matrix of  $\mathcal{Z}$  from the given hybrid matrices?

*port Conditions must be fulfilled  
Current from first port at <sup>first</sup> terminal = 2nd port of second terminal*

- b) Assume that the necessary conditions are fulfilled and find the hybrid matrix of  $\mathcal{Z}$  depending on  $H_{\mathcal{X}}$  and  $H_{\mathcal{Y}}$ .

$$\begin{bmatrix} u_1 \\ i_2 \end{bmatrix} = H \begin{bmatrix} i_1 \\ u_2 \end{bmatrix}$$

$$\begin{aligned} H_{\mathcal{Z}} &= H_{\mathcal{X}} + H_{\mathcal{Y}} \\ &= \begin{bmatrix} 0\Omega & 0.5 \\ -0.5 & 0S \end{bmatrix} \end{aligned}$$

c) What type of two-port behaves identically to  $\mathcal{Z}$ ? Give the parameter characterizing that two-port.

$$U_1 = 0.5U_2 \Rightarrow \text{transformer with } n=0.5$$
$$i_2 = -0.5i_1$$


NIC :

$$\left. \begin{aligned} U_1 &= -kU_2 \\ i_1 &= -\frac{1}{k}i_2 \end{aligned} \right\} \text{ Pg 56}$$

transformer :

$$\left. \begin{aligned} U_1 &= nU_2 \\ i_2 &= -ni_1 \end{aligned} \right\}$$

3.6

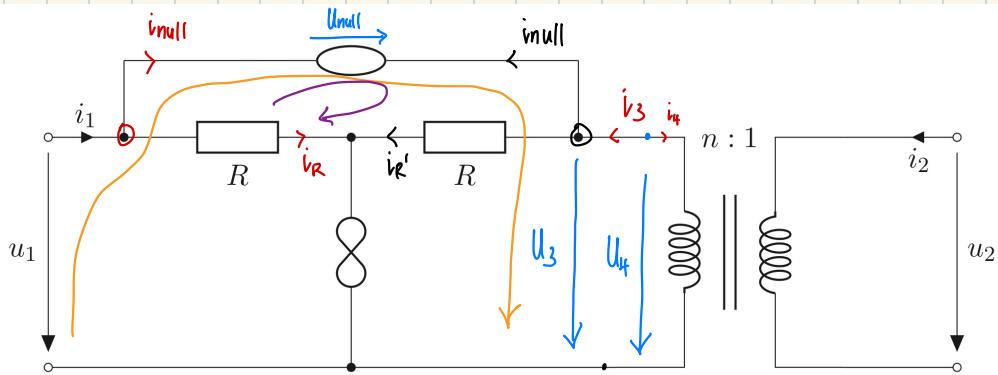

a) What is the connection between the NIC and the transformer?

$$KVL: -U_1 + U_{\text{null}}^0 + U_3 = 0$$

$$U_1 = U_3$$

$$KCL: i_1 - i_{\text{null}}^0 - i_R = 0$$

$$i_1 = i_R$$

$$KCL: i_R' = i_3$$

$$KVL: -R_{iR} + U_{\text{null}}^0 + R_{iR'} = 0$$

$$R_{iR} = R_{iR'}, i_R = i_{R'}$$

$$i_1 = i_3$$

$\Rightarrow$  NIC with  $K = -1$

$$\left. \begin{array}{l} U_4 = nU_2 \\ i_2 = -ni_4 \end{array} \right\} \text{transformer}$$

Cascade Connection

$\Rightarrow$  transmission representative

b) Determine the transmission matrix  $A$  of the two-port. What type of two-port is it?

$$\tilde{A} = \tilde{A}_{\text{NIC}} \quad \tilde{A}_{\text{transf}}$$

$$\tilde{A}_{\text{NIC}} = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix}, \quad \tilde{A}_{\text{transf}} = \begin{bmatrix} n & 0 \\ 0 & \frac{1}{n} \end{bmatrix}$$

$$\tilde{A} = \begin{bmatrix} n & 0 \\ 0 & -\frac{1}{n} \end{bmatrix} \Rightarrow \begin{aligned} u_1 &= nu_2 \\ i_1 &= \frac{1}{n}(-i_2) \\ &= \frac{1}{n}(i_2) \end{aligned}$$

$\rightarrow$  NIC with  $k = -n$

c) Is the two-port reciprocal?  $\rightarrow$  if got  $\tilde{A}$  matrix,  $\det = 1$

$$\det \tilde{A} \stackrel{!}{=} 1$$


use representation found, do not convert

$$\det \begin{bmatrix} n & 0 \\ 0 & -\frac{1}{n} \end{bmatrix} = -1 \neq 1$$

$\Rightarrow$  not reciprocal


## 4.2 Amplifier Circuit

Consider the following circuit.

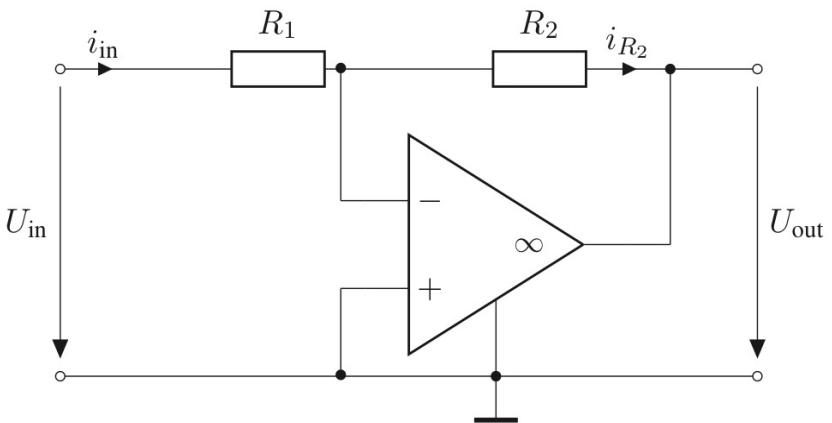

The Op-Amp is operated in the linear region.

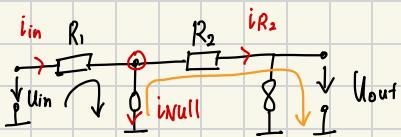- a) What is the relationship between  $i_{in}$  and  $i_{R_2}$ ?



$$a) \text{KCL: } i_{in} - i_{R_2} - i_{\text{innull}} = 0$$

$$i_{R_2} = i_{in}$$

- b) Express  $u_{in}$  depending on  $i_{in}$ .

$$b) \text{KVL: } -U_{in} + R_1 i_{in} + U_{\text{inull}} = 0$$

$$U_{in} = R_1 i_{in}$$

c) Find  $u_{\text{out}}$  depending on  $i_{\text{in}}$ .

$$\text{KVL: } -U_{\text{Null}} + R_2 i_{R_2} + U_{\text{out}} = 0$$
$$U_{\text{out}} = -R_2 i_{R_2} = -R_2 i_{\text{in}}$$

d) Determine  $u_{\text{in}}$  depending on  $u_{\text{out}}$ .

$$U_{\text{in}} = -\frac{R_1}{R_2} U_{\text{out}}$$

e) What is the voltage gain  $\nu$  of the circuit? What is the purpose of the circuit?


$$U_{\text{out}} = \left( -\frac{R_2}{R_1} \right) U_{\text{in}}$$

$$\nu = -\frac{R_2}{R_1}$$

Purpose  $\Rightarrow$  amplify and invert voltage  
inverting amplifier

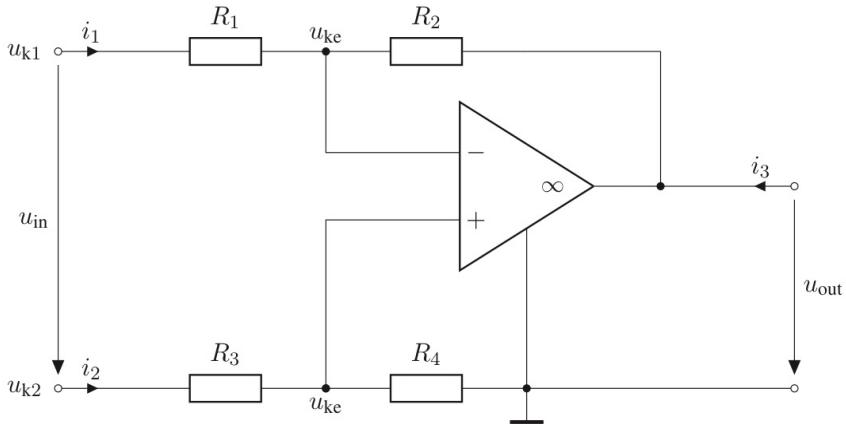
## 4.5 Difference Amplifier

The following circuit is a summer with an Op-Amp operated in the linear region.



This circuit is called potential difference amplifier if the output voltage  $u_{\text{out}}$  only depends on the difference  $u_{\text{in}} = u_{k1} - u_{k2}$  of the two input potentials, i.e.,  $u_{\text{out}} = v_d u_{\text{in}}$ .

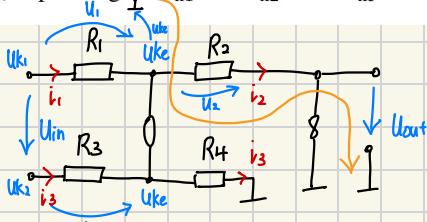- a) Determine  $u_{\text{out}}$  depending on  $u_{k1}$  and  $u_{k2}$ . Use  $u_{\text{ke}}$  for the potential of the Op-Amp inputs.



$$\text{a) KVL: } U_i = U_{k1} - U_{ke}$$

$$\rightarrow \text{KVL: } U_3 = U_{k2} - U_{ke}$$

$$U_i = U_{k1} - U_{ke}$$

$$i_1 = \frac{U_i}{R_1} = \frac{U_{k1} - U_{ke}}{R_1}$$

$$\text{Ohm: } i_3 = \frac{U_3}{R_3}$$

$$\rightarrow U_{ke} = R_4 i_3 = \frac{R_4}{R_3} U_3$$

$$U_2 = R_2 i_1 = \frac{R_2}{R_1} (U_{k1} - U_{ke})$$

$$U_{ke} = \frac{R_4}{R_3} (U_{k2} - U_{ke})$$

$$(U_{ke} + \frac{R_4}{R_3} U_{ke}) = \frac{R_4}{R_3} \cdot U_{k2}$$

$$\frac{R_3 + R_4}{R_3} U_{ke} = \frac{R_4}{R_3} \cdot U_{k2}$$

$$U_{ke} = \frac{R_4}{R_3 + R_4} \cdot U_{k2}$$

$$\begin{aligned} \text{KVL: } & -U_{ke} + U_2 + U_{out} = 0 \\ (U_{out} &= -U_2 + U_{ke}) \\ & = -\frac{R_2}{R_1} U_{k1} + \frac{R_2}{R_1} U_{ke} + U_{ke} \\ & = -\frac{R_2}{R_1} U_{k1} + \frac{R_1 + R_2}{R_1} U_{ke} \\ & = -\frac{R_2}{R_1} U_{k1} + \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} \cdot U_{k2} \end{aligned}$$

- b) When behaves the circuit like a potential difference amplifier? Give the resulting difference gain  $v_d$ .

$$\frac{R_2}{R_1} = \frac{R_1+R_2}{R_1} \cdot \frac{R_4}{R_3+R_4}$$
$$= \frac{R_2}{R_1} \left( 1 + \frac{R_1}{R_2} \right) \cdot \frac{1}{1 + R_3/R_4}$$

3

$$\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\Rightarrow U_{out} = -\frac{R_2}{R_1} U_{k1} + \frac{R_2}{R_1} U_{k2}$$


$$= -\frac{R_2}{R_1} (U_{k1} - U_{k2})$$

$$\Rightarrow \text{potential difference amp.} = -\frac{R_2}{R_1}$$

$v_d$
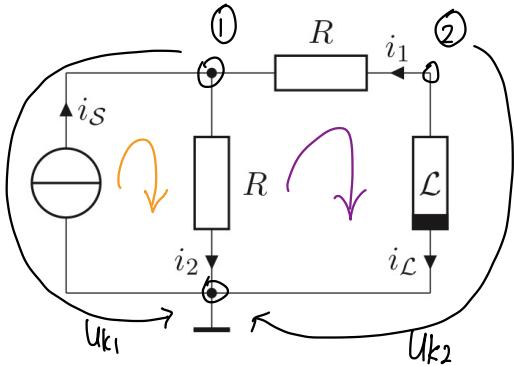
## 5.1 Kirchhoff's Laws

Consider the following circuit with non-linear load  $\mathcal{L}$ .



- a) What is the number of nodes and what is the number of branches of the circuit?

$$b=4, n=3$$

- b) Give the number of linearly independent KCL equations. What is thus the size of the node incidence matrix  $A$ ?

$$\begin{aligned} n-1 &= 2 \text{ KCL eqn} \\ A &\in \{0, 1, -1\}^{\frac{n-1 \times b}{2 \times 4}} \end{aligned}$$

- c) Give the number of linearly independent KVL equations. What is therefore the size of the loop incidence matrix  $B$ ?

$$\begin{aligned} b-(n-1) &= 4-2 = 2 \text{ KVL eqn} \\ B &\in \{0, 1, -1\}^{2 \times 4} \end{aligned}$$

d) Find the loop incidence matrix  $B$  of the given circuit.

$$KVL : U_s + U_2 = 0$$

$$KVL : -U_2 - U_1 + U_L = 0$$

$$\underline{U} = [U_1, U_2, U_s, U_L]^T$$

$$\underline{B}\underline{U} = 0$$

$$\underline{B} = \begin{bmatrix} 0 & 1 & 1 & 0 \\ -1 & -1 & 0 & 1 \end{bmatrix}$$

e) Determine the node incidence matrix  $A$  of the circuit.

$$KCL : \underline{A}\underline{i} = 0$$

$$\underline{i} = [i_1, i_2, i_s, i_L]^T$$

$$\underline{A} = \begin{bmatrix} -1 & 1 & -1 & 0 \\ 1 & 0 & 0 & 1 \end{bmatrix}$$

f) What is the rank of  $A$ , i.e., what is the number of linearly independent row vectors in  $A$ ? Justify your answer.

Based on the node incidence matrix  $A$ , a different form of the KVL equations can be found.

$$\text{rank } (\underline{A}) = 2$$

two linearly independent row


g) Formulate this alternative form of the KVL.

$$\underline{U} = \underline{A}^T \underline{U}_k$$

$$\underline{U}_k = [U_{k1}, U_{k2}]^T$$

$$\begin{bmatrix} U_1 \\ U_2 \\ U_s \\ U_L \end{bmatrix} = \begin{bmatrix} -1 & 1 \\ 1 & 0 \\ -1 & 0 \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} U_{k1} \\ U_{k2} \end{bmatrix} = \begin{bmatrix} U_{k2} - U_{k1} \\ U_{k1} \\ -U_{k1} \\ U_{k2} \end{bmatrix}$$

5.2

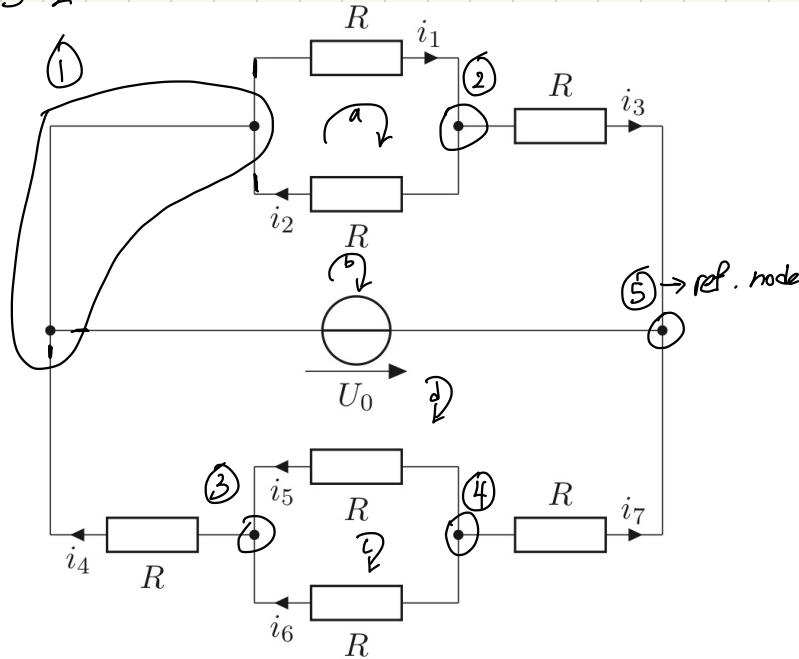

a) What is the number of nodes? Mark the nodes in the circuit.

b) Determine the node incidence matrix  $A$  of the circuit.

$$b = 8! \quad n = 5$$

$$\underline{i} = [i_0 \ i_1 \ i_2 \ i_3 \ i_4 \ i_5 \ i_6 \ i_7]$$

$$A = \begin{matrix} \textcircled{1} & \left[ \begin{array}{ccccccc} 1 & 1 & -1 & 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 & 1 \end{array} \right] \\ \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \end{matrix}$$

c) What is the number of linearly independent KVL equations?

$$b - (n-1) = 4 \text{ KVL eqn} \rightarrow \text{holes in circuit}$$


d) Find the loop incidence matrix  $B$ .

$$\underline{B} \underline{u} = 0$$


$$\underline{u} = [u_0 \ u_1 \ u_2 \ u_3 \ u_4 \ u_5 \ u_6 \ u_7 \ u_8]^T$$

$$\underline{\underline{B}} = \begin{bmatrix} 0 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 1 & -1 & 0 \end{bmatrix}$$

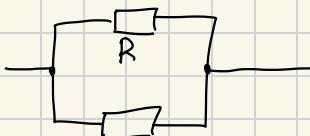e) Combine the resistors to a single resistor  $R_{\text{tot}}$ . Draw the resulting equivalent circuit diagram.


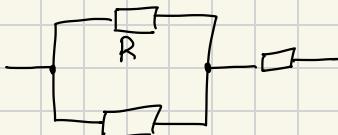
$$R_{II} = R \parallel R = \frac{RR}{R+R} = \frac{R}{2}$$




$$R + R_{II}R = R + \frac{R}{2} = \frac{3R}{2}$$




$$\frac{R}{2} + R + R = \frac{R}{2} + 2R = \frac{5R}{2}$$
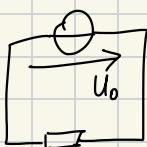
$$R_{\text{tot}} = \frac{3R}{2} \parallel \frac{5R}{2} = \frac{\frac{3R}{2} \cdot \frac{5R}{2}}{\frac{3R+5R}{2}} = \frac{\frac{15}{4}R^2}{4R} = \frac{15}{16}R$$



$$R_{\text{tot}} = \frac{15}{16} R$$

5.3

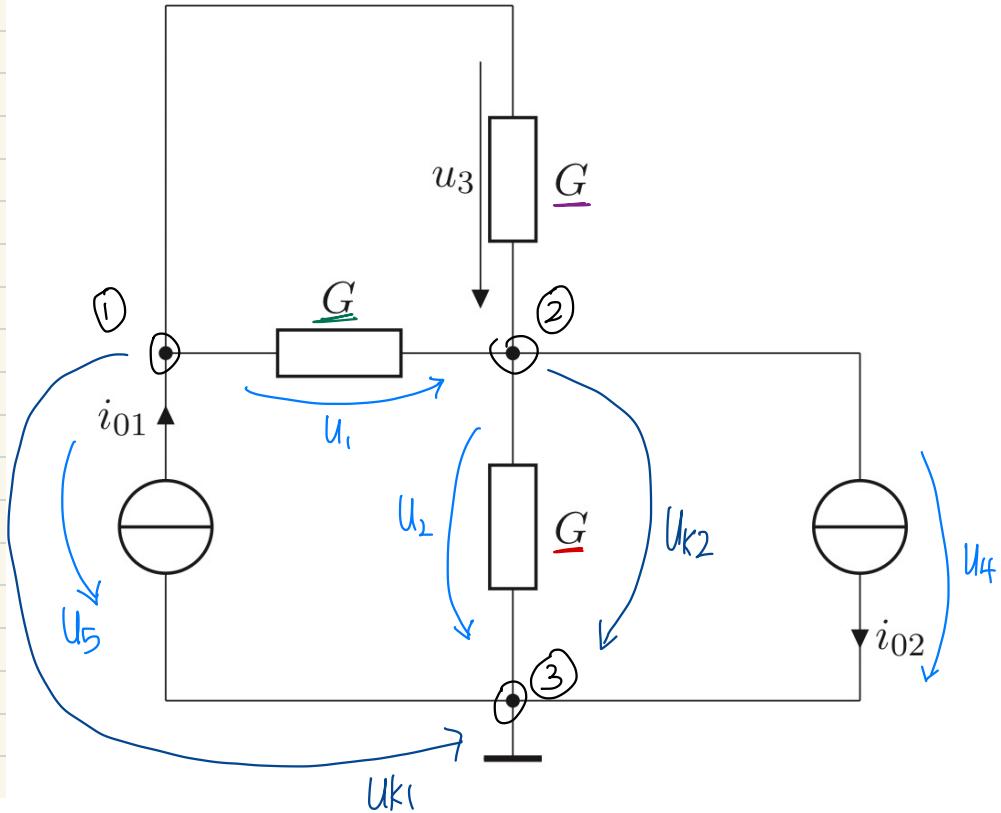

- a) Label the branches by introducing branch voltages.

- b) What is number of linearly independent KVL equations? Find the KVL equations in the form  $Bu = 0$ .

$$b=5 \quad n=3$$

$$b - (n-1) = 5 - (3-1) = 3$$

$$\tilde{B}u = 0$$

$$\tilde{B} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & -1 \\ 0 & -1 & 0 & 1 & 0 \end{bmatrix}$$

- c) What is the number of linearly independent KCL equations? Determine the KCL equations in the form  $Ai = 0$ .

By Tellegen's law,  $\tilde{A}\tilde{B}^T = 0$ .

- d) Verify Tellegen's law.

$$n-1 = 2 \text{ KCL eqns}$$

$$\tilde{A}i = 0$$

$i_1, i_2, i_3, i_4, i_5$

$$\tilde{A} = \begin{bmatrix} 1 & 0 & 1 & 0 & 1 \\ -1 & 1 & -1 & 1 & 0 \end{bmatrix}$$

$$\text{Tellegen: } \tilde{A}\tilde{B}^T = 0$$

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 1 \\ -1 & 1 & -1 & 1 & 0 \end{bmatrix} \cdot \begin{bmatrix} -1 & 1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & -1 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} = 0 \rightarrow \text{verified}$$

e) Find a representation of the circuit elements in the form  $[M, N] \begin{bmatrix} u \\ i \end{bmatrix} = e$ .

$$\begin{array}{l} \text{---} \\ \sim \end{array} M \begin{array}{l} \text{---} \\ \sim \end{array} U + \begin{array}{l} \text{---} \\ \sim \end{array} N \begin{array}{l} \text{---} \\ \sim \end{array} I = \underline{e}$$

$$i_1 = U, G$$

$$-G U_1 + i_1 = 0$$

$$-G U_2 + i_2 = 0$$

$$-G U_3 + i_3 = 0$$

$$i_4 = i_{02}$$

$$i_5 = -i_{01}$$

$$\begin{array}{l} \text{---} \\ \sim \end{array} M = \begin{bmatrix} -G & & & & \\ & -G & & & \\ & & -G & & \\ & & & 0 & \\ & & & & 0 \end{bmatrix} \quad \begin{array}{l} \text{---} \\ \sim \end{array} N = \begin{bmatrix} 1 & & & & \\ & 1 & & & \\ & & 1 & & \\ & & & 1 & \\ & & & & 1 \end{bmatrix}$$

$$\underline{e} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ i_{02} \\ -i_{01} \end{bmatrix}$$

f) Give the condition for the circuit elements such that  $N$  is invertible.

Circuit elements are voltage controlled

$$\tilde{N}^{-1} = \tilde{I}$$

g) Collect the equations of the previous subproblems and formulate the tableau equation system.

$$\left[ \begin{array}{cc|cc|c} -1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & -1 \\ 0 & -1 & 0 & 1 & 0 \\ \hline 0 & & 1 & 0 & 1 \\ & & -1 & 1 & -1 & 1 & 0 \end{array} \right] \xrightarrow{\sim} \left[ \begin{array}{cc|cc|c} -G & & 1 & & \\ -G & & 1 & & \\ -G & & 1 & & \\ 0 & & 1 & & \\ 0 & & & & 1 \end{array} \right] \xrightarrow{\sim} \left[ \begin{array}{cc|cc|c} \mathbf{B} & & & & \\ \mathbf{M} & & & & \\ \mathbf{N} & & & & \end{array} \right]$$

$$\left[ \begin{array}{c} \mathbf{U}_1 \\ \mathbf{U}_2 \\ \mathbf{U}_3 \\ \mathbf{U}_4 \\ \mathbf{U}_5 \end{array} \right] = \left[ \begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right] = \left[ \begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{array} \right] = \left[ \begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right] \quad \mathbf{e}$$

h) Is the equation system in Subproblem g) uniquely solvable?

Yes, all rows are linearly independent

i) Formulate the nodal analysis for the circuit. To this end, mark the node voltages.

$$\mathbf{U}_k = \begin{bmatrix} \mathbf{U}_{k1} \\ \mathbf{U}_{k2} \end{bmatrix}$$

$$\textcircled{1} \quad \begin{bmatrix} G+G & -G-G \\ -G-G & G+G \end{bmatrix} \begin{bmatrix} \mathbf{U}_{k1} \\ \mathbf{U}_{k2} \end{bmatrix} = \begin{bmatrix} i_{01} \\ -i_{02} \end{bmatrix}$$

flow in  $\oplus$   
flow out  $\ominus$

when element  
single entry  $\nwarrow$  connected  
with reference

element connected with 2  
node = 4 entries  
2  $\oplus$  in main diagonal  
2  $\ominus$  in other diagonal

$$\begin{bmatrix} 2G & -2G \\ -2G & 3G \end{bmatrix} \cdot \begin{bmatrix} U_{k1} \\ U_{k2} \end{bmatrix} = \begin{bmatrix} i_{o1} \\ -i_{o2} \end{bmatrix}$$

j) Find  $u_3$ .

$$U_3 = U_{k1} - U_{k2}$$

$$\begin{bmatrix} 2G - 2G & -2G + 3G \end{bmatrix} \cdot \begin{bmatrix} U_{k1} \\ U_{k2} \end{bmatrix} = i_{o1} - i_{o2}$$

$$U_{k2} = \frac{1}{G} (i_{o1} - i_{o2})$$

$$\begin{bmatrix} 2G & -2G \end{bmatrix} \cdot \begin{bmatrix} U_{k1} \\ U_{k2} \end{bmatrix} = i_{o1}$$

$$2G U_{k1} - 2G U_{k2} = i_{o1}$$

$$2G U_{k1} - 2(i_{o1} - i_{o2}) = i_{o1}$$

$$2G U_{k1} = 3i_{o1} - 2i_{o2}$$


$$U_{k1} = \frac{3}{2G} i_{o1} - \frac{1}{G} i_{o2}$$

$$U_3 = U_{k1} - U_{k2}$$


$$= \frac{3}{2G} i_{o1} - \frac{1}{G} i_{o2} - \frac{1}{G} (i_{o1} - i_{o2})$$

$$= \frac{1}{2G} u_{D1} + 0$$

5.4

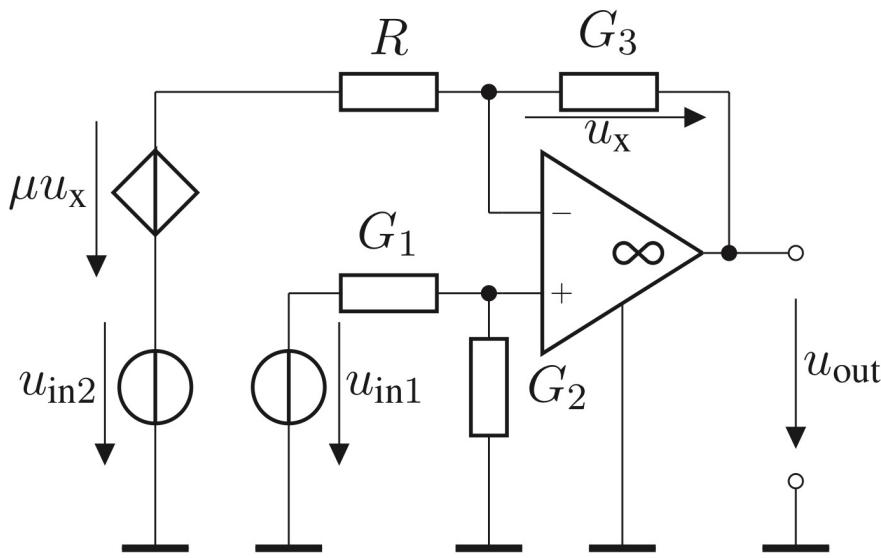

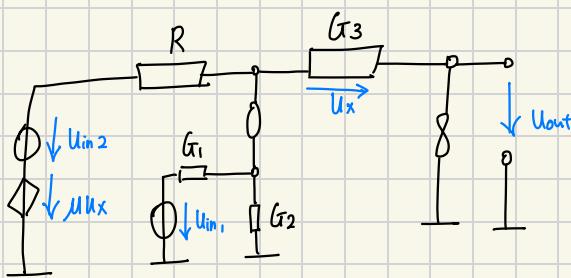- a) Give the elements which are not voltage-controlled. Discuss how these elements are transformed to voltage-controlled elements.






- a) nullator, norator

$$R \rightarrow \frac{1}{R}$$


$u_{in1}, u_{in2}, VCVS$

→ Source transform

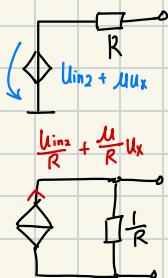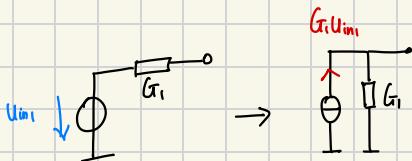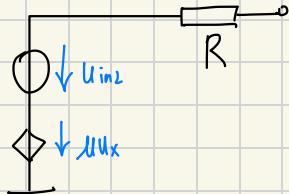- b) Draw the equivalent circuit diagram where the non-voltage-controlled elements are replaced by voltage-controlled elements. Include the equivalent circuit diagram of the Op-Amp according to the linear region.



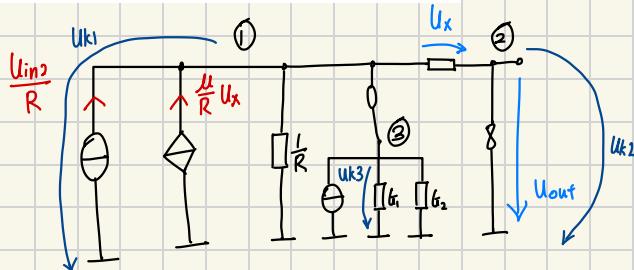- c) Number the nodes of the equivalent circuit diagram.



ignore nullator & norator  $\rightarrow \text{OC}$

- d) Determine  $u_x$  and  $u_{out}$  depending on the node voltages.

$$U_x = U_{k1} - U_{k2}$$

- e) Find the node conductance matrix  $G'_k$ , the node voltage vector  $u'_k$ , and the node current source vector  $i'_q$  ignoring the Op-Amp.

$$\left[ \begin{array}{cc|c} \frac{1}{R} + G_3 - \frac{\mu}{R} & -G_3 + \frac{\mu}{R} & \frac{1}{R} + G_3 - \frac{\mu}{R} \\ \hline -G_3 & G_3 & 0 \end{array} \right] \begin{bmatrix} u_{k1} \\ u_{k2} \\ u_{k3} \end{bmatrix} = \begin{bmatrix} \frac{u_{in2}}{R} \\ 0 \\ G_1 u_{in1} \end{bmatrix}$$

Nullator between ① & ③

- f) Incorporate the Op-Amp to obtain  $G_k$ ,  $u_k$ , and  $i_q$ .

$$\left[ \begin{array}{cc|c} -G_3 + \frac{\mu}{R} & \frac{1}{R} + G_3 - \frac{\mu}{R} & u_{k2} \\ \hline 0 & G_1 + G_2 & u_{k3} \end{array} \right] = \begin{bmatrix} \frac{u_{in2}}{R} \\ G_1 u_{in1} \end{bmatrix}$$

- g) Solve the resulting equation system.

$$2nd \text{ eqn.: } (G_1 + G_2)u_{k3} = G_1 u_{in1}$$

$$u_{k3} = \frac{G_1}{G_1 + G_2} u_{in1}$$

$$1st \text{ eqn.: } (-G_3 + \frac{\mu}{R})u_{k2} + (\frac{1}{R} + G_3 - \frac{\mu}{R})u_{k3} = \frac{u_{in2}}{R}$$

$$(-G_3 + \frac{\mu}{R})u_{k2} + \left(\frac{1}{R} + G_3 - \frac{\mu}{R}\right) \frac{G_1}{G_1 + G_2} u_{in1} = \frac{u_{in2}}{R}$$

$$u_{k2} = \frac{1}{\mu - G_3 R} \cdot u_{in2} - \frac{\left(\frac{1}{R} + G_3 - \frac{\mu}{R}\right) G_1}{G_1 + G_2} \frac{1}{\frac{\mu}{R} - G_3} u_{in1}$$

$$= \frac{1}{\mu - G_3 R} \cdot u_{in2} - \frac{(1 + RG_3 - \mu) G_1}{G_1 + G_2} \frac{1}{\mu - RG_3} u_{in1}$$

h) Determine  $u_{\text{out}}$  depending on  $u_{\text{in}1}$  and  $u_{\text{in}2}$ .

$$\begin{aligned} h) \quad u_{\text{out}} &= u_{\text{k2}} \\ &= \frac{1}{\mu - G_3 R} u_{\text{in}2} - \frac{(1 + RG_2 - \mu) G_1}{(G_1 + G_2)(\mu - RG_3)} u_{\text{in}1} \end{aligned}$$

i) Is it possible to choose a value for the gain factor  $\mu$  such that  $u_{\text{out}}$  is independent of  $u_{\text{in}2}$ ? If yes, find the corresponding  $\mu$ .

$$i) \quad \mu \rightarrow \infty$$

$$u_{\text{out}} \rightarrow \frac{G_1}{G_1 + G_2} u_{\text{in}1}$$


j) Is it possible to choose a value for the gain factor  $\mu$  such that  $u_{\text{out}}$  is independent of  $u_{\text{in}1}$ ? If yes, find the corresponding  $\mu$ .

$$j) \quad 1 + RG_3 - \mu = 0 \rightarrow u_{\text{in}1} \text{ disappear}$$

$$\mu = 1 + RG_3$$

$$\rightarrow u_{\text{out}} = u_{\text{in}2}$$

5.5

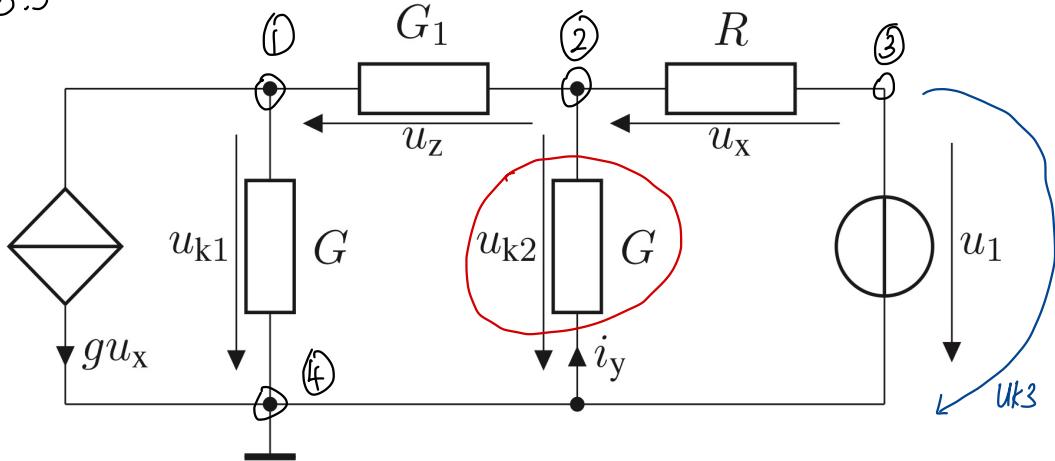a) Express  $u_x$  depending on the node voltages and  $u_1$ .

$$u_x = u_{k3} - u_{k2}$$

$$u_{k3} = u_1$$

$$u_x = u_1 - u_{k2}$$

b) Find  $i_y$  depending on the node voltages and  $u_1$ .

$$i_G = G u_{k2}$$



$$KCL = i_G + i_y = 0$$

$$i_y = -i_G = -G u_{k2}$$

c) Determine  $u_z$  depending on the node voltages and  $u_1$ .

$$u_z = u_{k2} - u_{k1}$$

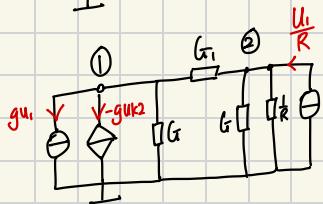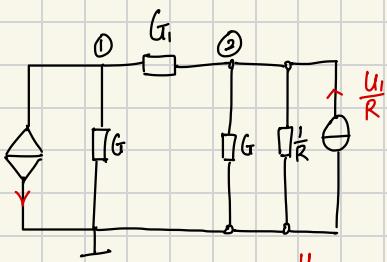d) Change the circuit such that the nodal analysis can be employed.



e) Formulate the nodal analysis.

$$\begin{bmatrix} G + G_1 & -G_1 - g \\ -G_1 & G + \frac{1}{R} + G_1 \end{bmatrix} \begin{bmatrix} U_{k1} \\ U_{k2} \end{bmatrix} = \begin{bmatrix} -g u_i \\ \frac{U_i}{R} \end{bmatrix}$$

f) Solve the resulting equation system.

$$-G_1 U_{k1} + (G + \frac{1}{R} + G_1) U_{k2} = \frac{U_i}{R}$$

$$U_{k1} = \frac{G + \frac{1}{R} + G_1}{G_1} U_{k2} - \frac{U_i}{R G_1}$$

$$(1) : (G + G_1) U_{k1} + (-G_1 - g) U_{k2} = -g u_i$$

$$\frac{G + G_1}{G_1} \cdot (G + \frac{1}{R} + G_1) U_{k2} - \frac{G + G_1}{R G_1} U_i + (-G_1 - g) U_{k2} = -g u_i$$

$$\frac{(G + G_1)(G + \frac{1}{R} + G_1) - G_1(G_1 + g)}{G_1} \cdot u_{k2} = \left( \frac{G_1 + G}{RG_1} - g \right) u_1$$

$$\frac{R \cdot G^2 + G + \frac{1}{R} + RG_1 + R G_1 + G_1 + \frac{1}{R} - RG_1}{G_1} \cdot u_{k2} = \frac{G_1 + G - gRG_1}{RG_1} \cdot u_1$$

$$(R \cdot G^2 + G + G_1 + 2GG_1R - gG_1R) u_{k2} = (G + G - gRG_1) \cdot u_1$$

$$u_{k2} = \frac{G_1 + G - gRG_1}{RG^2 + G + G_1 + 2GG_1R - gG_1R} u_1$$

$$u_{k1} = \frac{GR + 1 + G_1R}{G_1R} \cdot \frac{G + G_1 - RG_1g}{RG^2 + G + G_1 + 2GG_1R - gG_1R} u_1 - \frac{u_1}{RG_1}$$

g) What do you obtain for  $i_y$  and  $u_z$ ?

$$i_y = -u_{k2}$$

$$= -G \frac{G + G_1 - RG_1g}{RG^2 + G + G_1 + 2GG_1R - gG_1R} u_1$$

$$u_z = u_{k2} - u_{k1}$$

h) Can  $g$  chosen such that  $i_y$  is zero? If yes, give the according value of  $g$ .


i) Can  $g$  chosen such that  $u_z$  is zero? If yes, give the according value of  $g$ .

$$i_y = 0$$

$$G + G_1 - RG_1g = 0$$

$$g = \frac{G + G_1}{RG_1}$$

if  $i_y = 0$ ,

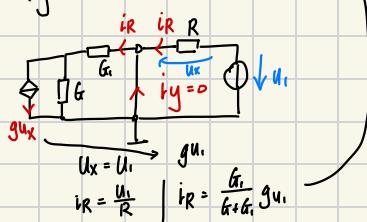


## 6.1 Strictly Linear Reactances

Consider the voltage source  $u(t) = U_0 \sin(\omega t)$ .

Firstly, the voltage source is connected to a strictly linear capacitor  $C$  at time  $t = 0$ .

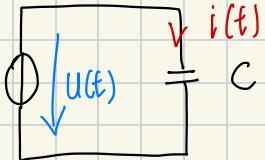- a) Find the current  $i(t)$  flowing through the capacitor for  $t \geq 0$ .



$$i(t) = C \dot{u}(t)$$

$$= U_0 \cos(\omega t) \cdot \omega$$

- b) What is the flux  $\Phi(t)$  for  $t \geq 0$  under the assumption that  $\Phi(0) = \Phi_0$ ?

$$\begin{aligned}\Phi(t) &= \Phi(0) + \int_0^t u(t') dt' \\ &= \Phi_0 + \int_0^t U_0 \sin(\omega t') dt' \\ &= \Phi_0 + U_0 \left[ -\cos(\omega t) \frac{1}{\omega} \right]_0^t\end{aligned}$$

$$\Phi(t) = \Phi_0 + U_0 \left( -\cos(\omega t) \frac{1}{\omega} + 1 \frac{1}{\omega} \right)$$

- c) Determine the charge  $q(t)$ .


$$q(t) = C u(t) = C U_0 \sin(\omega t)$$

- d) What is therefore the initial condition  $q(0)$ ?

$$q(0) = C U_0 \sin(\omega \cdot 0) = 0$$

Secondly, the voltage source is connected to a strictly linear inductor  $L$  at time  $t = 0$ .

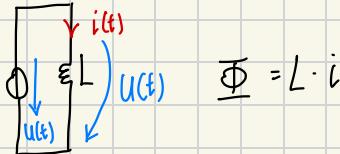- e) Find the current  $i(t)$  flowing through the inductor for  $t \geq 0$  assuming that  $i(t_0 = 0) = -\frac{U_0}{\omega L} \cos(\omega t_0)$ .



$$\underline{\Phi}(t) = \underline{\Phi}_0 + \frac{1}{\omega} U_0 - \frac{U_0}{\omega} \cos(\omega t)$$

$$i(t) = \frac{1}{L} \underline{\Phi}(t) = \frac{\underline{\Phi}_0}{L} + \frac{U_0}{WL} - \frac{U_0}{WL} \cos(\omega t)$$

$$= \frac{\underline{\Phi}_0}{L} + \frac{U_0}{WL} - \frac{U_0}{WL} = \frac{\underline{\Phi}_0}{L} = -\frac{U_0}{WL}$$

- f) Give the flux  $\Phi(t)$  for  $t \geq 0$ .

$$\begin{aligned}\underline{\Phi}(t) &= \underline{\Phi}_0 + \frac{U_0}{\omega} - \frac{U_0}{\omega} \cos(\omega t) \\ &= -\frac{U_0}{\omega} \cos(\omega t)\end{aligned}$$

alternatively :  $U(t) = L i(t)$   
 $i(t) = \frac{1}{L} U(t)$

$$= \frac{U_0}{L} \sin(\omega t)$$

$$i(t) = \int_0^t \frac{U_0}{L} \sin(\omega t') dt'$$

$$= \frac{U_0}{L} \left[ -\cos(\omega t') \cdot \frac{1}{\omega} \right]_0^t$$


$$= \frac{U_0}{WL} - \frac{U_0}{WL} \cos(\omega t)$$

g) Determine the charge  $q(t)$  for  $t \geq 0$  under the assumption that  $q(0) = \frac{U_0}{\omega^2 L}$ .

$$\begin{aligned} q(t) &= q(0) + \int_0^t i(t') dt' \\ &= \frac{U_0}{\omega^2 L} + \int_0^t -\frac{U_0}{\omega L} \cos(\omega t') dt' \\ &= \frac{U_0}{\omega^2 L} + \left[ -\frac{U_0}{\omega L} \sin(\omega t') \frac{1}{\omega} \right]_0^t \\ &= \frac{U_0}{\omega^2 L} - \frac{U_0}{\omega^2 L} \sin(\omega t) \end{aligned}$$

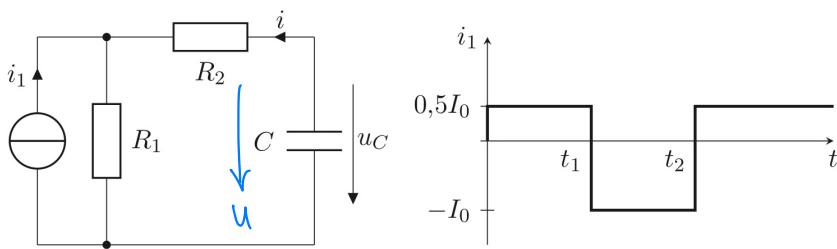
## 7.2 RC-Circuit with Piecewise Linear Excitation

Consider the following circuit with piecewise linear excitation  $i_1$ .




- a) Find the representation of the linear part as a linear source.

Capacitor replaced with OC:

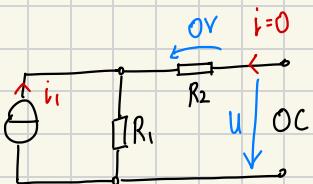


Capacitor replaced with SC:

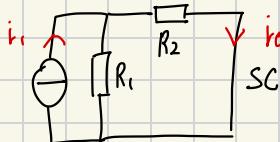

Current div:

$$\frac{i_0}{i_1} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1}{R_1 + R_2}$$

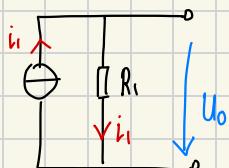
$$i_0 = \frac{R_1}{R_1 + R_2} \cdot i_1$$



$$U_v = R_v i_1$$

internal resistance:

$$R_v = \frac{U_v}{i_0} = R_1 + R_2$$

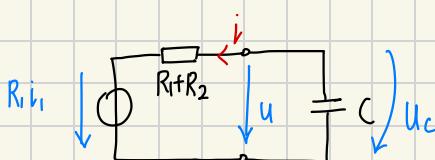


b) What is the time constant  $\tau$  of the circuit?

$$\begin{aligned}\tau &= R_1 C \\ &= (R_1 + R_2) C\end{aligned}$$

c) Determine the voltage  $u_C(t)$  for  $t \geq 0$  when  $u_C(0) = 0$  and where  $t_1 = \tau$  and  $t_2 = 2\tau$ .

$$U_C(t) = R_1 i_1 + (U_{C0} - R_1 i_1) e^{-\frac{t-t_0}{\tau}}$$

$$U_o = R_1 i_1$$

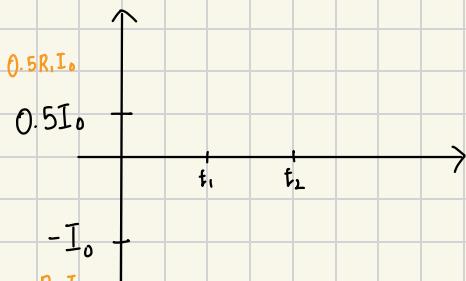

$$= R_1 I_0$$

$$U_C(0) = 0$$

$$0 \leq t \leq t_1 : U_C(t) = 0.5 R_1 I_0 (1 - e^{-\frac{t}{\tau}})$$

$$t = t_1 : U_C(t_1) = 0.5 R_1 I_0 (1 - e^{-1})$$


$$\approx \frac{1}{3} R_1 I_0$$

$$\begin{aligned}t_1 \leq t \leq t_2 : U_C(t) &= -R_1 I_0 + \left(\frac{1}{3} R_1 I_0 + R_1 I_0\right) e^{\frac{t-t_1}{\tau}} \\ &= -R_1 I_0 + \frac{4}{3} R_1 I_0 \cdot e^{-\frac{t_1}{\tau} + 1}\end{aligned}$$

$$U_C(t_2) = -R_1 I_0 + \frac{4}{3} R_1 I_0 \cdot \frac{1}{3} = -\frac{5}{9} R_1 I_0 \quad \nearrow 2\tau$$

$$\begin{aligned}t \geq t_3 : U_C(t) &= 0.5 R_1 I_0 + \left(-\frac{5}{9} R_1 I_0 - 0.5 R_1 I_0\right) e^{-\frac{t-t_2}{\tau}} \\ &= 0.5 R_1 I_0 - \frac{19}{18} R_1 I_0 \cdot e^{-\frac{t-t_2}{\tau}}\end{aligned}$$

d) Sketch  $u_C(t)$ .

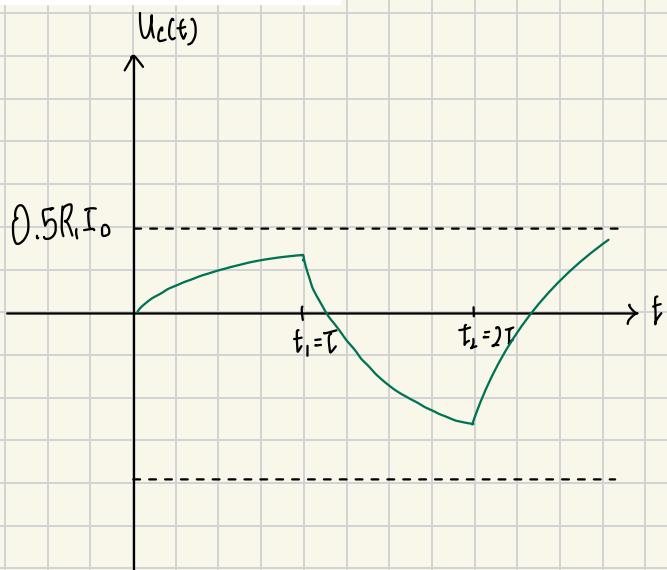


e) Find  $i_C(t)$ .


$$0 \leq t \leq t_1 : i_C(t) = C \cdot \dot{u}(t) = 0.5 I_0 e^{\frac{t}{T}}$$

$$t_1 \leq t \leq t_2 : i_C(t) = -\frac{4}{3} I_0 e^{\frac{-t}{T} + 1}$$

$$t \geq t_2 : i_C(t) = \frac{19}{18} I_0 e^{-\frac{t}{T} + 2}$$

f) Sketch  $i_C(t)$ .

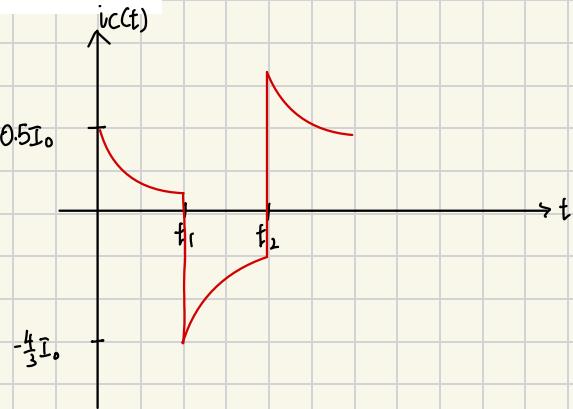

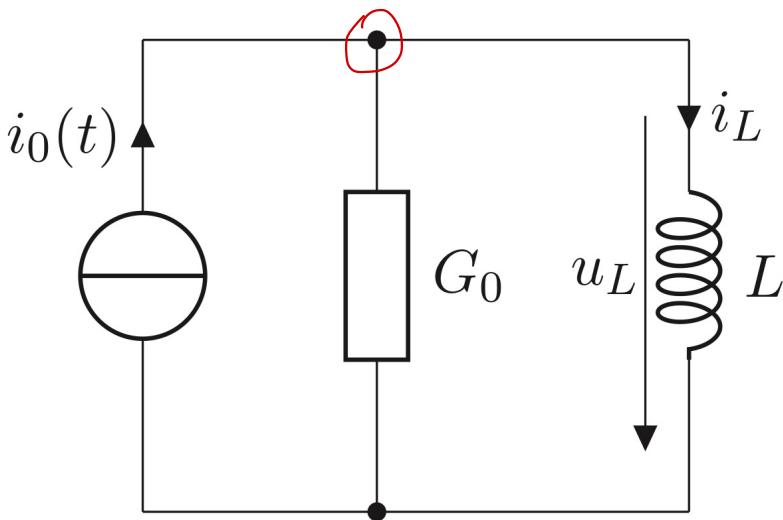

The excitation is given by

$$i_0(t) = \begin{cases} 0 & \text{for } t < 0, \\ I_0 e^{-\frac{t}{G_0 L}} \cos(\omega t) & \text{for } t \geq 0. \end{cases}$$

- a) Determine  $i_L(t)$  for  $t > 0$  assuming that  $i_L(0) = I_0$ . Use the abbreviation  $\tau = G_0 L$ .

$$\text{KCL: } -i_0 + i_L + G_0 u_L = 0$$

$$u_L = L \cdot \overset{\circ}{i}_L$$

$$-i_0 + i_L + G_0 L \overset{\circ}{i}_L = 0$$

$$\overset{\circ}{i}_L = \frac{1}{G_0 L} i_L + \frac{1}{G_0 L} i_0$$

$$t \geq 0 : i_0(t) = I_0 e^{-\frac{t}{G_0 L}} \cos(\omega t)$$

$$\tau = G_0 L, \quad i_L(0) = I_0 \xrightarrow{t=0} = 0$$


$$i_L(t) = I_0 e^{-\frac{t}{\tau}} + \int_{t_0=0}^t \frac{1}{\tau} e^{-\frac{t-t'}{\tau}} I_0 \cdot e^{\frac{t'}{\tau}} \cos(\omega t') dt'$$

$$= I_0 e^{-\frac{t}{\tau}} + \int_0^t \frac{1}{\tau} e^{-\frac{t}{\tau}} \cdot I_0 \cos(\omega t') dt'$$


$$= I_0 e^{-\frac{t}{T}} + \frac{1}{\omega T} e^{-\frac{t}{T}} \cdot I_0 \sin(\omega t)$$
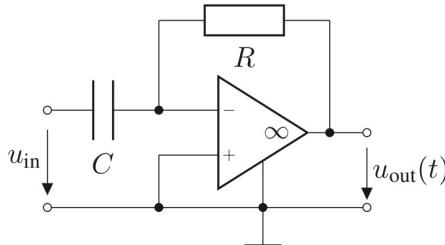
## 7.5 Integrator and Differentiator

Given is following circuit. The Op-Amp is operated in the linear region.



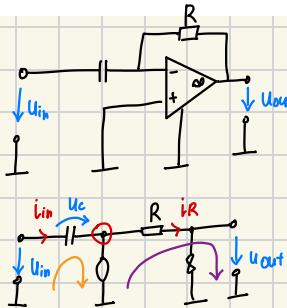- a) Find the output voltage  $u_{\text{out}}(t)$  depending on the input voltage  $u_{\text{in}}$  for  $t > t_0$ .



$$\text{KVL: } -u_{\text{in}} + u_c = 0$$

$$u_c = u_{\text{in}}$$

$$\text{Cap: } i_{\text{in}} = C \dot{u}_{\text{in}}$$

$$\text{KCL: } i_{\text{in}} - i_R = 0$$

$$i_R = i_{\text{in}} = C \dot{u}_{\text{in}}$$


$$\text{KVL: } R i_R + u_{\text{out}} = 0$$

$$u_{\text{out}} = -R i_R$$

$$= -R C \dot{u}_{\text{in}}$$

$\Rightarrow$  differentiator

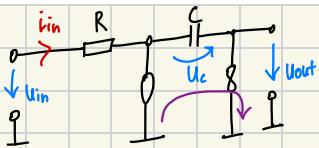- b) Exchange the capacitor and the resistor. Determine the output voltage  $u_{\text{out}}(t)$  for  $t > t_0$  and  $u_C(t_0) = 0$ .



$$U_{\text{in}} = R i_{\text{in}}$$

$$i_{\text{in}} = \frac{1}{R} U_{\text{in}}$$

$$\text{Cap. : } i_{\text{in}} = C \dot{U}_c$$

$$\frac{1}{R} U_{\text{in}} = C \dot{U}_c$$

$$U_c(t) = \frac{1}{RC} \int U_{\text{in}}(t') dt'$$

$$\text{KVL: } U_c + U_{\text{out}} = 0$$


$$U_{\text{out}}(t) = -U_c(t)$$

$$= -\frac{1}{RC} \int U_{\text{in}}(t') dt'$$

$\Rightarrow$  integrator

## 8.1 Formulation of State Equations (1)

Given is following circuit.

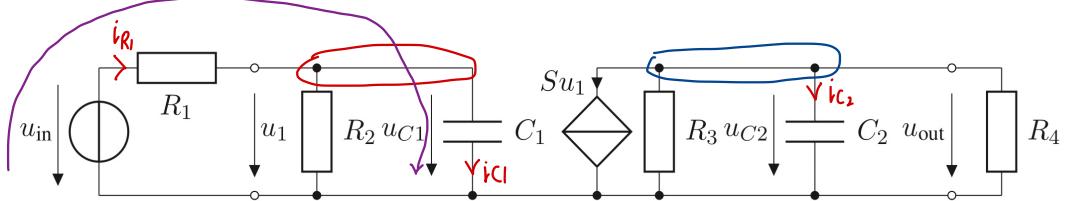

- a) Formulate the state equations. Give  $x$ ,  $A$ ,  $b$ , and  $v$ .

$$\underline{X} = \begin{bmatrix} U_{C1}, U_{C2} \end{bmatrix}^T$$

excitation  $\underline{V} = U_{in}$

$$KCL: -i_{R1} + i_{C1} + \frac{1}{R_2} U_{C1} = 0$$

$$KVL: -U_{in} + R_1 i_{R1} + U_{C1} = 0$$

$$i_{R1} = \frac{U_{in} - U_{C1}}{R_1}$$

Sub into KCL:

$$i_{C1} = -\frac{1}{R_2} U_{C1} + \frac{U_{in} - U_{C1}}{R_1}$$

$$= -\left(\frac{1}{R_1} + \frac{1}{R_2}\right) U_{C1} + \frac{1}{R_1} U_{in}$$

$$i_{C1} = C_1 \dot{U}_{C1}, \quad i_{C2} = C_2 \dot{U}_{C2}$$

$$\dot{U}_{C1} = -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) U_{C1} + \frac{1}{R_1 C_1} U_{in}$$

$$\dot{U}_{C2} = -\sum_{C_2} U_{C1} - \left(\frac{1}{R_3 C_2} + \frac{1}{R_4 C_2}\right) U_{C2}$$

$$\dot{\underline{X}} = A \underline{X} + B \underline{V} \quad \text{search for } U_{in}$$

$$\underline{B} = \begin{bmatrix} \frac{1}{R_1 C_1} \\ 0 \end{bmatrix}$$

$$U_{C_1} \& U_{C_2}$$

$$\downarrow \tilde{A} = \begin{bmatrix} -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) & 0 \\ -\frac{S}{C_2} & -\left(\frac{1}{R_3 C_2} + \frac{1}{R_4 C_2}\right) \end{bmatrix}$$

b) Find the output equation. Give  $C^T$  and  $d$ .

$$U_{out} = U_{C_2} = [0, 1] \cdot \underline{x} + 0 \cdot v$$

$$\underline{C}^T = [0, 1], \quad d = 0$$

$$y = U_{C_2} = \underline{C}^T \underline{x} + dv$$

$$\Rightarrow d = 0$$


$$U_{C_2} = \underline{C}^T \underline{x}$$

$$= \underbrace{[0, 1]}_{C^T}^T \cdot \underline{x}$$


$$y = U_{C_2} = 0 \cdot U_{C_1} + 1 \cdot U_{C_2}$$
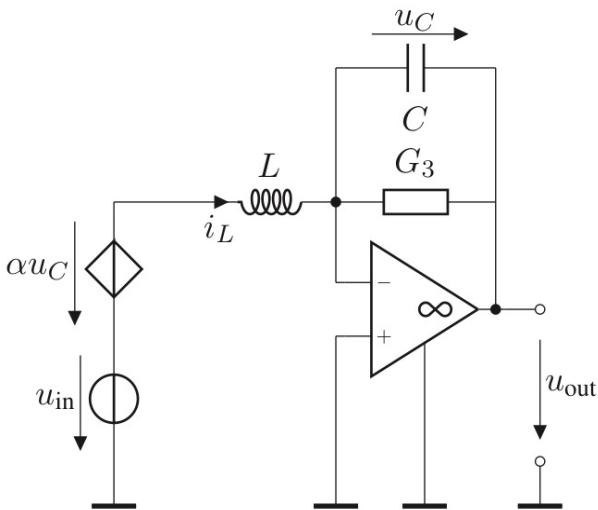
## 8.2 Formulation of State Equations (2)

Given is following circuit with an Op-Amp operated in the linear region.



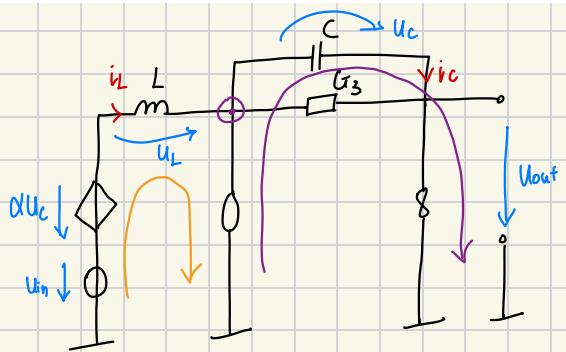- a) Formulate the state equations. Give  $x$ ,  $A$ ,  $b$ , and  $v$  an.



inductor must find KVL  
with  $u_L$

Capacitor find KCL with  $i_C$

$$v = u_{in}$$

$$\underline{x} = [i_L, u_C]^T$$

$$KVL : -U_{in} - \alpha U_C + U_L = 0$$

$$U_L = \alpha U_C + U_{in}$$

$$KCL : -i_L + i_C + G_3 U_C = 0$$

$$i_C = i_L - G_3 U_C$$

$$U_L = L \dot{i}_L , \quad i_C = C \dot{U}_C$$

$$\dot{i}_L = \frac{\alpha}{L} U_C + \frac{1}{L} U_{in}$$

$$\dot{U}_C = \frac{1}{C} \dot{i}_L - \frac{G_3}{C} U_C$$

$$b = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \quad A = \begin{bmatrix} 0 & \frac{\alpha}{L} \\ \frac{1}{C} & -\frac{G_3}{C} \end{bmatrix}$$

b) Find the output equation. Give  $c^T$  and  $d$ .

$$KVL: U_C + U_{out} = 0$$

$$U_{out} = -U_C$$


$$= [0, -1] X + 0 \cdot U_{in}$$

$$C^T = [0, -1]$$

$$d = 0$$
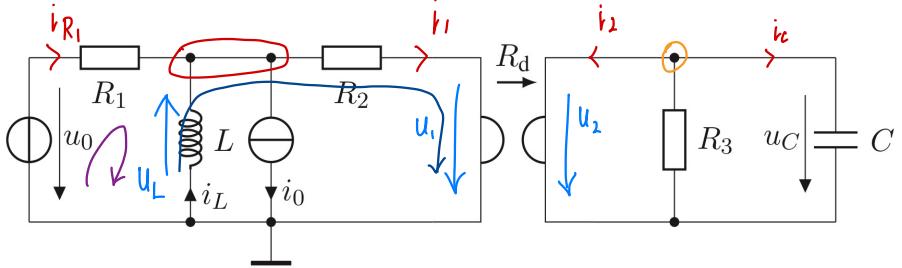
### 8.3 Formulation of State Equations (3)

Given is the following circuit with a gyrator.



- a) Find the parameters  $x$ ,  $A$ ,  $B$ , and  $v$ .

$$\text{gyrator: } U_1 = R_d (-i_2)$$

$$U_2 = R_d i_1$$

$$\text{KCL: } -i_{R1} - i_L + i_0 + i_1 = 0 \rightarrow -i_{R1} - i_L + i_0 + \frac{1}{R_d} U_C = 0$$

$$\text{KVL: } -U_0 + R_1 i_{R1} - U_L = 0$$

$$i_{R1} = -i_L + i_0 + \frac{1}{R_d} U_C$$

$$U_2 = U_C = R_d i_1$$

$$i_1 = \frac{1}{R_d} U_C$$

$$\rightarrow U_L = -U_0 + R_1 i_{R1}$$

$$U_L = -U_0 + R_1 (-i_L + i_0 + \frac{1}{R_d} U_C)$$

$$= -R_1 i_L + \frac{R_1}{R_d} U_C + R_1 i_0 - U_0$$

$$\text{KCL: } i_2 + i_C + \frac{1}{R_3} U_C = 0$$

$$-\frac{1}{R_d} U_1 + i_C + \frac{1}{R_3} U_C = 0$$

$$\text{KVL: } U_L + U_1 + R_2 i_1 = 0$$

$$U_L + U_1 + \frac{R_2}{R_d} U_C = 0 \rightarrow U_1 = -U_L - \frac{R_2}{R_d} U_C$$

$$\frac{1}{Rd}U_L + \frac{R_2}{R^2d}U_C + i_C + \frac{U_o}{R_3} = 0$$

Sub  $U_C$  from above :

$$-\frac{R_1}{R^2d}i_L + \frac{R_1}{R^2d}U_C + \frac{R_1}{Rd}i_o - \frac{U_o}{Rd} + \frac{R_2}{R^2d}U_C + i_C + \frac{U_o}{R_3} = 0$$

$$i_C = -\left(\frac{R_1}{R^2d} + \frac{R_2}{R^2d} + \frac{1}{R_3}\right)U_C + \frac{R_1}{Rd}i_L - \frac{R_1}{Rd}i_o + \frac{U_o}{Rd}$$

$$i_L^o = -\frac{R_1}{L}i_L + \frac{R_1}{RdL}U_C + \frac{R_1}{L}i_o - \frac{1}{L}U_o$$

$$U_C^o = -\left(\frac{R_1}{R^2dC} + \frac{R_2}{R^2dC} + \frac{1}{R_3C}\right)U_C + \frac{R_1}{RdC}i_L - \frac{R_1}{RdC}i_o + \frac{1}{RdC}U_o$$


$$\underline{X} = \begin{bmatrix} i_L \\ U_C \end{bmatrix}, \quad \underline{A} = \begin{bmatrix} -\frac{R_1}{L} & \frac{R_1}{RdL} \\ \frac{R_1}{RdC} & -\left(\frac{R_1}{R^2dC} + \frac{R_2}{R^2dC} + \frac{1}{R_3C}\right) \end{bmatrix}$$

$$\underline{Y} = \begin{bmatrix} i_o \\ U_o \end{bmatrix}, \quad \underline{B} = \begin{bmatrix} \frac{R_1}{L} & -\frac{1}{L} \\ -\frac{R_1}{RdC} & \frac{1}{RdC} \end{bmatrix}$$

$$\underline{X}^o = \underline{A} \underline{X} + \underline{B} \underline{Y}$$
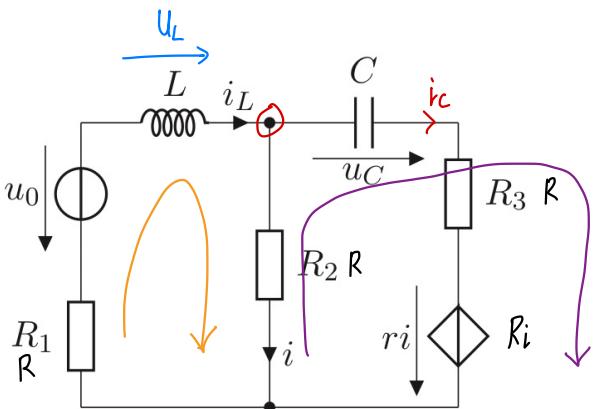
## 8.4 Formulation of State Equations (4)

Consider the following circuit with  $R_1 = R_2 = R_3 = r = R$ .



- Formulate the state equations.
- Give  $x$ ,  $A$ ,  $b$ , and  $v$ .

$$\text{KVL: } R_i i_L - U_0 + U_L + R_i = 0$$

$$\text{KVL: } -R_i + U_C + R_i c + R_i = 0 \rightarrow R_i c = -U_C$$

$$RC \dot{U}_C = -U_C$$

$$\dot{U}_C = -\frac{1}{RC} U_C$$

$$\text{KCL: } i_L - i_C - i = 0$$

$$i_L + \frac{U_C}{R} - i = 0$$

$$\Rightarrow i = i_L + \frac{U_C}{R}$$


$$R i_L - U_0 + U_L + R i_L + U_C = 0$$

$$U_L = -2R i_L - U_C + U_0$$

$$\dot{i}_L = -\frac{2R}{L} i_L - \frac{1}{L} U_C + \frac{1}{L} U_0$$

$$\underline{X} = \begin{bmatrix} U_C \\ i_L \end{bmatrix}, \quad \underline{A} = \begin{bmatrix} -\frac{1}{RC} & 0 \\ -\frac{1}{L} & -\frac{2R}{L} \end{bmatrix}$$
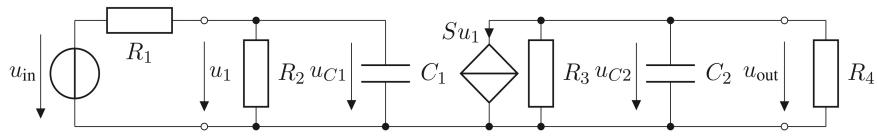
$$\underline{Y} = U_B, \quad \underline{B} = \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix}$$



Equivalent circuit diagram:

$$\dot{U}_{C_1} = \frac{1}{(R_1 || R_2)C_1} U_{C_1} + \frac{1}{(R_2 || R_1)C_1} U_{in} - \frac{R_2}{R_1 + R_2} U_{in}$$

$$\dot{U}_{C_2} = -\frac{1}{R_3 || R_4 C_2} U_{C_2} - \frac{S}{C_2} U_{C_1}$$

## 8.5 Solution of Homogeneous State Equations (1)

Consider the circuit in Problem 8.1.

Given are the following element values:  $R_1 = 1/3 \Omega$ ,  $R_2 = 1 \Omega$ ,  $R_3 = 2 \Omega$ ,  $R_4 = 2 \Omega$ ,  $C_1 = 1 F$ ,  $C_2 = 1 F$ ,  $S = -3 S$ , and  $u_{in} = 0 V$ .

- a) Find the eigenvalues of the state matrix.

$$R_1 || R_2 = \frac{1}{3} \Omega || 1 \Omega$$

$$= \frac{\frac{1}{3} \cdot 1}{\frac{1}{3} + 1} = \frac{1}{3} \frac{1}{4/3} = \frac{1}{4} \Omega$$

$$R_3 || R_4 = 1 \Omega$$

$$\dot{U}_{C_1} = -4 \frac{1}{S} U_{C_1}$$

$$\dot{U}_{C_2} = -1 \frac{1}{3} U_{C_2} + 3 \frac{1}{S} U_{C_1}$$

$$\tilde{A} = \begin{bmatrix} -4 & 0 \\ 3 & -1 \end{bmatrix} \frac{1}{s}$$

$$\lambda_1 = -4\frac{1}{s}, \lambda_2 = -1\frac{1}{s}$$

$$(\tilde{A} - \lambda_1 \tilde{I}) \tilde{q}_1 = 0$$

$$\begin{bmatrix} 0 & 0 \\ 3 & 3 \end{bmatrix} \tilde{q}_1 = 0$$

$$\tilde{q}_1 = \begin{bmatrix} 3 \\ -3 \end{bmatrix} \frac{1}{s}$$

$$\begin{bmatrix} -3 & 0 \\ 3 & 0 \end{bmatrix} \tilde{q}_2 = 0$$

$$\tilde{q}_2 = \begin{bmatrix} 0 \\ -3 \end{bmatrix} \frac{1}{s}$$

- c) Give the resulting general solution and the general solution for  $u_{C1}(t_0) = 1 \text{ V}$  and  $u_{C2} = -1.5 \text{ V}$ .

$$\begin{aligned} X(t) &= \xi_{01} e^{\lambda_1 t} \tilde{q}_1 + \xi_{02} e^{\lambda_2 t} \tilde{q}_2 \\ &= \xi_{01} e^{-4\frac{1}{s}} \begin{bmatrix} 3 \\ -3 \end{bmatrix} + \xi_{02} e^{-1\frac{1}{s}} \begin{bmatrix} 0 \\ -3 \end{bmatrix} \frac{1}{s} \end{aligned}$$

$$X(0) = \begin{bmatrix} 1V \\ -1.5V \end{bmatrix} = \xi_{01} \begin{bmatrix} 3 \\ -3 \end{bmatrix} \frac{1}{s} + \xi_{02} \begin{bmatrix} 0 \\ -3 \end{bmatrix} \frac{1}{s}$$

$$1V = \xi_{01} 3 \frac{1}{s} \rightarrow \xi_{01} = \frac{1}{3} Vs$$


$$-1.5V = \frac{1}{3} Vs (-3) \frac{1}{s} + \xi_{02} (-3) \frac{1}{s}$$

$$-0.5V = \xi_{02} (-3) \frac{1}{s}$$



$$\rightarrow \xi_{02} = \frac{1}{6} Vs$$

$$x(t) = 1Ve^{-4\frac{t}{5}} \begin{bmatrix} 1 \\ -1 \end{bmatrix} + \frac{1}{2}Ve^{-\frac{t}{5}} \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

d) Draw  $u_{C1}(t)$  and  $u_{C2}(t)$ .

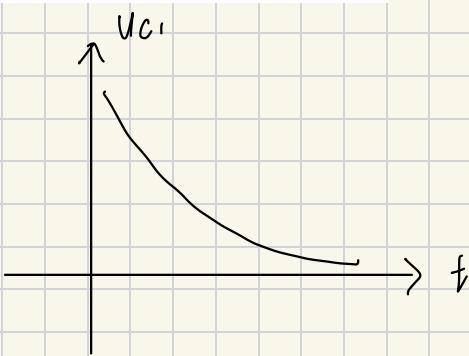

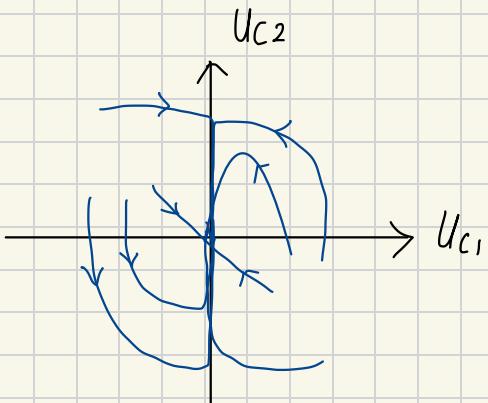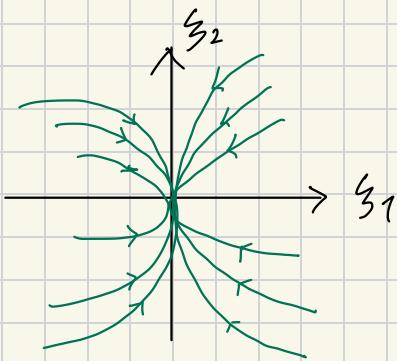e) Sketch the resulting phase portrait in the  $u_{C1}$ - $u_{C2}$ -plane.



$$a) R_1 \parallel R_2 = \frac{1}{4} \Omega$$

$$R_3 \parallel R_4 = 1 \Omega$$

$$C_1 = C_2 = -1F$$


$$S = 3S$$

$$\dot{U}_{C1} = 4 \frac{1}{5} U_{C1}$$


$$\dot{U}_{C2} = 1 \frac{1}{3} U_{C2} + 3 \frac{1}{5} U_{C1}$$

$$\tilde{A} = \begin{bmatrix} 4 & 0 \\ 3 & 1 \end{bmatrix}$$

b) c) same as 8.5

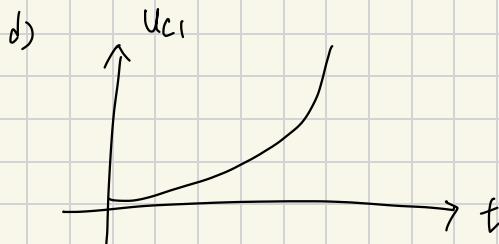

e)

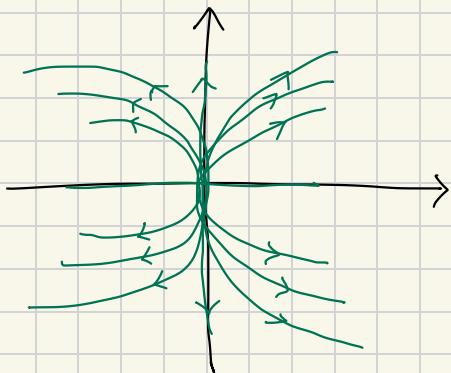

8.7

a)  $R_1 \parallel R_2 = 7\Omega$   
 $R_3 \parallel R_4 = 1\Omega$

$C_1 = 1F$

$C_2 = -1F$




$S = 3S$


$\ddot{U}_{C_1} = -1\frac{1}{3} U_{C_1}$

$\ddot{U}_{C_2} = 1\frac{1}{3} U_{C_2} + 3\frac{1}{3} U_{C_1}$

$$\tilde{A} = \begin{bmatrix} -1 & 0 \\ 3 & 1 \end{bmatrix} \frac{1}{S}$$

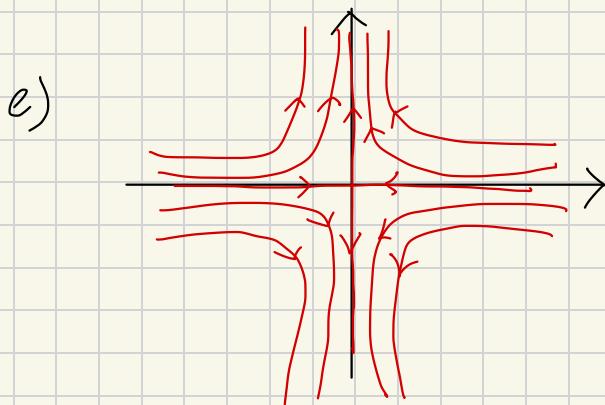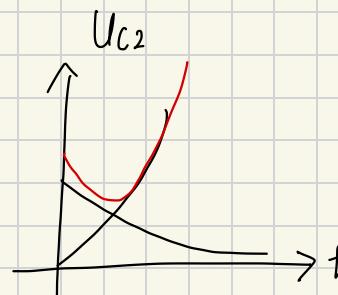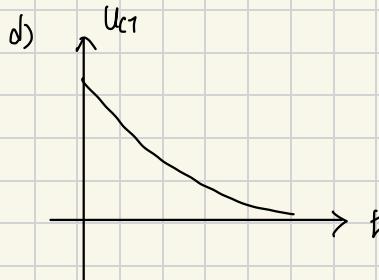$\lambda_1 = -1\frac{1}{3}, \lambda_2 = +7\frac{1}{3}$



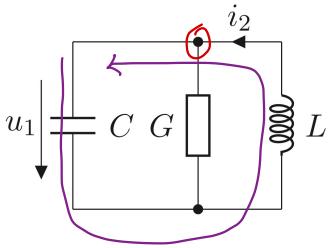

- a) Formulate the state equation. Determine the state matrix  $A$  for  $G = 4\text{S}$ ,  $C = 1\text{F}$ , and  $L = 1/3\text{H}$ .

$$\underline{X} = [u_1, i_2]^T$$

$$\text{KCL: } Cu_1 + Gu_1 - i_2 = 0$$

$$\text{KVL: } u_1 + Li_2 = 0$$

$$\dot{u}_1 = -\frac{G}{C}u_1 + \frac{1}{C}i_2$$

$$\dot{i}_2 = -\frac{1}{L}u_1$$

$$\dot{u}_1 = -4\frac{1}{S}u_1 + \frac{1}{1F}i_2$$

$$\dot{i}_2 = -\frac{3}{H}u_1$$

$$\dot{\underline{X}} = \underline{A}\underline{X}$$

$$\underline{A} = \begin{bmatrix} -4\frac{1}{S} & \frac{1}{1F} \\ -3\frac{1}{H} & 0 \end{bmatrix}$$

- b) Find and sketch the solution for the initial conditions  $u_1(t_0) = 1\text{V}$  and  $i_2(t_0) = -1\text{A}$ .

$$\begin{aligned} \det(\underline{A} - \lambda \underline{I}) &= (-4-\lambda)(-\lambda) + 3\frac{1}{S^2} \\ &= \lambda^2 + 4\lambda\frac{1}{S} + 3\frac{1}{S^2} = 0 \end{aligned}$$

$$\lambda_{1/2} = -2 \pm \sqrt{4-3}$$

$$\begin{aligned} &= -2 \pm 1 \\ \lambda_1 &= -1\frac{1}{S}, \quad \lambda_2 = -3\frac{1}{S} \end{aligned}$$

$$(A - \lambda_1 I) q_1 = \begin{bmatrix} -3\frac{1}{s} & \frac{1}{1F} \\ -3\frac{1}{H} & 1\frac{1}{3} \end{bmatrix} q_1 = 0$$

$$q_1 = \begin{bmatrix} 1S \\ 3F \end{bmatrix}$$

$$\begin{bmatrix} -1\frac{1}{s} & \frac{1}{1F} \\ -3\frac{1}{H} & 3\frac{1}{s} \end{bmatrix} q_2 = 0$$

$$q_2 = \begin{bmatrix} 1S \\ 1F \end{bmatrix}$$

$$X(t) = \xi_{01} e^{-\frac{t}{s}} \begin{bmatrix} 1S \\ 3F \end{bmatrix} + \xi_{02} e^{-\frac{3t}{s}} \begin{bmatrix} 1S \\ 1F \end{bmatrix} \quad \left( \frac{-1F}{1s} \right) x$$

$$t_0 = 0 :$$

$$X(0) = \begin{bmatrix} 1V \\ -1A \end{bmatrix} = \xi_{01} \begin{bmatrix} 1S \\ 3F \end{bmatrix} + \xi_{02} \begin{bmatrix} 1S \\ 1F \end{bmatrix}$$

$$\frac{1F}{1s} = 1S$$

$$-1A = \xi_{01} 1F / -\xi_{02} 1F$$

$$-1A = \xi_{01} 3F + \xi_{02} 1F$$

$$-2A = \xi_{01} (2F) \rightarrow 2S \cdot s$$


$$\xi_{01} = -1 \frac{V}{s}$$

$$\xi_{01} 1S + \xi_{02} 1S = 1V$$

$$\xi_{02} = 2 \frac{V}{s}$$

$$X(t) = 1 \frac{V}{s} e^{-\frac{t}{s}} \begin{bmatrix} 1S \\ 3F \end{bmatrix} + 2 \frac{V}{s} e^{-\frac{3t}{s}} \begin{bmatrix} 1S \\ 1F \end{bmatrix}$$

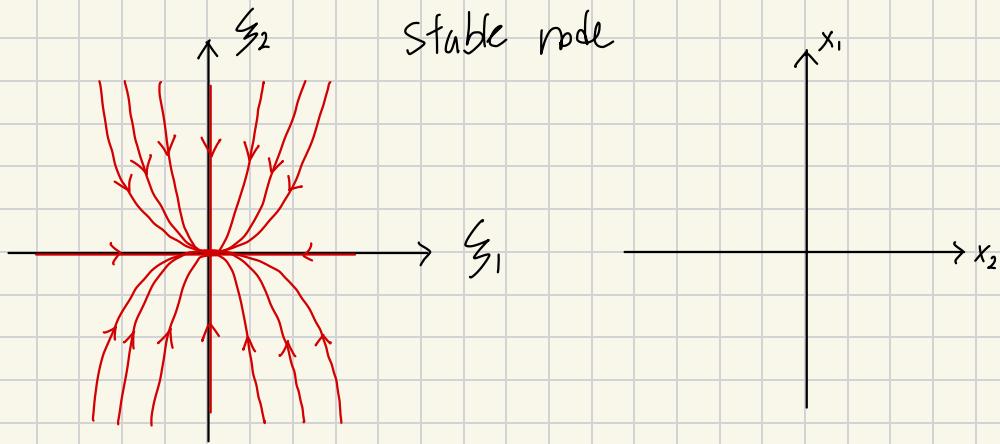c) Sketch corresponding phase portrait in the  $x_1$ - $x_2$ -plane.



$$\lambda_2 < \lambda_1 < 0$$

- d) Determine and sketch the solution for  $G = -4\text{S}$ ,  $C = 1\text{F}$ , and  $L = 1/3\text{H}$ . The initial conditions are  $u_1(t_0) = 1\text{V}$  and  $i_2(t_0) = -1\text{A}$ .

$$4\frac{1}{S}u_1 + \frac{1}{1F}i_2 = \dot{u}_1$$

$$-\frac{3}{H}u_1 = \dot{i}_2$$


$$\tilde{A} = \begin{bmatrix} 4\frac{1}{S} & \frac{1}{1F} \\ -3\frac{1}{H} & 0 \end{bmatrix}$$

$$\lambda^2 - 4\lambda\frac{1}{S} + 3\frac{1}{S^2} = 0$$

$$\lambda_{1/2} = +2 \pm \sqrt{1}$$

$$\begin{aligned}\lambda_1 &= 3\frac{1}{S} \\ \lambda_2 &= +1\frac{1}{S}\end{aligned}$$

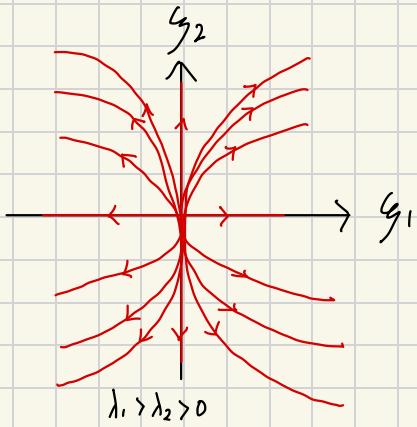e) Sketch the corresponding phase portrait in the  $x_1$ - $x_2$ -plane.



Unstable node

f) Find and sketch the solution for  $G = 1\text{S}$ ,  $C = 1\text{F}$ , and  $L = -1/2\text{H}$ . The initial conditions are  $u_1(t_0) = -1\text{V}$  and  $i_2(t_0) = -1.5\text{A}$ .

$$\tilde{A} = \begin{bmatrix} -1\frac{1}{3} & \frac{1}{1\text{F}} \\ 2\frac{1}{H} & 0 \end{bmatrix}$$


$$\lambda^2 + \lambda \frac{1}{3} - 2\frac{1}{3^2} = 0$$

$$\begin{aligned} \lambda_{1/2} &= -\frac{1}{2} \pm \sqrt{\frac{1}{4} + 2} \\ &= -\frac{1}{2} \pm \frac{3}{2} \end{aligned}$$

$$\lambda_1 = 1\frac{1}{3}$$

$$\lambda_2 = -2\frac{1}{3}$$

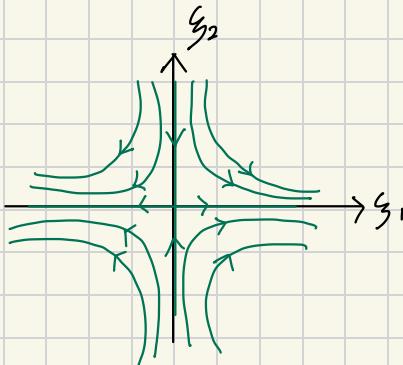g) Sketch the corresponding phase portrait in the  $x_1$ - $x_2$ -plane.



Saddle point


- h) Determine and sketch the solution for  $G = 0 \text{ S}$ ,  $C = 1 \text{ F}$ , and  $L = 1 \text{ H}$ . The initial conditions are  $u_1(t_0) = 1 \text{ V}$  and  $i_2(t_0) = 0 \text{ A}$ .

$$\tilde{A} = \begin{bmatrix} 0 & \frac{1}{1F} \\ -\frac{1}{1H} & 0 \end{bmatrix}$$

$$\lambda^2 + \frac{1}{S^2} = 0$$

$$\lambda_{1/2} = \pm j \frac{1}{S}$$

i)

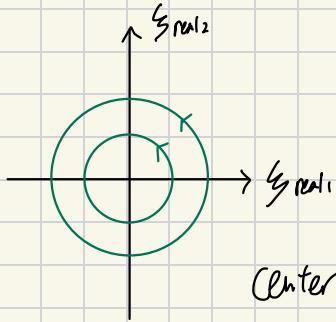


- j) Find and sketch the solution for  $G = 2 \text{ S}$ ,  $C = 1 \text{ F}$ , and  $L = 1/2 \text{ H}$ . The initial conditions are  $u_1(t_0) = -2 \text{ V}$  and  $i_2(t_0) = -2 \text{ A}$ .

$$\tilde{A} = \begin{bmatrix} -2 \frac{1}{S} & 1 \frac{1}{F} \\ -2 \frac{1}{F} & 0 \end{bmatrix}$$

$$\lambda^2 + 2\lambda \frac{1}{S} + 2 \frac{1}{S^2} = 0$$

$$\lambda_{1/2} = -1 \pm \sqrt{-2}$$

$$= -1 \pm j$$

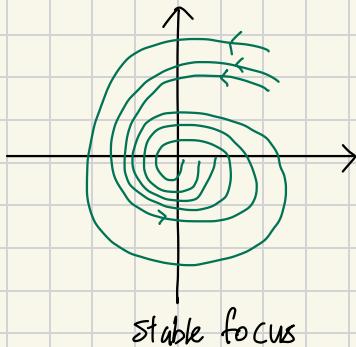

k) Sketch the corresponding phase portrait in the  $\xi_{\text{real}1}\text{-}\xi_{\text{real}2}$ -plane.

Gegeben seien nun die Elementwerte  $G = -2 \text{ S}$ ,  $C = 1 \text{ F}$ , and  $L = 1/2 \text{ H}$ .


$$\tilde{A} = \begin{bmatrix} 2\frac{1}{3} & 1\frac{1}{12} \\ -2\frac{1}{12} & 0 \end{bmatrix}$$

$$\lambda^2 - 2\frac{1}{3}\lambda + 2\frac{1}{3^2} = 0$$

$$\lambda_{1/2} = 1 \pm \sqrt{1}$$


$$= 1 \pm j$$
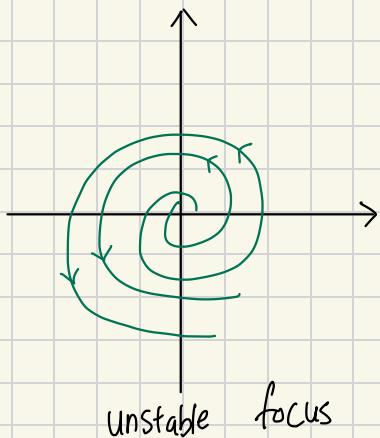
$$\lambda_1 = 1+j, \quad \lambda_2 = 1-j$$


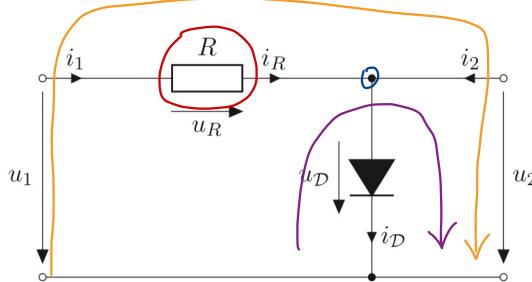
### 3.1 Representation Forms of Two-Ports

Given is the following non-linear two-port consisting of an Ohmic resistor and a pn-diode.



Use the conductance  $G = \frac{1}{R}$  in case that the resulting expression can be simplified.

- a) Find  $u_R$ ,  $u_D$ ,  $i_R$ , and  $i_D$  depending on the port quantities.

$$\text{KVL: } -U_1 + U_R + U_2 = 0$$

$$U_R = U_1 - U_2$$

$$\text{KVL: } -U_D + U_2 = 0$$

$$U_D = U_2$$

$$\text{KCL: } -i_1 + i_R = 0$$

$$i_R = i_1$$

$$\text{KCL: } i_D - i_1 - i_2 = 0$$

$$i_D = i_1 + i_2$$

- b) Give the representations for the two one-ports included in the given two-port, both in voltage- and in current-controlled form.

$$U_R = R i_R$$

$$i_R = G U_R$$

$$i_D = I_S \left( e^{\frac{U_D}{U_T}} - 1 \right)$$

$$U_D = U_T \ln \left( \frac{i_D}{I_S} + 1 \right)$$

Now derive the following six explicit representations of the two-port.

c) Voltage-controlled representation:  $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = g \left( \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \right)$

$$U_R = U_1 - U_2$$

$$i_R = G U_R$$

$$i_1 = G U_1 - G U_2$$

$$i_D = i_1 + i_2$$

$$i_2 = i_D - i_1$$

$$U_D = U_2$$

$$i_D = I_s (e^{\frac{U_2}{U_T}} - 1)$$

$$i_2 = I_s (e^{\frac{U_2}{U_T}} - 1) - G U_1 + G U_2$$

$$g(U_1, U_2) = \begin{bmatrix} G U_1 - G U_2 \\ I_s (e^{\frac{U_2}{U_T}} - 1) - G U_1 + G U_2 \end{bmatrix}$$

d) Current-controlled representation:  $\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = r \left( \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \right)$

$$i_D = i_1 + i_2$$

$$U_D = U_T \ln \left( \frac{i_1 + i_2}{I_s} + 1 \right) = U_2$$

$$U_1 = U_R + U_2 = R i_1 + U_2$$

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} R i_1 + U_T \ln \left( \frac{i_1 + i_2}{I_s} + 1 \right) \\ U_T \ln \left( \frac{i_1 + i_2}{I_s} + 1 \right) \end{bmatrix}$$

e) Hybrid representation:  $\begin{bmatrix} u_1 \\ i_2 \end{bmatrix} = h \left( \begin{bmatrix} i_1 \\ u_2 \end{bmatrix} \right)$

$$U_1 = U_R + U_2$$

$$U_1 = R_{V_1} + U_2$$

$$i_2 = i_D - i_1$$

$$= I_s(e^{\frac{U_2}{U_T}} - 1) - i_1$$

f) Transmission representation:  $\begin{bmatrix} u_1 \\ i_1 \end{bmatrix} = a \left( \begin{bmatrix} u_2 \\ -i_2 \end{bmatrix} \right)$

$$U_D = U_2$$

$$i_D = I_s(e^{\frac{U_2}{U_T}} - 1)$$

$$i_1 = i_D - i_2$$

$$= I_s(e^{\frac{U_2}{U_T}} - 1) + (-i_2)$$

$$U_1 = U_R + U_2$$

$$= R_{V_1} + U_2$$

$$U_1 = RI_s(e^{\frac{U_2}{U_T}} - 1) + R(-i_2) + U_2$$

g) Inverse transmission representation:  $\begin{bmatrix} u_2 \\ i_2 \end{bmatrix} = a' \left( \begin{bmatrix} u_1 \\ -i_1 \end{bmatrix} \right)$

$$U_2 = U_1 - U_R$$

$$= U_1 + R(-i_1)$$

$$i_2 = i_D - i_1$$

$$i_D = I_s(e^{\frac{U_2}{U_T}} - 1)$$

$$= I_s(e^{\frac{(U_1 + RC - i_1)}{U_T}} - 1)$$

$$i_2 = I_s \left( e^{\frac{u_t + R(i_1)}{u_r} - 1} \right) + (-i_1)$$

h) Inverse hybrid representation:  $\begin{bmatrix} i_1 \\ u_2 \end{bmatrix} = h' \left( \begin{bmatrix} u_1 \\ i_2 \end{bmatrix} \right)$

$$i_1 = v_R = G u_R$$

$$u_R = U_1 - U_2$$

$$i_1 = G u_1 - G u_2$$

$$U_2 = U_T \ln \left( \frac{i_D}{I_s} + 1 \right)$$


$$i_D = i_1 + i_2$$

$$U_2 = U_T \ln \left( \frac{i_1 + i_2}{I_s} + 1 \right)$$

$$i_1 = G u_1 - G \cdot U_T \ln \left( \frac{i_1 + i_2}{I_s} + 1 \right)$$

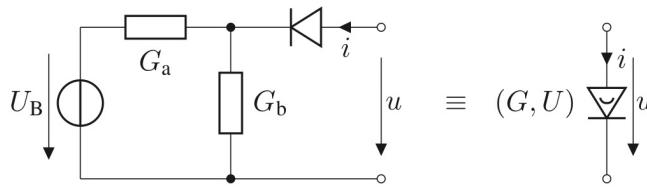
## 2.8 Realization of a Piecewise Linear Resistor

The following circuit  $\mathcal{S}$  realizes a concave resistor.



Firstly, the parameters  $G$  and  $U$  of the equivalent concave resistor are determined depending on the parameters  $U_B$ ,  $G_a$ , and  $G_b$  of  $\mathcal{S}$ .

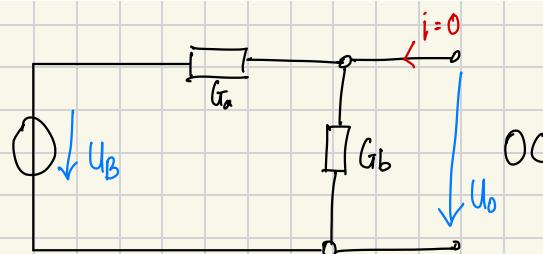- a) Find the breakthrough point of the piecewise linear circuit  $\mathcal{S}$ . To this end, assume that the diode is also operated in its breakthrough point.




Voltage divider:

$$\frac{U_o}{U_B} = \frac{\frac{1}{G_b}}{\frac{1}{G_a} + \frac{1}{G_b}} = \frac{G_a}{G_a + G_b}$$

$$U_o = \frac{G_a}{G_a + G_b} U_B$$

$$a) U_o = \frac{G_a}{G_a + G_b} U_B$$

$$b) G = G_a + G_b$$

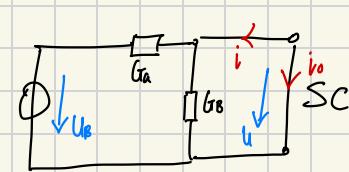


$$SC: U_o = 0$$

$$i_o = G_a U_B$$


$$R_{\text{inf}} = \frac{U_o}{i_o} = \frac{1}{G_a + G_b}$$

$$U_o = \frac{G_a}{G_a + G_b} U_B$$

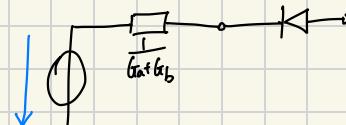

II
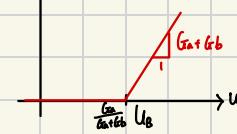
$$c) \left( G_a + G_b, \frac{G_a}{G_a + G_b} U_B \right)$$



- b) Determine the slope  $G$  of the right segment of the characteristic of  $\mathcal{S}$  if the diode is operate in the conductive region.

- c) Draw the characteristic of  $\mathcal{S}$  in the  $u$ - $i$ -plane and label the axes.

- d) Express  $G_a$  and  $G_b$  depending on the parameters  $U$  and  $G$ . These equations constitute the *design rule* for  $\mathcal{S}$ .

$$d) \quad U = \frac{G_a}{G} U_B$$

$$G_a = G \cdot \frac{U}{U_B}$$

$$G_x = G_a + G_b$$

$$\begin{aligned} G_b &= G - G_a \\ &= G - (G \cdot \frac{U}{U_B}) \\ &= G(1 - \frac{U}{U_B}) \end{aligned}$$

- e) What are the conditions for  $G$  and  $U$  such that the circuit  $\mathcal{S}$  is equivalent to the concave resistor  $(G, U)$  can be realized on a chip?

$$G_a \geq 0$$

$$U > 0$$

$$G \geq 0$$


---


$$1 - \frac{U}{U_B} \geq 0$$

$$U \leq U_B$$


- f) Simplify  $\mathcal{S}$  and the design rule for the case that  $U = 0$ .

$$G_a = 0$$


$$G_b = G$$

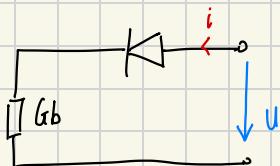

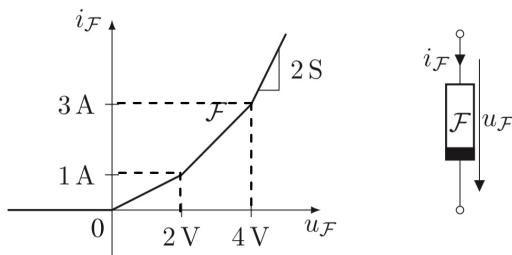The piecewise linear resistor  $\mathcal{F}$  with following characteristic is now realized.



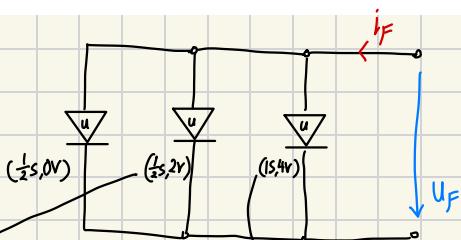- g) Implement  $\mathcal{F}$  as the parallel connection of three concave resistors  $(G_j, U_j)$ ,  $j \in \{1, 2, 3\}$  and give the corresponding parameter values.



- h) Realize  $\mathcal{F}$  with ideal diodes, Ohmic resistors, and the voltage source  $U_B = 10V$ . Draw the complete circuit with all element values.


$$G_b = \frac{1}{2}S, \quad G_a = 0, \quad U = 0V$$

$$G_a = \frac{1}{2}S \cdot \frac{2V}{10V} = \frac{1}{10}S$$

$$G_b = \frac{1}{2}S - \frac{1}{10}S = \frac{2}{5}S$$


$$G_a = 1S \cdot \frac{4V}{10V} = \frac{2}{5}S$$
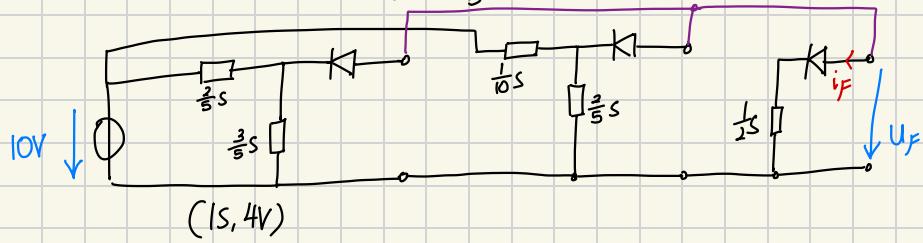
$$G_b = 1S - \frac{2}{5}S = \frac{3}{5}S$$




2.3

ideal diode

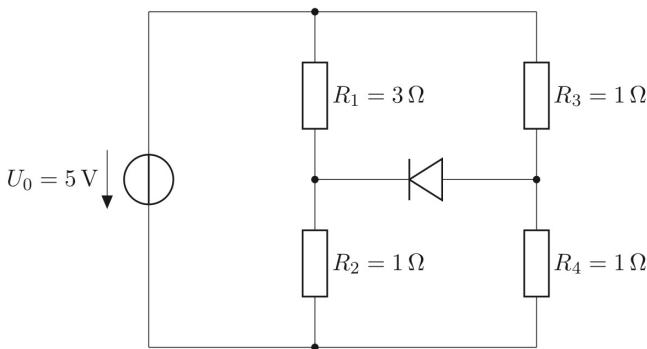

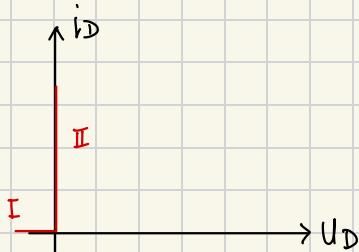
- Find the operating point of the circuit assuming that the diode is operated in the cut-off region.
- Determine the operating point of the circuit assuming that the diode is operated in the conductive region.



a) Diode is in region I

$$i_D = 0, \quad U_D < 0$$

$\Rightarrow$  OC

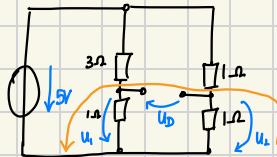

$$KVL: -U_2 + U_D + U_1 = 0$$

$$U_D = U_2 - U_1$$

Use voltage divider for  $U_1, U_2$

$$U_1 = \frac{1\Omega}{1\Omega+3\Omega} \cdot 5V = \frac{5}{4}V$$

$$U_2 = \frac{1\Omega}{1\Omega+1\Omega} \cdot 5V = \frac{5}{2}V$$


$$U_D = \frac{5}{2}V - \frac{5}{4}V = \frac{5}{4}V > 0$$

Contradiction

b) Diode : II

$$U_D = 0, i_D > 0$$

$\Rightarrow$  SC

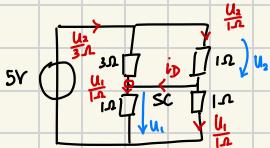


$$KVL: \frac{U_1}{1\Omega} - \frac{U_2}{3\Omega} - i_D = 0$$

$$i_D = \frac{U_1}{1\Omega} - \frac{U_2}{3\Omega}$$

$$\text{Uppercase: } 3\Omega // 1\Omega = \frac{3 \cdot 1}{3+1} = \frac{3}{4}\Omega$$
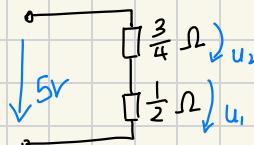
$$1\Omega // 1\Omega = \frac{1 \cdot 1}{1+1} = \frac{1}{2}\Omega$$



$$\frac{U_1}{5V} = \frac{\frac{1}{2}\Omega}{\frac{3}{4}\Omega + \frac{1}{2}\Omega} = \frac{\frac{1}{2}}{\frac{5}{4}} = \frac{2}{5}$$

$$U_1 = 2V$$

$$\frac{U_2}{5V} = \frac{\frac{3}{4}\Omega}{\frac{3}{4}\Omega}$$

$$U_2 = 3V$$

$$i_D = \frac{U_1}{1\Omega} - \frac{U_2}{3\Omega}$$


$$= 2A - 1A$$

$$= 1A > 0 \checkmark$$

$\rightarrow$  ideal diode is conductive
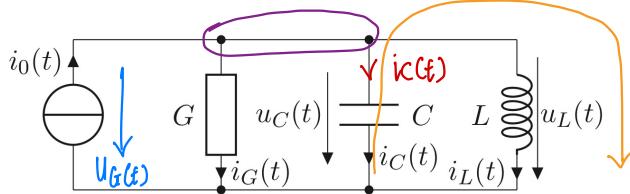
## 9.1 RLC-Resonant Circuit

Consider the following parallel  $RLC$ -resonant circuit with a sinusoidal  $i_0(t) = I_{0m} \cos(\omega t + \pi)$ .



- a) Formulate the state equation for this circuit. Give  $A$ .

$$\underline{x}(t) = [u_C(t), i_L(t)]^T$$

$$v(t) = i_0(t)$$

$$\dot{\underline{x}}(t) = A\underline{x}(t) + b v(t)$$

$$KVL: -u_C(t) + u_L(t) = 0$$

$$u_L(t) = u_C(t)$$

$$L \frac{d}{dt} i_L(t) = u_C(t)$$

$$i_L(t) = \frac{u_C(t)}{L}$$

$$KCL: -i_0(t) + i_G(t) + i_L(t) = 0$$

$$\text{Ohm: } i_G(t) = G u_C(t)$$

$$i_C(t) = -G u_C(t) - i_L(t) + i_0(t)$$

$$u_C(t) = -\frac{G}{C} u_C(t) - \frac{1}{C} i_L(t) + \frac{1}{C} i_0(t)$$

$$A = \begin{bmatrix} -\frac{G}{C} & -\frac{1}{C} \\ \frac{1}{L} & +0 \end{bmatrix}, \quad b = \begin{bmatrix} \frac{1}{C} \\ 0 \end{bmatrix}$$

b) What are the eigenvalues of  $A$ ?

$$\text{def}(\tilde{A} - \lambda \tilde{I}) = \text{def} \begin{bmatrix} -\frac{G}{C} - \lambda & -\frac{1}{C} \\ \frac{1}{L} & -\lambda \end{bmatrix}$$

$$= \lambda^2 + \frac{G}{C}\lambda + \frac{1}{LC}\lambda = 0$$

$$\lambda_{1/2} = -\frac{G}{2C} \pm \sqrt{\left(\frac{G}{2C}\right)^2 - \frac{1}{LC}}$$

$$= -\frac{G}{2C} \pm \frac{G}{2C} \sqrt{1 - \frac{4C^2}{GLC}}$$

$$x^2 + px + q = 0$$

$$x_{1/2} = -\frac{p}{2} \pm \sqrt{\left(\frac{p}{2}\right)^2 - q}$$

$$ax^2 + bx + c = 0$$

$$x_{1/2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

c) Give the relationship between  $i_L(t)$  and  $u_C(t)$ .

$$U_C(t) = i_L(t)$$

$$U_C(t) = L \cdot i_L'(t)$$


d) Express the phasor  $I_L$  depending on the phasor  $U_C$  corresponding to  $u_C(t)$ .

$$U_C = j\omega L I_L$$

$$I_L = \frac{U_C}{j\omega L}$$

e) Determine the phasor  $I_G$  depending on  $U_C$ .

$$I_G = G U_C$$

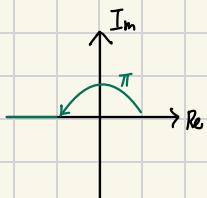

f) Give  $I_0$  corresponding to  $i_0(t)$ .

$$\begin{aligned} I_0 &= I_{0m} e^{j\pi} \\ &= -I_{0m} \end{aligned}$$

g) Find  $I_0$  depending on  $U_C$ .

$$I_C = j\omega C \cdot U_C$$

$$KCL : -I_0 + I_G + I_C + I_L = 0$$

$$I_0 = G U_C + j\omega C U_C + \frac{1}{j\omega L} U_C$$

$$= \left( G + j\omega C + \frac{1}{j\omega L} \right) U_C$$

h) What is, therefore,  $U_C$  depending on  $I_0$ ?

$$U_C = \frac{I}{G + j\omega C + \frac{1}{j\omega L}} I_0$$

$$= \frac{j\omega L}{1 + Gj\omega L + (j\omega)^2 LC}$$

i) Determine the angular frequencies  $\omega$  such that  $U_C$  is real-valued.

$$\frac{x}{y} = \frac{x \cdot y^*}{y \cdot y^*} = \frac{x \cdot y^*}{|y|^2}$$

$$U_C = \frac{j\omega L}{1 + j\omega GL + (j\omega)^2 LC} \cdot \frac{1 - \omega^2 LC - j\omega GL}{1 - \omega^2 LC - j\omega GL} I_0$$

$$= \frac{\omega^2 GL^2 + j\omega L(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega GL)^2} \left( \frac{-I_{om}}{I_0} \right) \in \mathbb{R}$$

for  $U_C \in \mathbb{R}$ :  $\omega L(1 - \omega^2 LC) = 0$

$$\text{I) } \omega = 0 \quad \text{III) } \omega \rightarrow \infty$$

$$\text{II) } 1 - \omega^2 LC = 0$$

$$\omega = \frac{1}{\sqrt{LC}}$$

j) Give the values of  $U_C$  for these angular frequencies.

$$U_C(j0) = 0$$

$$U_C\left(j\frac{1}{\sqrt{LC}}\right) = \frac{\frac{1}{LC} GL^2}{\left(G\frac{1}{\sqrt{LC}}\right)^2} \left(-I_{om}\right) = \frac{\frac{GL}{C}}{G^2 \cdot \frac{1}{LC}} \left(-I_{om}\right)$$

$$= -\frac{1}{G} I_{om}$$

$$U_C(j\infty) = 0$$

zero for low/high frequencies, non-zero for in between



Thus, this circuit is a bandpass and one of these values for  $U_C$  corresponds to the maximum  $U_{C,\max}$  of  $|U_C|$ .

- k) Perform a dual transform of the given circuit with the duality constant  $R_d$ . Draw the resulting circuit.

$$U_{C,\max} = \frac{1}{G} I_{om}$$

parallel connections

$R_d$  → series Connection


Current source

$R_d$  → voltage source


$$G \xrightarrow{R_d} R^d = R_d G$$

$$( \xrightarrow{R_d} L^d = R_d^2 C$$
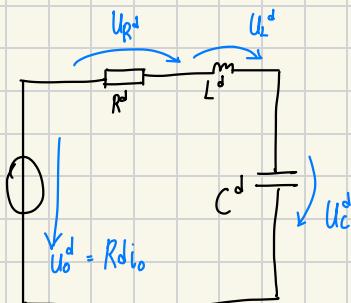
$$L \xrightarrow{R_d} C^d = \frac{1}{R_d^2} L$$




q.3

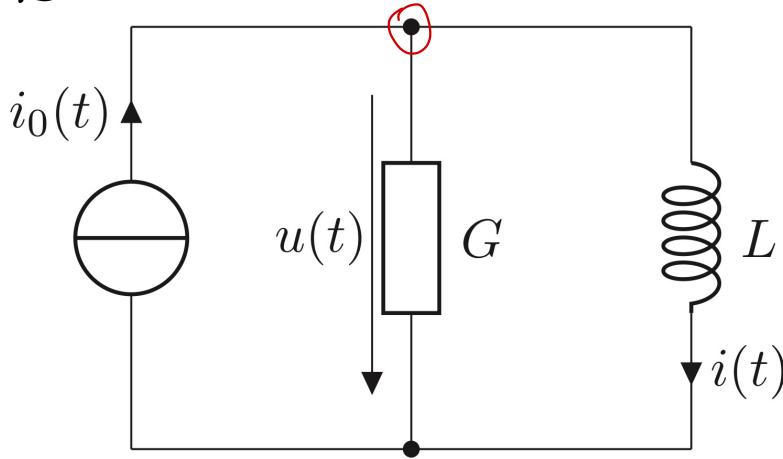

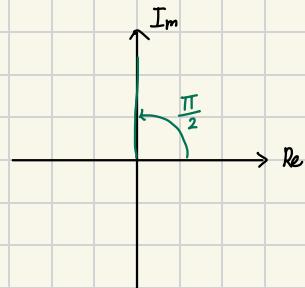- a) Give the phasor  $I_0$  for  $i_0(t) = \hat{I}_0 \cos(\omega t)$  and also for  $i_0(t) = \hat{I}_0 \sin(\omega t)$ .

$$\text{KCL: } i_0(t) - Gu(t) - i(t) = 0$$

$$\begin{aligned} a) \quad i_0(t) &= \hat{I}_0 \cos(\omega t) & i_0(t) &= \hat{I}_0 \sin(\omega t) \\ I_0 &= \hat{I}_0 & &= \hat{I}_0 \cos\left(\omega t + \frac{\pi}{2}\right) \\ & & I_0 &= \hat{I}_0 e^{j\frac{\pi}{2}} \\ & & &= j\hat{I}_0 \end{aligned}$$



- b) What is the relationship between  $i(t)$  and  $u(t)$ ?

$$U(t) = L i(t)$$

- c) Express this relationship for the phasors  $I$  and  $U$ .

$$U = j\omega L I$$

- d) Based on the Kirchhoff's laws and Ohm's law, give  $I$  depending on  $U$  and  $I_0$ .

from KCL:

$$I = I_0 - Gu$$

- e) Find the phasor  $I$  depending on  $I_0$ .

$$U = j\omega L(I_0 - Gu)$$

$$U + j\omega GLU = j\omega L I_0$$

$$U = \frac{j\omega L}{1 + j\omega GL} I_0$$

$$I = I_0 - \frac{j\omega LG}{1 + j\omega LG} I_0 = \frac{1}{1 + j\omega LG} I_0$$

In the following,  $i_0(t)$  is the input to the circuit and  $i(t)$  its output.

- f) Show that the circuit is a lowpass, i.e., signals  $i_0(t)$  with low frequency can pass and portions with high frequency are suppressed. To this end, investigate  $\left| \frac{I}{I_0} \right|$  for  $\omega = 0$ ,  $\omega = \frac{1}{GL}$ , and  $\omega \rightarrow \infty$ .

$$\left| \frac{I}{I_0} \right| = \sqrt{1 + (\omega LG)^2}$$

$$\omega = 0 : \left| \frac{I}{I_0} \right| = 1$$

$$\omega = \frac{1}{GL} : \left| \frac{I}{I_0} \right| = \frac{1}{\sqrt{2}}$$

$$\omega \rightarrow \infty : \left| \frac{I}{I_0} \right| \rightarrow 0$$

$\rightarrow$  Lowpass

g) Determine the phasor  $I$  for  $I_0 = \frac{1}{\sqrt{2}}(1 + j)\hat{I}_1$  and  $\omega = \frac{1}{GL}$ .

$$I_0 = \frac{1}{\sqrt{2}}(1 + j)\hat{I}_1$$

$$\omega = \frac{1}{GL}$$

$$I = \frac{1}{1+j} \cdot \frac{1}{\sqrt{2}}(1+j)\hat{I}_1$$

$$= \frac{\hat{I}_1}{\sqrt{2}}$$

h) Find  $I$  for  $I_0 = (1 - 0.5j)\hat{I}_2$  and  $\omega = \frac{2}{GL}$ .

$$I_0 = \left(1 - \frac{1}{2}j\right)\hat{I}_2 \quad \omega = \frac{2}{GL}$$

$$I = \frac{1}{1+2j} \left(1 - \frac{1}{2}j\right)\hat{I}_2$$

$$= \frac{1-j^2}{1+4} \left(1 - \frac{1}{2}j\right)\hat{I}_2$$

$$= \frac{|-2j - \frac{1}{2}j - 1|}{5} \hat{I}_2 = -\frac{1}{2}j \hat{I}_2$$

i) Give  $i(t)$  for both cases.

$$i(t) = \operatorname{Re} \{ I e^{j\omega t} \}$$

$$\text{I)} \quad i(t) = \operatorname{Re} \left\{ \frac{\hat{I}_1}{\sqrt{2}} e^{j\frac{1}{GL}t} \right\}$$

↓ Euler's rule, cos as (I) is in Re

$$= \frac{\hat{I}_1}{\sqrt{2}} \cos\left(\frac{1}{GL}t\right)$$

$$\text{II)} \quad i(t) = \operatorname{Re} \left\{ -\frac{1}{2} j \hat{I}_2 e^{j\frac{2}{GL}t} \right\}$$

$$= \operatorname{Re} \left\{ -\frac{1}{2} j \hat{I}_2 \left( \cos\left(\frac{2}{GL}t\right) + j \sin\left(\frac{2}{GL}t\right) \right) \right\}$$

$$= \frac{1}{2} \hat{I}_2 \sin\left(\frac{2}{GL}t\right)$$

↓  $j \cdot j = (\sqrt{-1})^2 = -1$

$$\therefore -1 \cdot -\frac{1}{2} = \frac{1}{2}$$

use sin as (II) in  $I_m$

Now the input current is given by

$$i_0(t) = \hat{I}_1 \cos\left(\frac{1}{GL}t + \frac{\pi}{4}\right) + \sqrt{1.25} \hat{I}_2 \cos\left(\frac{2}{GL}t + \arctan(-0.5)\right).$$

j) Find  $i(t)$  resulting from this particular  $i_0(t)$ .

$$\tan(\varphi) = -0.5 = \frac{I_m}{R_e} = -\frac{1}{2}$$

$$\rightarrow R_e = 2$$

$$I_m = -1$$

$$\Rightarrow X \cdot (2-j)$$

$$|2-j| = \sqrt{4+(-1)^2}$$

$$= \sqrt{5} \cdot \sqrt{1.25} = \sqrt{6.25} = 2.5 = \frac{1}{2}$$

$$\text{Phasor} = \hat{I}_1 e^{j\frac{\pi}{4}}$$

$$= \hat{I}_1 \left( \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right)$$

$$= \underbrace{\hat{I}_0}_{\text{from g}} \frac{1}{\sqrt{2}} (1+j)$$

Phasor:

$$\frac{5}{2} \hat{I}_2 \cdot (2-j) \frac{1}{\sqrt{5}} \sqrt{1.25} \approx \underbrace{\hat{I}_2}_{\text{from h}} \left( 1 - j \frac{1}{2} \right)$$

$$i(t) = \frac{I_1}{\sqrt{2}} \cos\left(\frac{1}{GL}t\right) + \frac{1}{2}\hat{I}_2 \sin\left(\frac{2}{GL}t\right)$$

k) Assuming that  $i_G(t) = Gu(t)$ , investigate  $\left|\frac{I_G}{I_0}\right|$  for  $\omega = 0$ ,  $\omega = \frac{1}{GL}$ , and  $\omega \rightarrow \infty$ .

$$\begin{aligned} I_G &= G U_G \\ &= j\omega L G I \end{aligned}$$

$$= \frac{j\omega L G}{1 + j\omega L G} I_0$$

$$\left| \frac{I_G}{I_0} \right| = \frac{\omega L G}{\sqrt{1 + (\omega L G)^2}}$$

$$\omega = 0 : \left| \frac{I_G}{I_0} \right| = 0$$

$$\omega = \frac{1}{LG} : \left| \frac{I_G}{I_0} \right| = \frac{1}{\sqrt{2}}$$


$$\omega \rightarrow \infty : \left| \frac{I_G}{I_0} \right| \rightarrow 1$$

→ highpass
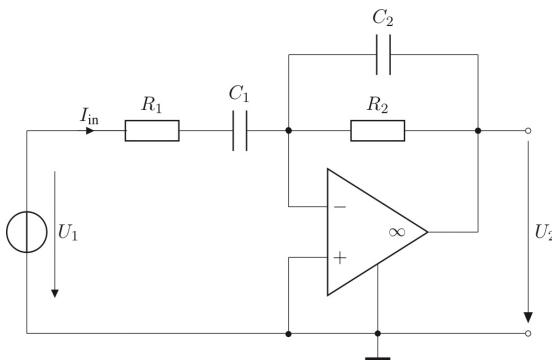
## 9.4 Transfer Function


Consider the following circuit with ideal Op-Amp, the resistors  $R_1$  and  $R_2$ , and the capacitors  $C_1$  and  $C_2$ .

The Op-Amp is operated in the linear region.



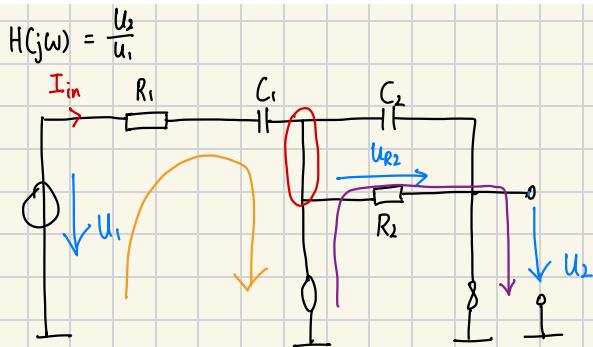- a) Determine the transfer function  $H(j\omega) = U_2/U_1$  by formulating the KVL and KCL equations taking into account the properties of the ideal Op-Amp (nullor).

Set  $R_1 = R$ ,  $R_2 = 10R$ ,  $C_1 = C$ , and  $C_2 = 10C$ . Also use  $RC = 1$ .



$$\text{KVL: } -U_1 + R_1 I_{\text{in}} + \frac{1}{j\omega C_1} I_{\text{in}} = 0$$

$$(R_1 + \frac{1}{j\omega C_1}) I_{\text{in}} = U_1$$

$$I_{\text{in}} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} U_1$$

$$\text{KCL: } I_{\text{in}} - \frac{1}{R_2} U_{R2} - j\omega C_2 U_{R2} = 0$$

$$I_{\text{in}} = \left( \frac{1}{R_2} + j\omega C_2 \right) U_{R2}$$

$$U_{R2} = -\frac{R_2}{1 + j\omega R_2 C_2} I_{\text{in}}$$

$$KVL: U_{R2} + U_2 = 0$$

$$U_2 = -U_{R2}$$

$$= -\frac{R_2}{1+j\omega R_2 C_2} \frac{j\omega C_1}{1+j\omega R_1 C_1} U_i$$

$$H(j\omega) = -\frac{j\omega R_2 C_1}{(1+j\omega R_2 C_2)(1+j\omega R_1 C_1)}$$

b) Investigate  $H(j\omega)$  at  $\omega = 0$ ,  $\omega = \frac{1}{10}$ , and  $\omega \rightarrow \infty$ .

$$H(j\omega) = -\frac{j\omega 10RC}{(1+j\omega 10RC)(1+j\omega RC)}$$

$$= -\frac{j\omega \cdot 10}{(1+j\omega(\infty))(1+j\omega)}$$

$$\omega=0 : H(j0) = 0$$

$$\omega=\frac{1}{10} : H(j\frac{1}{10}) = \frac{-j}{(1+j10)(1+j\frac{1}{10})} = \frac{-j}{1+j10+j\frac{1}{10}-1} = \frac{-j}{j\frac{101}{10}} = \frac{-j}{\frac{101}{10}}$$


$$\omega \rightarrow \infty : H(j\omega) \rightarrow 0$$

c) What can the circuit be used for?


bandpass
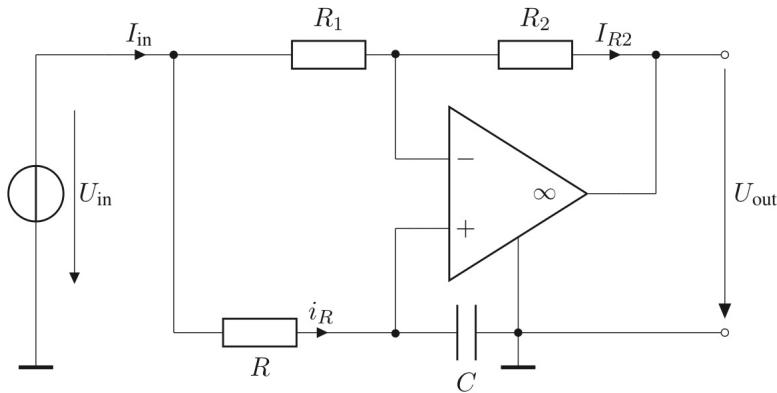
## 9.5 Transfer Function, Allpass

Consider the circuit below. The Op-Amp is operated in the linear region.



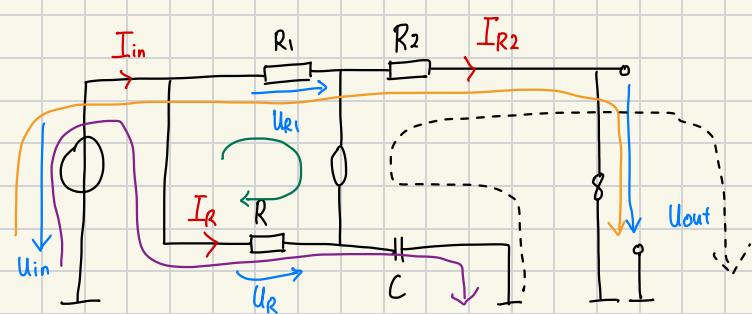- a) Determine the transfer function  $H(j\omega) = U_{\text{out}}/U_{\text{in}}$ .



$$\text{KVL: } -U_{\text{in}} + RI_R + \frac{1}{j\omega C} I_R = 0$$

$\downarrow$   
 impedance of  
 Capacitor

$$\Rightarrow U_{\text{in}} = \left( R + \frac{1}{j\omega C} \right) I_R$$

$$\text{KVL: } -U_{\text{in}} + R_1 I_{R2} + R_2 I_{R2} + U_{\text{out}} = 0$$

$$\text{KVL: } U_{R1} - U_R = 0$$

$$U_{R1} = U_R$$

$$R I_R = R_1 I_{R2}$$

$$I_{R2} = \frac{R}{R_1} I_R \quad \swarrow$$

$$\text{KVL: } -\frac{1}{j\omega C} I_R + R_2 I_{R2} + U_{out} = 0$$

$$\left( \frac{R}{R_1} R_2 - \frac{1}{j\omega C} \right) I_R + U_{out} = 0$$

$$U_{out} = -\left( \frac{R}{R_1} R_2 - \frac{1}{j\omega C} \right) I_R$$

$$U_{in} = (R + j\omega C) I_R$$

$$H(j\omega) = \frac{U_{out}}{U_{in}}$$

$$= \frac{-\left( \frac{R}{R_1} R_2 - \frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}}$$

b) Find  $R_1$  and  $R_2$  such that the circuit is an allpass ( $|H(j\omega)| = 1$ ).

$$|H(j\omega)| = \left| \frac{-1 + \frac{R}{R_1} R_2 j\omega C}{1 + j\omega R C} \right|$$

$$= \sqrt{\frac{1 + \left(\omega \frac{R}{R_1} R_2 C\right)^2}{1 + (\omega R C)^2}} = 1$$

$$1 \left( \omega \frac{R}{R_1} R_2 C \right)^2 = 1 \left( \omega R C \right)^2$$

$$\frac{R}{R_1} R_2 = R$$


$$\frac{R_2}{R_1} = 1$$

$R_2$  &  $R_1$  must be the same

Purposes of allpass is to change phasors
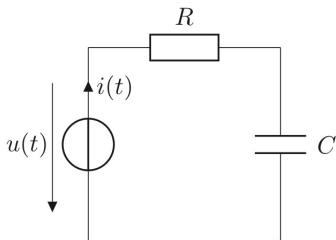
## 9.6 Complex Power

Consider the following circuit with  $u(t) = \hat{U} \cos(\omega t)$ .



- a) Give the complex phasor  $U$  corresponding to  $u(t)$  depending on  $R$ ,  $C$ , and the phasor  $I$ .

$$i(t) = \operatorname{Re} \{ I e^{j\omega t} \} \quad U(t) = \hat{U} \cos(\omega t)$$

$$U(t) = \operatorname{Re} \{ U e^{j\omega t} \}$$

$$Z_{\text{overall}} = R + \frac{1}{j\omega C}$$

$$U = Z_{\text{overall}} \cdot I$$

$$= (R + \frac{1}{j\omega C}) I$$

- b) Determine the complex power  $P$  that is consumed by the circuit depending on  $U$ .

$$P = \frac{1}{2} U I^* \\ = \frac{1}{2} U \cdot \frac{-j\omega C U^*}{1 - j\omega R C}$$

$$= \frac{1}{2} \frac{-j\omega C}{1 - j\omega R C} |U|^2$$

c) Give the average power  $P_W$  and the blind power  $P_B$  depending on  $U$ .

$$P = P_W + j P_B$$

$$P = \frac{1}{2} \frac{-j\omega C(1+j\omega RC)}{1+(\omega RC)^2} |U|^2$$

$$= \frac{1}{2} \frac{\omega^2 RC^2 - j\omega C}{1+(\omega RC)^2} |U|^2$$

$$P_W = \frac{1}{2} \frac{\omega^2 RC^2}{1+(\omega RC)^2} |U|^2$$

$$P_B = \frac{1}{2} \frac{-j\omega C}{1+(\omega RC)^2} |U|^2$$

d) Find the apparent power  $S = |P|$ .

$$S = \sqrt{\frac{(\omega^2 RC^2)^2 + (\omega C)^2}{1+(\omega RC)^2}} |U|^2$$

e) What is the energy that is delivered by the source in every period?

$$P_W = \frac{1}{T} \underbrace{\int_0^T p(t) dt}_E$$

$$E = T \cdot P_W$$

$$= \frac{1}{2} \frac{\omega^2 RC^2}{1+(\omega RC)^2} |U|^2$$

angular freq.:  $\omega = \frac{2\pi}{T} \rightarrow T = \frac{2\pi}{\omega}$

$$E = \pi \cdot \frac{\omega^2 RC^2}{1+(\omega RC)^2} |U|^2$$

- f) Find the angular frequency  $\omega$  such that this energy is maximized. Give the maximum energy  $E_{\max}$ .

$$\frac{dE}{d\omega} = \pi |U|^2 \cdot \left( \frac{RC^2 (1 + (\omega RC)^2)}{(1 + (\omega RC)^2)^2} - \frac{2\omega (RC)^2 \omega RC^2}{(1 + (\omega RC)^2)^2} \right) = 0$$

$$RC^2 (1 + (\omega RC)^2) - 2\omega (RC)^2 \omega RC^2 = 0$$

$$1 + (\omega RC)^2 - 2(\omega RC)^2 = 0$$

$$1 - (\omega RC)^2 = 0$$

$$| = \omega RC$$


$$\omega = \frac{1}{RC}$$

$$E_{\max} = \pi \frac{C}{1 + (1)^2}$$

$$= \frac{\pi}{2} C$$
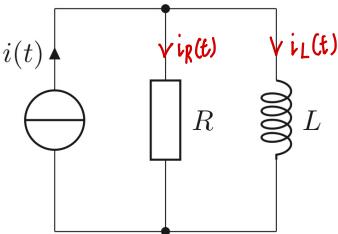
## 9.7 Complex Power

Consider the following circuit with  $i(t) = \hat{I} \cos(\omega t + \varphi)$ .



- a) Give the current phasor  $I$  corresponding to  $i(t)$ .

$$I = I e^{j\varphi}$$

$$i(t) = \operatorname{Re} \{ I e^{j\omega t} \}$$

- b) Determine the impedance  $Z$  of the parallel connection of  $R$  and  $L$ .

$$Z = Z_R \parallel Z_L$$

$$= R \parallel j\omega L$$

$$= \frac{R \cdot j\omega L}{R + j\omega L}$$

- c) Find the complex power of the circuit.

$$U = Z I$$

$$P = \frac{1}{2} U I^*$$

$$= \frac{1}{2} Z I \cdot I^*$$

$$= \frac{1}{2} \frac{j\omega LR}{R + j\omega L} |I|^2$$

d) How much energy is dissipated by the circuit in every period?

$$\begin{aligned}
 P &= P_W + jP_B \\
 &= \frac{1}{2} \frac{j\omega LR(R - j\omega L)}{R^2 + (\omega L)^2} |I|^2 \\
 &= \frac{1}{2} \frac{\omega^2 L^2 R + j\omega L R^2}{R^2 + (\omega L)^2} |I|^2 \\
 \Rightarrow P_W &= \frac{1}{2} \frac{\omega^2 L^2 R}{R^2 + (\omega L)^2} |I|^2 \\
 &= \frac{1}{T} E, \quad T = \frac{2\pi}{\omega}
 \end{aligned}$$

$$\begin{aligned}
 E &= TP_W \\
 &= \pi \cdot \frac{\omega L^2 R}{R^2 + (\omega L)^2} \cdot |I|^2
 \end{aligned}$$

e) Find the angular frequency  $\omega$  to maximize the energy. What is the value of the maximum energy?

$$\frac{dE}{d\omega} = \pi \cdot \frac{L^2 R (R^2 + (\omega L)^2) - 2\omega L^2 \cdot \omega L^2 R}{(R^2 + (\omega L)^2)^2} |I|^2 = 0$$

$$R^2 + \omega^2 L^2 - 2\omega^2 L^2 = 0$$

$$R^2 - \omega^2 L^2 = 0$$

$$\omega = \frac{R}{L}$$

$$E_{\max} = \pi \frac{R^2 L}{R^2 + R^2} |I|^2 = \frac{\pi}{2} L |I|^2$$

