

## Circuit Theory

**Exam:** EDE1201 / Examination**Date:** Monday 12<sup>th</sup> April, 2021**Examiner:** Dr.-Ing. Michael Joham**Time:** 16:30 – 18:10

### Working instructions

- This exam consists of **20 pages** with a total of **8 problems**.  
Please make sure now that you received a complete copy of the exam.
- The total amount of achievable credits in this exam is 90 credits.
- Detaching pages from the exam is prohibited.
- Allowed resources: **maximally 5 two-sided DIN A4 cheat sheets**
- Subproblems marked by \* can be solved without results of previous subproblems.
- **All** answers to be written on the spaces provided. Additional sheets are included at the end of the booklet. Other additional answer sheets will not be accepted.
- Please use only **blue** or **black** pens for writing.
- Laptops, calculators, mobile phones, smart watches, or any wireless devices are **not** allowed in the examination hall. Please **switch off** all electronic devices, put them into your bag, and close the bag.

### At the end of the examination,

Please ensure that you have written your **Student ID** on each page on top right corner.


Failure to do so will mean that your work will not be identified.

**The university reserves the right not to mark your script if you fail to follow these instructions.**

Left room from _____ to _____ / Early submission at _____
---

## Problem 1 Kirchhoff's Laws (6 credits)

Consider the following circuit.

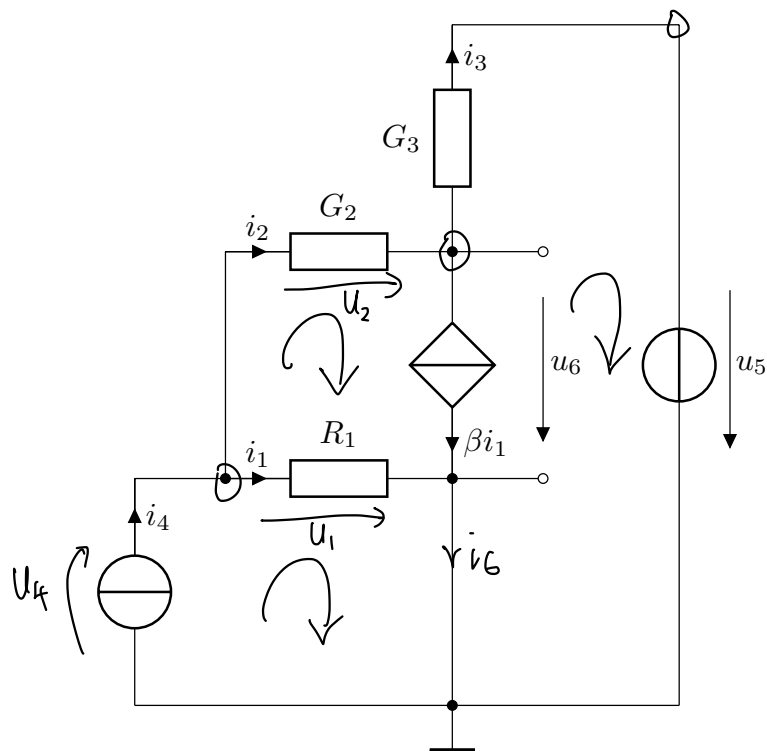

- 0 ☐ 1 ☐ a)\* What is the number of nodes of the circuit?

4

- 0 ☐ 1 ☐ b)\* Give the number of branches of the circuit.

6

- 0 ☐ 1 ☐ 2 ☐ c) Find the node incidence matrix.

$$\begin{aligned} -i_4 + i_1 + i_2 &= 0 \\ -i_2 + i_3 + i_6 &= 0 \\ -i_3 + i_5 &= 0 \end{aligned} \quad \hat{A} = \begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 0 & 1 & 0 \end{bmatrix}$$

B

d) Determine the loop incidence matrix.


☐ 0  
☐ 1  
☐ 2

$$\begin{aligned}u_4 + u_1 &= 0 \\ -u_1 + u_2 + u_6 &= 0 \\ -u_6 + u_3 + u_5 &= 0\end{aligned}$$

$$\tilde{B} = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix}$$
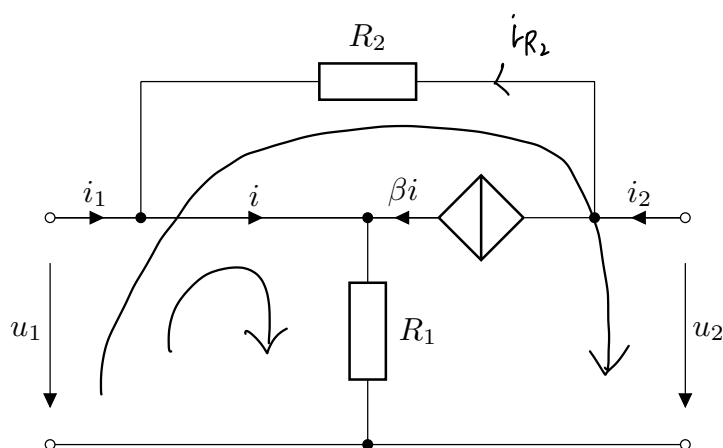
## Problem 2 Two-Ports (16 credits)

Given is the following two-port  $\mathcal{N}$ .



Note that  $R_1 > 0$  and  $R_2 > 0$ .

0  
1  
2

a)\* Determine  $u_1$  depending on  $i$ .

$$u_1 = (i + \beta i) R_1 \quad i_{R_1} = i + \beta i$$

$$u_1 = (1 + \beta) i R_1$$

0  
1  
2

b)\* Find  $u_2$  depending on  $i$  and  $i_2$ .

$$i_{R_2} = i_2 - \beta i$$

$$u_2 = R_2 (i_2 - \beta i) + u_1$$

$$= R_2 (i_2 - \beta i) + (1 + \beta) i R_1$$

$$R_2 (i_2 - \beta i) = R_2 \left( i_2 - \frac{\beta(i_1 + i_2)}{1 + \beta} \right) + (i_1 + i_2) R_1$$

By appropriate analysis, it can be shown that  $i = \frac{i_1 + i_2}{1 + \beta}$ .

c) Give the resistance matrix  $\mathbf{R}_{\mathcal{N}}$  of the two-port  $\mathcal{N}$ .

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \mathbf{R} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$u_1 = (1 + \beta) i R_1 = (i_1 + i_2) R_1$$

$$u_2 = R_2 (i_2 - \beta i) + (1 + \beta) i R_1$$

$$u_1 = r_{11} i_1 + r_{12} i_2$$

$$u_2 = r_{21} i_1 + r_{22} i_2$$

$$\begin{bmatrix} r_{11} = R_1 & r_{12} = R_1 \\ r_{21} = R_1 - \frac{\beta R_2}{1 + \beta} & r_{22} = R_1 + \frac{R_2}{1 + \beta} \end{bmatrix}$$

d) Find  $\beta$  such that the two-port  $\mathcal{N}$  is reciprocal.

$$r_{12} = r_{21}$$

$$R_1 = R_1 - \frac{\beta R_2}{1 + \beta}$$

$$\beta = 0$$


The alternative two-port  $\mathcal{M}$  has the following resistance matrix

$$\mathbf{R}_{\mathcal{M}} = \begin{bmatrix} R_1 \left(1 + \frac{1}{1 + \beta}\right) & R_1 + \frac{R_2}{1 + \beta} \\ R_1 - \frac{\beta R_2}{1 + \beta} & R_2 \end{bmatrix}.$$


e)\* Give the resistance matrix  $\mathbf{R}_{\infty}$  of  $\mathcal{M}$  for the limit  $\beta \rightarrow \infty$ .

$$\mathbf{R}_{\infty} = \begin{bmatrix} R_1 & R_1 \\ R_1 - R_2 & R_2 \end{bmatrix}$$

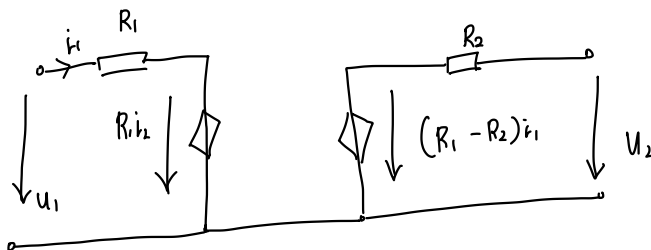f) Draw the equivalent circuit diagram for the resistance matrix  $\mathbf{R}_{\infty}$ .



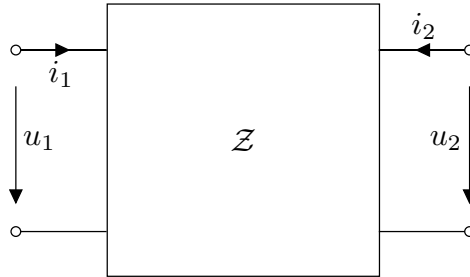Now, consider the two-port  $\mathcal{Z}$ .



The transmission matrix of  $\mathcal{Z}$  is given by

$$\mathbf{A}_{\mathcal{Z}} = \begin{bmatrix} 1 & R_2 \\ -\frac{1}{R_1} & 1 \end{bmatrix}.$$

0 ☐ 1 ☐ 2 ☐ g)\* Is the two-port  $\mathcal{Z}$  current-controlled, i.e., does its resistance matrix exist? Justify your answer.


Yes, since  $a_{21} \neq 0$

0 ☐ 1 ☐ 2 ☐ 3 ☐ h)\* Find a two-port matrix for the two-port  $\mathcal{Z}^d$  which is dual to  $\mathcal{Z}$ . The duality constant is denoted by  $R_d$ .

$$\begin{aligned} \begin{bmatrix} u_1 \\ i_1 \end{bmatrix} &= \mathbf{A} \begin{bmatrix} u_2 \\ -i_2 \end{bmatrix} \\ R_d i_1^d &= R_d i_2^d - \frac{R_2}{R_d} u_2^d \\ \frac{1}{R_d} u_1^d &= -\frac{R_d}{R_1} i_2^d - \frac{1}{R_d} u_2^d \times R_d \\ \mathbf{A}_{\mathcal{Z}^d} &= \begin{bmatrix} -1 & \frac{R_d^2}{R_1} \\ -\frac{R_2}{R_d} & -1 \end{bmatrix} \end{aligned}$$
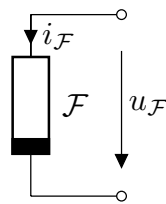
### Problem 3 Non-Linear One-Port (6 credits)

Given is the non-linear one-port  $\mathcal{F}$ .



The characteristic of  $\mathcal{F}$  can be written as

$$i_{\mathcal{F}} = g(u_{\mathcal{F}}) = \frac{2}{3u_0 R} \left( u_{\mathcal{F}} - \frac{u_0}{2} \right)^2 - \frac{u_0}{R}$$

where  $u_0 > 0$  and  $R > 0$  are constants.

Due to the connection of  $\mathcal{F}$ , its operating point voltage is known as  $U_{\mathcal{F}} = 2u_0$ .

a)\* Find the operating point current  $I_{\mathcal{F}}$  of  $\mathcal{F}$ .

0  
1

$$\begin{aligned} I_{\mathcal{F}} = g(2u_0) &= \frac{2}{3u_0 R} \left( 2u_0 - \frac{u_0}{2} \right)^2 - \frac{u_0}{R} \\ &= \frac{2}{3u_0 R} \left( \frac{3u_0}{2} \right)^2 - \frac{u_0}{R} = \frac{2}{3u_0 R} \cdot \frac{9u_0^2}{4} - \frac{u_0}{R} \\ &= \frac{3u_0}{2R} - \frac{u_0}{R} = \frac{u_0}{2R} \end{aligned}$$


b) Linearize  $\mathcal{F}$  in the given operating point with  $U_{\mathcal{F}} = 2u_0$ , that is, find  $i_{\mathcal{F},\text{lin}}$ .

0  
1  
2  
3

$$\begin{aligned} g_{\mathcal{F}} &= \left. \frac{di_{\mathcal{F}}}{du_{\mathcal{F}}} \right|_{U_{\mathcal{F}}=2u_0} = \frac{4}{3u_0 R} \left( 2u_0 - \frac{u_0}{2} \right) \\ &= \frac{4}{3u_0 R} \left( \frac{3u_0}{2} \right) = \frac{2}{R} \\ i_{\mathcal{F},\text{lin}} &= \frac{2}{R} (u_{\mathcal{F}} - 2u_0) + I_{\mathcal{F}} = \frac{2u_{\mathcal{F}}}{R} - \frac{4u_0}{R} + \frac{u_0}{2R} \\ &= \frac{2u_{\mathcal{F}}}{R} - \frac{7u_0}{2R} \end{aligned}$$


c) Draw an equivalent circuit diagram for the linearized one-port with  $i_{\mathcal{F},\text{lin}} = g_{\text{lin}}(u_{\mathcal{F}})$ . Give the element values depending on  $u_0$  and  $R$ .

0  
1  
2

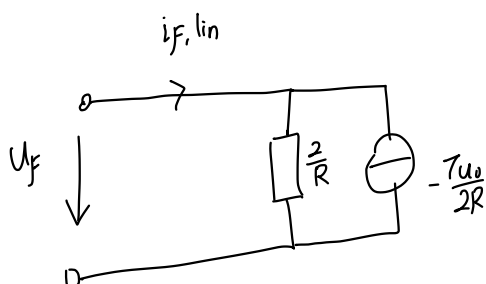

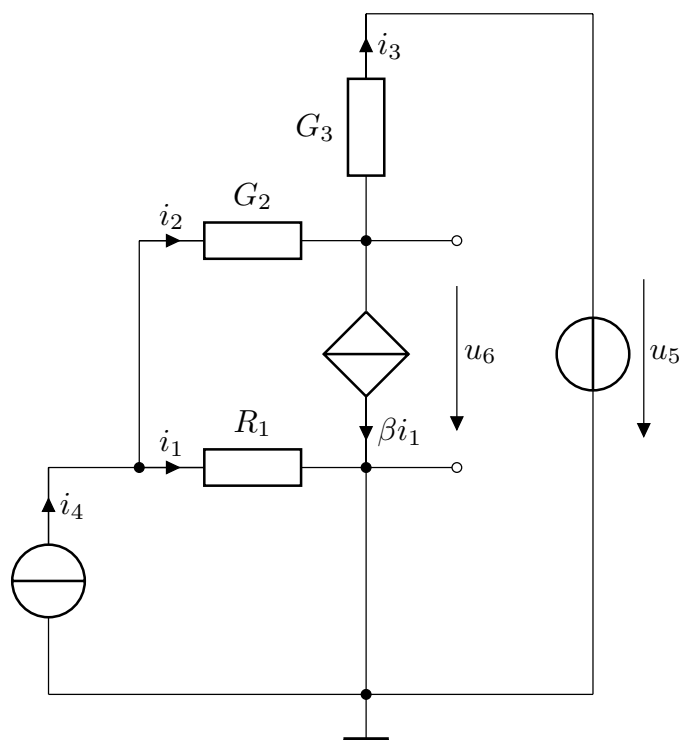
## Problem 4 Nodal Analysis (10 credits)

The circuit of Problem 1 is investigated with the help of the nodal analysis.



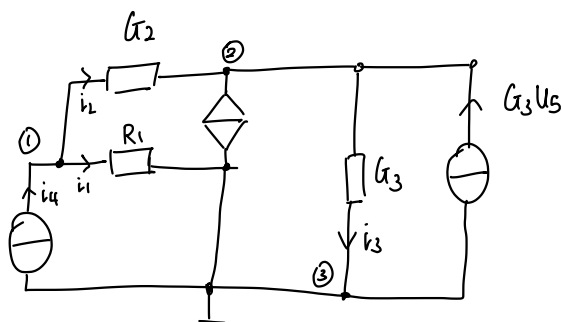- 0 ☐ a)\* Prepare the circuit for the nodal analysis. To this end, express  $i_1$  by the node voltages and  
 1 ☐ perform a source transform. Label the nodes.  
 2 ☐  
 3 ☐



- 0 ☐ b)\* Express  $u_6$  depending on the node voltages.  
 1 ☐

$$u_6 = u_{k2}$$




c) Formulate the equation system of the nodal analysis in the form  $\mathbf{Y}_k \mathbf{u}_k = \mathbf{i}_q$ .

$$\begin{bmatrix} \frac{1}{R_1} + G_2 & -G_2 \\ -G_2 + \frac{\beta}{R_1} & G_2 + G_3 \end{bmatrix} \begin{bmatrix} u_{k1} \\ u_{k2} \end{bmatrix} = \begin{bmatrix} i_4 \\ G_3 u_5 \end{bmatrix}$$

☐ 0  
☐ 1  
☐ 2  
☐ 3  
☐ 4  
☐ 5  
☐ 6
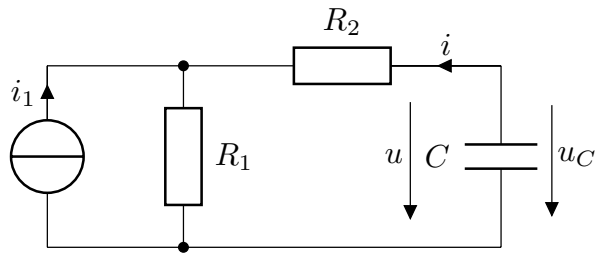
## Problem 5 First-Order Circuit (7 credits)

Consider the following first-order circuit with  $R_1, R_2, C > 0$ .



0 ☐  
1 ☐  
2 ☐  
3 ☐

a)\* Find the representation of the resistive part as a linear source.

0 ☐  
1 ☐

b) What is the time constant  $\tau$  of the circuit?

0 ☐  
1 ☐

c) Justify why the circuit is stable.


Suppose that the excitation is constant, i.e.,  $i_1(t) = I_1$ . Additionally, note that  $u_C(0) = (R_1 + R_2)I_1$ . Use simply  $\tau$  for the time constant.

0 ☐  
1 ☐  
2 ☐

d) Find  $u_C(t)$  for  $t \geq 0$ .
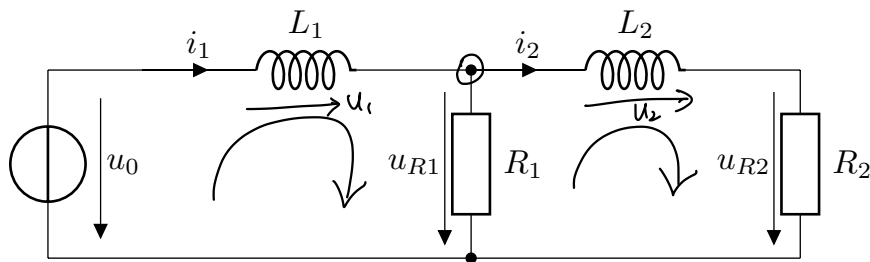
## Problem 6 Linear Second-Order Circuit (27 credits)

In this problem, the following linear circuit with the independent constant voltage source  $u_0$  and the two inductors  $L_1$  and  $L_2$  is investigated.



Note that  $u_{R1}$  is the output of the circuit.

a)\* Give the state variables of the circuit.

0  
1

$$i_1, i_2$$

b)\* Determine the state equations of the circuit.

0  
1  
2  
3  
4  
5

$$\begin{aligned} \text{KVL: } -U_0 + U_1 + U_{R1} &= 0 \\ \text{KVL: } -U_{R1} + U_2 + U_{R2} &= 0 \\ \text{KCL: } i_{R1} &= i_1 - i_2 \\ i_{L1} &= \frac{1}{L_1} U_0 - \frac{R_1}{L_1} i_1 + \frac{R_1}{L_1} i_2 \\ i_{L2} &= \frac{R_1}{L_2} i_1 - \frac{R_1}{L_2} i_2 - \frac{R_2}{L_2} i_2 \\ &= \frac{R_1}{L_2} i_1 - \frac{R_1 + R_2}{L_2} i_2 \\ U_1 &= U_0 - R_1 i_{R1} \\ &= U_0 - R_1 (i_1 - i_2) \\ U_2 &= U_{R1} - U_{R2} \\ &= R_1 (i_1 - i_2) - R_2 \cdot i_2 \end{aligned}$$

c) What are the state matrix and the input vector for the circuit?

0  
1  
2

$$b = \begin{bmatrix} \frac{1}{L_1} \\ 0 \end{bmatrix} \quad A = \begin{bmatrix} -\frac{R_1}{L_1} & \frac{R_1}{L_1} \\ \frac{R_1}{L_2} & -\frac{R_1 + R_2}{L_2} \end{bmatrix}$$

0 ☐  
1 ☐  
2 ☐


d) Give the output vector and the feedthrough if  $u_{R1}$  is the output.

$$C^T = [R_1, -R_1]$$

$$d = 0$$

0 ☐  
1 ☐  
2 ☐  
3 ☐

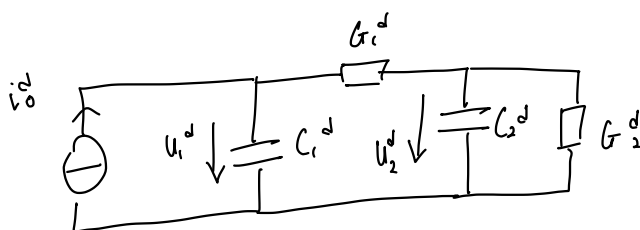e)\* Draw the circuit which is dual to the given circuit.



For a particular choice of the element values, the following normalized state matrix can be obtained

$$A = \begin{bmatrix} -1 & 1 \\ -3 & -5 \end{bmatrix}.$$

0 ☐  
1 ☐  
2 ☐  
3 ☐

f)\* Determine the eigenvalues of this state matrix.

$$\det(A - \lambda I) = (-1 - \lambda)(-5 - \lambda) - (1)(-3) = 0$$

$$= \lambda^2 - 6\lambda + 5 + 3 = 0$$

$$= \lambda^2 - 6\lambda + 8 = 0$$

$$\lambda_1 = -4 \quad \lambda_2 = -2$$

0 ☐  
1 ☐

g) Give the name of the equilibrium.

stable

h) Find the eigenvectors of the given state matrix.

0  
1  
2

$$[A - \lambda_1 I] q_1 = 0 \quad \begin{bmatrix} 3 & 1 \\ -3 & -1 \end{bmatrix} q_1 = 0 \quad q_1 = \begin{bmatrix} 1 \\ -3 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ -3 & -3 \end{bmatrix} q_2 = 0 \quad q_2 = \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

From now on,  $u_0 = 0$ . Correspondingly, the state equations read as

$$\begin{aligned} \dot{x}_1 &= -x_1 + x_2 \\ \dot{x}_2 &= -3x_1 - 5x_2. \end{aligned}$$

i)\* What is the equilibrium  $x_\infty$  of the circuit for  $u_0 = 0$ ?

0  
1  
2

$$\begin{aligned} \dot{x}_1 &= \dot{x}_2 = 0 \\ x_\infty &= 0 \end{aligned}$$

For a different second-order circuit, the eigenvalues and eigenvectors can be written as

$$\begin{aligned} \lambda_1 &= -4 & \lambda_2 &= 2 \\ \mathbf{q}_1 &= \begin{bmatrix} 1 \\ -3 \end{bmatrix} & \mathbf{q}_2 &= \begin{bmatrix} 1 \\ 1 \end{bmatrix}. \end{aligned}$$

The excitation is zero. In other words,  $v(t) = 0$ .

j)\* Why is this circuit unstable?

0  
1

$$\lambda_2 > 0$$

k)\* Give the general expression of the state vector  $x(t)$  of the circuit with the given eigenvalues and eigenvectors.

0  
1  
2

$$x(t) = \begin{bmatrix} 1 \\ -3 \end{bmatrix} e^{-4t} \cdot \zeta_{01} + \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{2t} \cdot \zeta_{02}$$

Due to  $v(t) = 0$ , the output equation is given by

$$y(t) = \mathbf{c}^T \mathbf{x}(t).$$

0 ☐  
1 ☐  
2 ☐

l)\* Determine a non-trivial output vector  $\mathbf{c}^T$ , such that  $y(t)$  converges to zero.

$$\text{Since } \lambda_2 = 2$$

$$\mathbf{c}^T = [1, -1]$$


0 ☐  
1 ☐

m) What is  $y(t)$  for this particular choice for  $\mathbf{c}^T$ ?

$$y(t) = 4 \sin e^{-4t}$$
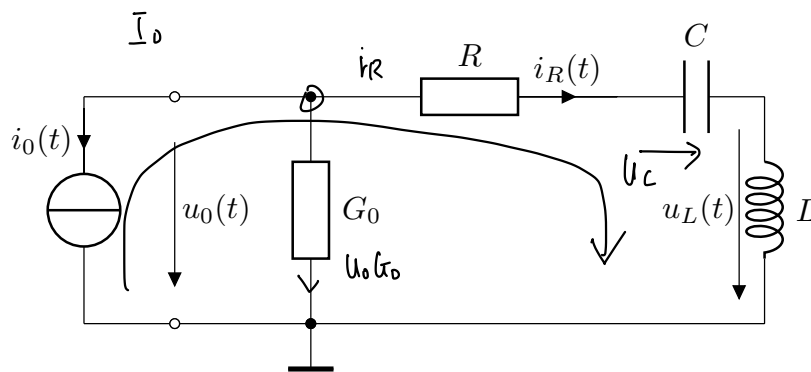
## Problem 7 Complex Phasor Analysis (13 credits)

Given is following circuit with  $G_0, R, C, L > 0$ .



$$u_C = \frac{1}{j\omega C} i_R$$

The current  $i_0(t)$  is sinusoidal with the angular frequency  $\omega$ .

a)\* Give the relationship between  $u_L(t)$  and  $i_R(t)$ .

0  
1

$$u_L(t) = L \dot{i}_R(t)$$

Let  $I_R$  be the phasor for  $i_R(t)$  and  $U_L$  the phasor for  $u_L(t)$ .

b)\* Find  $U_L$  depending on  $I_R$ .

0  
1

$$U_L = j\omega L I_R$$

c) Determine the phasor  $U_0$  depending on  $I_R$ .

0  
1  
2

$$\text{KVL: } -U_0 + R I_R + U_C + U_L = 0$$

$$U_0 = R I_R + \frac{1}{j\omega C} I_R + j\omega L I_R$$



d) What is, therefore,  $I_0$  depending on  $U_0$ ?

$$\begin{aligned} I_0 + G_0 U_0 + \tilde{I}_R &= 0 \\ I_0 &= -G_0 U_0 - \frac{1}{R + \frac{1}{j\omega C} + j\omega L} U_0 = 0 \\ &= -G_0 U_0 - \frac{j\omega C}{j\omega RC + 1 + j\omega^2 LC} U_0 \end{aligned}$$

For the voltage phasor  $U_0$  depending on the phasor  $I_0$  of the current source, it can be obtained that

$$U_0 = -\frac{1}{G_0} \frac{1 + j\omega/\omega_1 - \omega^2 LC}{1 + j\omega/\omega_2 - \omega^2 LC} I_0$$

with the constants  $\omega_1, \omega_2 > 0$ , where  $\omega_1 \neq \omega_2$ .



e)\* Find the complex power of the source depending on  $I_0$ .

$$\begin{aligned} P &= \frac{1}{2} U_0 I_0^* \\ &= -\frac{1}{2} \frac{1}{G_0} \frac{1 + j\omega/\omega_1 - \omega^2 LC}{1 + j\omega/\omega_2 - \omega^2 LC} |I_0|^2 \end{aligned}$$

Now,  $\omega, G_0, R, L > 0$  are constant.



f) Determine  $C$  depending on  $\omega, G_0, R$ , and  $L$  such that the blind power of the source is zero.


$$\begin{aligned} P &= -\frac{1}{2} \frac{1}{G_0} \frac{(1 + j\omega/\omega_1 - \omega^2 LC)(1 - j\omega/\omega_2 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega/\omega_2)^2} |I_0|^2 \\ &= -\frac{1}{2} \frac{1}{G_0} \frac{(\omega/\omega_1 - \omega/\omega_2)(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega/\omega_2)^2} |I_0|^2 = 0 \\ 1 - \omega^2 LC &= 0 \\ C &= \frac{1}{\omega^2 L} \end{aligned}$$



For the corresponding choice for  $C$ , we get


$$P = -\frac{1}{2} \frac{1}{G_0} \frac{R}{R + 1/G_0} |I_0|^2.$$

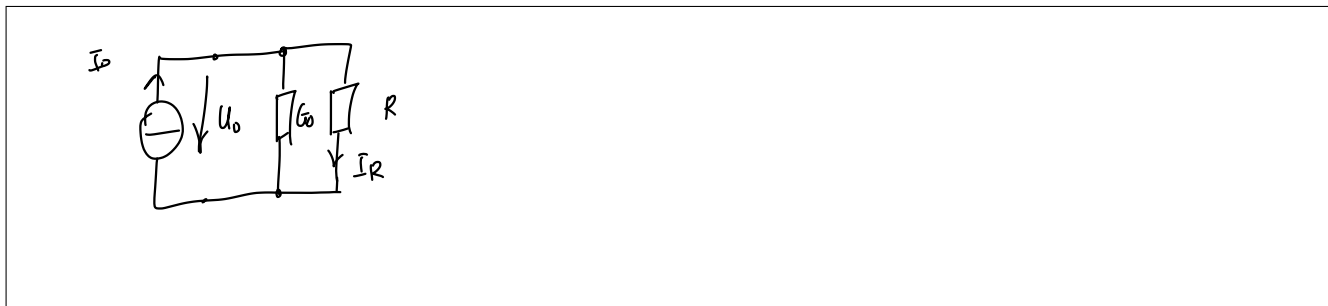g)\* Draw the corresponding equivalent circuit diagram. Mark  $U_0$ ,  $I_0$  and  $I_R$ .



## Problem 8 Op-Amp Circuit (5 credits)

Consider the following Op-Amp circuit.

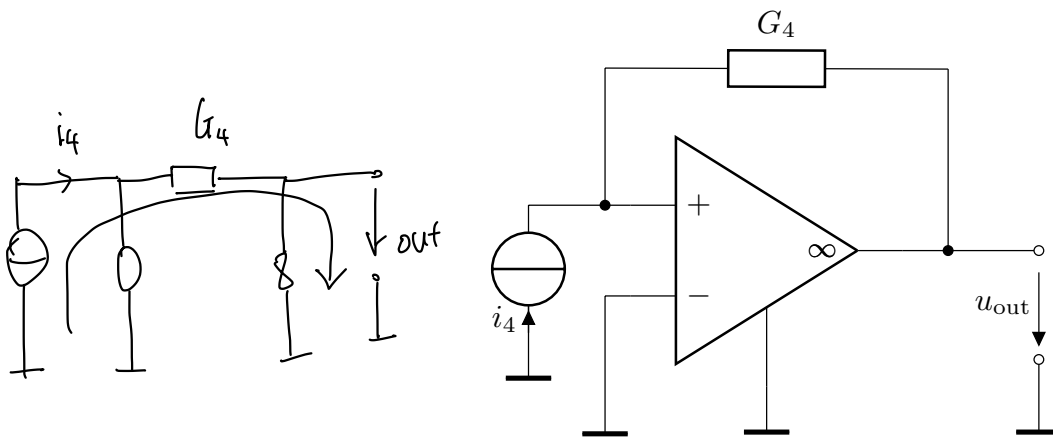

- 0 ☐ 1 ☐ 2 ☐ a)\* Find the voltage  $u_{out}$  depending on  $i_4$  and  $U_{sat}$  if the Op-Amp is operated in the linear region.

$$u_{out} = -\frac{i_4}{G_4} \quad v = IR$$

$$u_{out} + \frac{i_4}{G_4} = 0$$

Now, we assume that the Op-Amp is in the positive saturation. The saturation voltage is denoted by  $U_{sat}$ .

- 0 ☐ 1 ☐ b)\* Give  $u_{out}$  depending on  $i_4$  and  $U_{sat}$ .

$$u_{out} = U_{sat}$$

- 0 ☐ 1 ☐ 2 ☐ c) Determine the range for  $i_4$  such that the Op-Omp is in positive saturation.

$$u_d = U_{sat} + \frac{i_4}{G_4}$$

With  $u_d > 0$ , we can infer that  $i_4 > -U_{sat}G_4$



