

Note:



- During the attendance check a sticker containing a unique code will be put on this exam.
- This code contains a unique number that associates this exam with your registration number.
- This number is printed both next to the code and to the signature field in the attendance check list.

Circuit Theory

Exam: 1203 / EDE

Date: Tuesday 25th July, 2023

Examiner: Dr.-Ing. Michael Joham

Time: 15:00 – 16:40

	P 1	P 2	P 3	P 4	P 5	P 6	P 7
I							


Working instructions

- This exam consists of **18 pages** with a total of **7 problems**.
Please make sure now that you received a complete copy of the exam.
- The total amount of achievable credits in this exam is 90 credits.
- Detaching pages from the exam is prohibited.
- Allowed resources:
 - 5 double-sided DIN A4 pages of notes
 - one analog dictionary English ↔ native language
- Subproblems marked by * can be solved without results of previous subproblems.
- **Answers are only accepted if the solution approach is documented.** Give a reason for each answer unless explicitly stated otherwise in the respective subproblem.
- Do not write with red or green colors nor use pencils.
- Physically turn off all electronic devices, put them into your bag and close the bag.

Left room from _____ to _____ / Early submission at _____

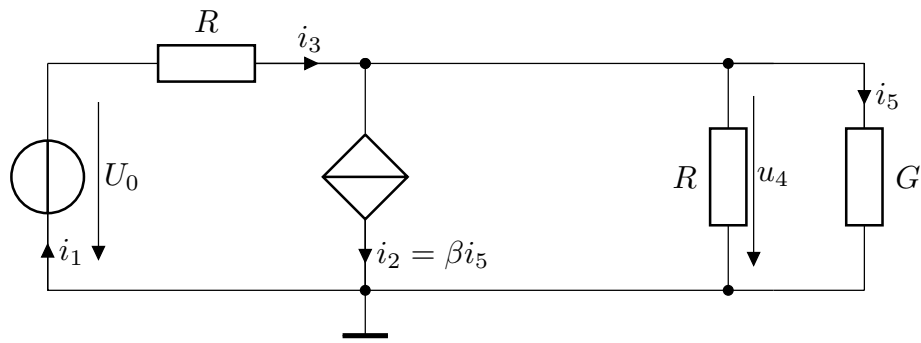Problem 1 Circuit Analysis (17 credits)

Consider the following circuit with a CCCS, three resistors, and a voltage source.



- 0 ☐ 1 ☐ 2 ☐ a)* What is the number of nodes n and the number of branches b of this circuit?

$$n = 3 \quad \checkmark$$

$$b = 5 \quad \checkmark$$

- 0 ☐ 1 ☐ b) Give the number of node voltages for above circuit.

$$n - 1 = 2 \quad \checkmark$$

- 0 ☐ 1 ☐ c) What is the number of linearly independent KCL equations in nullspace representation?

$$n - 1 = 2 \quad \checkmark$$

- 0 ☐ 1 ☐ d) Give the number of linearly independent KVL equations in nullspace representation.

$$b - (n - 1) = 3 \quad \checkmark$$

- 0 ☐ 1 ☐ 2 ☐ e)* Define the branch voltage vector \mathbf{u} and the branch current vector \mathbf{i} .

$$\mathbf{u} = [u_1, u_2, u_3, u_4, u_5]^T \quad \checkmark$$

$$\mathbf{i} = [i_1, i_2, i_3, i_4, i_5]^T \quad \checkmark$$

- 0 ☐ 1 ☐ f)* Give the number of equations for the KVL in rangespace representation.

$$b = 5 \quad \checkmark$$

g) Find the loop incidence matrix \mathbf{B} .

$$\begin{aligned} u_1 + u_3 + u_2 &= 0 \\ -u_2 + u_4 &= 0 \\ -u_4 + u_5 &= 0 \end{aligned}$$

$$\mathbf{B}\mathbf{u} = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix} \mathbf{u} \quad \checkmark\checkmark\checkmark$$

0
1
2
3

h)* Determine the node incidence matrix \mathbf{A} .

$$\begin{aligned} -i_1 + i_3 &= 0 \\ -i_3 + i_2 + i_4 + i_5 &= 0 \end{aligned}$$

$$\mathbf{A}\mathbf{i} = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 1 & 1 \end{bmatrix} \mathbf{i} \quad \checkmark\checkmark$$

0
1
2

i) Based on \mathbf{A} and \mathbf{B} , show that the Tellegen's theorem is fulfilled.

$$\mathbf{A}\mathbf{B}^T = \mathbf{0} \quad \checkmark$$

$$\mathbf{A}\mathbf{B}^T = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \quad \checkmark$$

0
1
2

j) Find i_3 depending on u_4 .

$$\text{KCL: } i_3 = i_2 + i_4 + i_5$$

$$\text{KVL: } u_5 = u_4$$

$$\text{Ohm: } i_4 = \frac{u_4}{R}$$


$$i_5 = Gu_4 \quad \checkmark$$

$$i_3 = \beta Gu_4 + \frac{u_4}{R} + Gu_4 \quad \checkmark$$

0
1
2

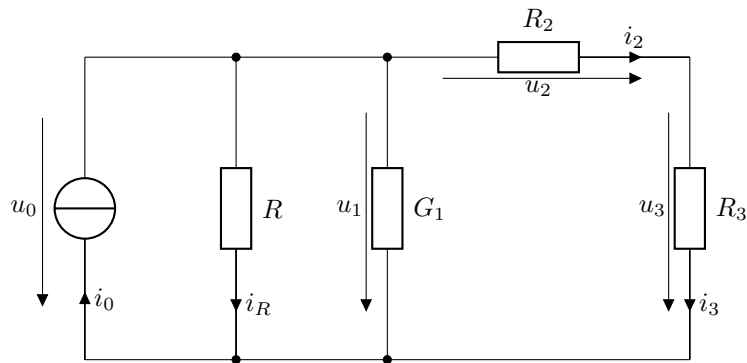Problem 2 Resistor Network (10 credits)

The following circuit with four resistors and a current source is given.



0 a)* Give the current i_R depending on u_0 .



$$i_R = \frac{1}{R} u_0 \quad \checkmark$$

0 b)* Determine the overall conductance G_{overall} of the parallel connection of R with G_1 .



$$G_{\text{overall}} = \frac{1}{R} + G_1 \quad \checkmark$$

0 c)* Find the voltage u_2 depending on i_2 .



$$u_2 = R_2 i_2 \quad \checkmark$$

0 d)* What is the overall resistance R_{overall} of the series connection of R_2 and R_3 ?



$$R_{\text{overall}} = R_2 + R_3 \quad \checkmark$$

0 e) Hence, what are the voltages u_2 and u_3 depending on u_0 ?



$$\text{voltage divider: } u_2 = \frac{R_2}{R_{\text{overall}}} u_0 = \frac{R_2}{R_2 + R_3} u_0 \quad \checkmark$$

$$u_3 = \frac{R_3}{R_{\text{overall}}} u_0 = \frac{R_3}{R_2 + R_3} u_0 \quad \checkmark$$

f) Find i_0 depending on u_0 .

☐ 0
☐ 1
☐ 2


$$\begin{aligned} \text{KCL: } i_0 &= i_R + G_1 u_1 + i_2 \quad \checkmark \\ i_0 &= \left(\frac{1}{R} + G_1 + \frac{1}{R_{\text{overall}}} \right) u_0 \quad \checkmark \end{aligned}$$

g) Determine i_2 depending on i_0 .

☐ 0
☐ 1
☐ 2

$$\text{current divider: } i_2 = \frac{\frac{1}{R_{\text{overall}}}}{\frac{1}{R} + G_1 + \frac{1}{R_{\text{overall}}}} i_0 \quad \checkmark \checkmark$$

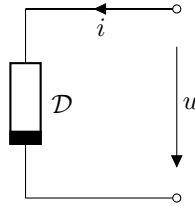Problem 3 Linearization of a One-Port (7 credits)



The characteristic of the one-port \mathcal{D} is given by

$$u = r_{\mathcal{D}}(i) = U_0 + U_0 \sin\left(\frac{i - I_0}{I_0}\right)$$

with the constants U_0 and I_0 .

0 ☐
1 ☐

a)* Give the port-quantities that control \mathcal{D} .

i (but not u) ✓

In the operating point, the current is $I = 2I_0$.

0 ☐
1 ☐

b)* Find the operating point value U of the voltage across \mathcal{D} .

$$U = r_{\mathcal{D}}(I_0) = U_0 + U_0 \sin\left(\frac{2I_0 - I_0}{I_0}\right) = U_0 + U_0 \sin(1) \quad \checkmark$$

In following, consider the different operating point $(U, I) = (U_0, I_0)$.

0 ☐
1 ☐
2 ☐
3 ☐
4 ☐

c)* Determine the linearization $r_{\mathcal{D},\text{lin}}(i)$ of \mathcal{D} in the given operating point $(U, I) = (U_0, I_0)$.

$$R_{\mathcal{D}} = \left. \frac{dr_{\mathcal{D}}(i)}{di} \right|_{i=I_0} = \frac{U_0}{I_0} \cos\left(\frac{i - I_0}{I_0}\right) \Big|_{i=I_0} \quad \checkmark$$

$$R_{\mathcal{D}} = \frac{U_0}{I_0} \quad \checkmark$$

$$r_{\mathcal{D},\text{lin}}(i) = U + R_{\mathcal{D}}(i - I) \quad \checkmark$$

$$r_{\mathcal{D},\text{lin}}(i) = U_0 + \frac{U_0}{I_0}(i - I_0) = \frac{U_0}{I_0} i \quad \checkmark$$

d) Draw the equivalent circuit diagram of $r_{\mathcal{D},\text{lin}}(i)$.

0
1



Sample Solution

Problem 4 Linear Two-Port (9 credits)

The resistance matrix of the two-port \mathcal{S} reads as

$$\mathbf{R}_{\mathcal{S}} = \begin{bmatrix} 0 & -\frac{1}{G_d} \\ \frac{1}{G_d} & 0 \end{bmatrix}$$

with finite G_d .

- 0 ☐ 1 ☐ a)* Based on the given resistance matrix $\mathbf{R}_{\mathcal{S}}$, show that the two-port \mathcal{S} is not reciprocal.

$$r_{12} = -r_{21}$$

Thus, $r_{12} \neq r_{21}$. ✓

- 0 ☐ 1 ☐ b)* What special two-port is \mathcal{S} ?

gyrator ✓

- 0 ☐ 1 ☐ c)* Determine the conductance matrix $\mathbf{G}_{\mathcal{S}}$ of \mathcal{S} .

$$\mathbf{G}_{\mathcal{S}} = \begin{bmatrix} 0 & G_d \\ -G_d & 0 \end{bmatrix} \checkmark$$

A different two-port \mathcal{Z} has got the conductance matrix

$$\mathbf{G}_{\mathcal{Z}} = \begin{bmatrix} 0 & -G_d \\ 2G_d & 0 \end{bmatrix}.$$

- 0 ☐ 1 ☐ d)* Why is \mathcal{Z} lossy?

$$\mathbf{G}_{\mathcal{Z}}^T = \begin{bmatrix} 0 & 2G_d \\ -G_d & 0 \end{bmatrix} \neq -\begin{bmatrix} 0 & -G_d \\ 2G_d & 0 \end{bmatrix} = -\mathbf{G}_{\mathcal{Z}} \checkmark$$

The two-ports \mathcal{S} and \mathcal{Z} are connected in parallel to get the two-port \mathcal{X} .

- 0 ☐ 1 ☐ 2 ☐ e) Find a two-port matrix for the two-port \mathcal{X} .

$$\mathbf{G}_{\mathcal{X}} = \mathbf{G}_{\mathcal{S}} + \mathbf{G}_{\mathcal{Z}} \checkmark$$
$$\mathbf{G}_{\mathcal{X}} = \begin{bmatrix} 0 & 0 \\ G_d & 0 \end{bmatrix} \checkmark$$

f) Give expressions for u_1 and i_1 of \mathcal{X} .

$$i_1 = 0 \quad \checkmark$$
$$u_1 = \frac{1}{G_d} i_2 \quad \checkmark$$

☐ 0
☐ 1
☐ 2

g) What special two-port is \mathcal{X} ?

voltage-controlled current source with gain factor G_d \checkmark


☐ 0
☐ 1

Sample Solution

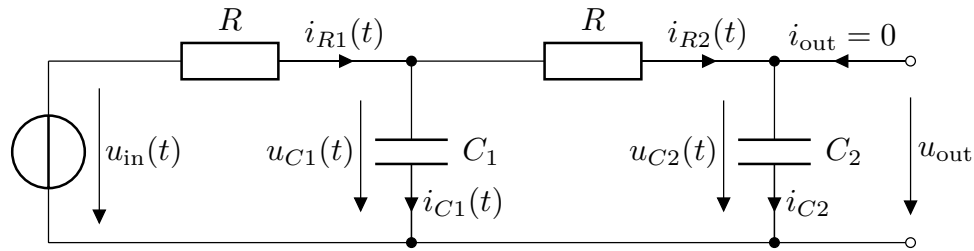Problem 5 Complex Phasor Analysis (16 credits)

Given is the following circuit with two capacitors.

The angular frequency of the sinusoidal excitation $u_{\text{in}}(t)$ is $\omega > 0$.



- 0 ☐ 1 ☐ a)* Give $i_{C1}(t)$ depending on $u_{C1}(t)$.

$$i_{C1}(t) = C_1 \dot{u}_{C1}(t) \quad \checkmark$$

Let I_{C1} denote the phasor corresponding to $i_{C1}(t)$ and U_{C1} the phasor for $u_{C1}(t)$.

- 0 ☐ 1 ☐ b) What is the current phasor I_{C1} depending on the voltage phasor U_{C1} ?

$$I_{C1} = j\omega C_1 U_{C1} \quad \checkmark$$

- 0 ☐ 1 ☐ 2 ☐ c)* Find the voltage phasor U_{C1} depending on the voltage phasor U_{out} (independent of other current or voltage phasors) taking into account that $I_{\text{out}} = 0$.

$$\begin{aligned} \text{KVL: } -U_{C1} + RI_{R2} + U_{\text{out}} &= 0 \quad \checkmark \\ U_{C1} &= j\omega RC_2 U_{\text{out}} + U_{\text{out}} \quad \checkmark \end{aligned}$$

- 0 ☐ 1 ☐ 2 ☐ d) Determine the current phasor I_{R1} depending on the voltage phasor U_{out} .

$$\begin{aligned} \text{KCL: } I_{R1} &= I_{C1} + I_{R2} \quad \checkmark \\ I_{R1} &= j\omega C_1 U_{C1} + j\omega C_2 U_{\text{out}} \\ I_{R1} &= (j\omega)^2 RC_1 C_2 U_{\text{out}} + j\omega C_1 U_{\text{out}} + j\omega C_2 U_{\text{out}} \quad \checkmark \end{aligned}$$

e)* Express the voltage phasor U_{C1} depending on the voltage phasor U_{in} and the current phasor I_{R1} .

0
1

$$U_{C1} = U_{in} - RI_{R1} \quad \checkmark$$

With the time constant τ , the transfer function of another circuit can be written as

$$H(j\omega) = \frac{U_{out}(j\omega)}{U_{in}(j\omega)} = \frac{1}{(j\omega\tau)^2 + \frac{3}{2}j\omega\tau + 1}.$$

f)* Investigate $|H(j\omega)|$ at $\omega = 0$, $\omega = \frac{1}{\tau}$, and $\omega \rightarrow \infty$.

0
1
2
3

$$\begin{aligned} |H(j0)| &= 1 \quad \checkmark \\ |H(j\frac{1}{\tau})| &= \frac{1}{|-1+\frac{3}{2}j+1|} = \frac{2}{3} \quad \checkmark \\ \lim_{\omega \rightarrow \infty} |H(j\omega)| &= 0 \quad \checkmark \end{aligned}$$

g) What filter type (lowpass, highpass, bandpass, bandstop, allpass) is the transfer function $H(j\omega)$? Justify your answer based on above results.

0
1

Since $|H(j0)| = 1$ and $\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$, it is a lowpass. \checkmark

The input voltage is given by $u_{in}(t) = 6 \text{ V} \cos(\frac{2}{\tau}t + \frac{\pi}{4})$.

h)* Give the phasor U_{in} corresponding to the given $u_{in}(t)$.

0
1

$$U_{in} = 6 \text{ V} e^{j\frac{\pi}{4}} \quad \checkmark$$

i) Find the output phasor U_{out} in polar form, i.e., as the product of magnitude and the exponential depending on the phase.

0
1
2
3

$$\begin{aligned} U_{out} &= H(j\frac{2}{\tau})U_{in} \\ H(j\frac{2}{\tau}) &= \frac{1}{(j2)^2 + 3j + 1} = \frac{1}{-3+3j} \quad \checkmark \\ H(j\frac{2}{\tau}) &= \frac{1}{3\sqrt{2}} e^{j\frac{-3\pi}{4}} \quad \checkmark \\ U_{out} &= \sqrt{2} \text{ V} e^{-j\frac{\pi}{2}} \quad \checkmark \end{aligned}$$

Let the output phasor be given by

$$U_{\text{out}} = 2 \text{ V } e^{j \frac{\pi}{3}}.$$

0
1


j)* Give the time-signal $u_{\text{out}}(t)$ corresponding to the phasor U_{out} .

$$u_{\text{out}}(t) = \text{Re}\{U_{\text{out}} e^{j\omega t}\} = 2 \text{ V } \cos(\omega t + \frac{\pi}{3}) \quad \checkmark$$

Sample Solution

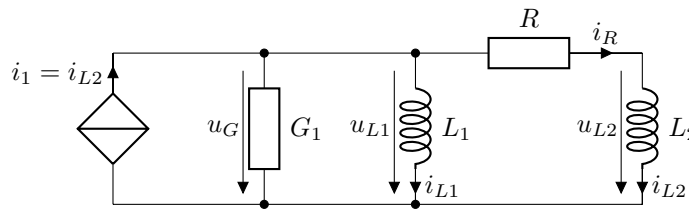Problem 6 Second-Order Circuit (16 credits)

Given is the following second-order circuit with the two inductors L_1 and L_2 connected to a CCCS and two resistors.



a)* Give the state variables of the circuit.

$$i_{L1}, i_{L2} \quad \checkmark$$

0
1

b) Define the state vector \mathbf{x} .

$$\mathbf{x} = \begin{bmatrix} i_{L1} \\ i_{L2} \end{bmatrix} \quad \checkmark$$

0
1

c)* Find u_{L1} depending on u_{L2} and i_R .

$$u_{L1} = u_{L2} + Ri_R \quad \checkmark$$

0
1

d)* Give i_{L2} depending on i_R .

$$i_{L2} = i_R \quad \checkmark$$

0
1

e)* Determine u_{L1} depending on u_G .

$$u_{L1} = u_G \quad \checkmark$$

0
1

f) Express u_{L1} depending on i_{L1} without using any time derivatives.

$$\begin{aligned} \text{KCL: } -i_{L2} + G_1 u_G + i_{L1} + i_R &= 0 \quad \checkmark \\ u_{L1} &= -\frac{1}{G_1} i_{L1} \quad \checkmark \end{aligned}$$

0
1
2

0 ☐ g) Find u_{L2} depending on i_{L1} and i_{L2} .

1 ☐

$$u_{L2} = -\frac{1}{G_1} i_{L1} - R i_{L2} \quad \checkmark$$

0 ☐ h) Give the state equations for the given circuit.

1 ☐
2 ☐

$$\begin{aligned} \dot{i}_{L1} &= -\frac{1}{G_1 L_1} i_{L1} \quad \checkmark \\ \dot{i}_{L2} &= -\frac{1}{G_1 L_2} i_{L1} - \frac{R}{L_2} i_{L2} \quad \checkmark \end{aligned}$$

The state equations for another second-order system read as

$$\begin{aligned} \dot{x}_1 &= -2x_1 \\ \dot{x}_2 &= -3x_1 + x_2 \end{aligned}$$

with the state vector $\mathbf{x} = [x_1, x_2]^T$.

0 ☐ i)* Find the state matrix \mathbf{A} .

1 ☐
2 ☐

$$\mathbf{A} = \begin{bmatrix} -2 & 0 \\ -3 & 1 \end{bmatrix} \quad \checkmark \checkmark$$

0 ☐ j) Determine the eigenvalues of \mathbf{A} .

1 ☐
2 ☐

$$\begin{aligned} \det(\mathbf{A} - \lambda \mathbf{1}) &= (-2 - \lambda)(1 - \lambda) = 0 \quad \checkmark \\ \lambda_1 &= -2 \text{ and } \lambda_2 = 1 \quad \checkmark \end{aligned}$$

0 ☐ k) Investigate **both** eigenvalues and explain why the circuit is unstable.

1 ☐
2 ☐

$\lambda_1 = -2$: stable eigenvalue
 $\lambda_2 = 1$: unstable eigenvalue
Due to λ_2 , the circuit is unstable. $\checkmark \checkmark$

Problem 7 Non-Linear Two-Port (15 credits)

The current-controlled characteristic of the non-linear two-port \mathcal{T} can be written as

$$\mathbf{u} = \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \mathbf{r}_{\mathcal{T}}(\mathbf{i}) = \begin{bmatrix} U_0(\frac{i_1}{I_0} + \frac{i_2^2}{I_0^2}) \\ R_0 i_1 + 2R_0 i_2 \end{bmatrix}$$

with the constants U_0 , I_0 , and $R_0 = \frac{U_0}{I_0}$.

a)* Find u_1 and u_2 of the two-port \mathcal{T} for $i_1 = 0$ and $i_2 = 0$.

$$u_1 = 0 \text{ and } u_2 = 0 \quad \checkmark$$

0
1

b) Argue why the two-port is sourcefree.

$$\text{The origin is part of the characteristic as } \mathbf{r}_{\mathcal{T}}(\mathbf{0}) = \mathbf{0}. \quad \checkmark$$

0
1

c)* Determine $\mathbf{r}_{\mathcal{T}}([i_2, i_1]^T)$.

$$\mathbf{r}_{\mathcal{T}}([i_2, i_1]^T) = \begin{bmatrix} R_0 i_2 + R_0 \frac{i_1^2}{I_0} \\ R_0 i_2 + 2R_0 i_1 \end{bmatrix} \quad \checkmark$$

0
1

d) Argue why the two-port \mathcal{T} is not symmetric.

$$\mathbf{r}_{\mathcal{T}}([i_2, i_1]^T) \neq \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \mathbf{r}_{\mathcal{T}}(\mathbf{i}) \quad \checkmark$$

0
1

e)* Why does the hybrid-controlled characteristic of \mathcal{T} not exist?

$$u_1 \text{ and } i_1 \text{ depend on } i_2^2. \quad \checkmark$$

It is impossible to find a unique expression for i_2 depending on the i_1 and u_2 . \checkmark

0
1
2

f)* Find the inverse hybrid representation of \mathcal{T} .

$$i_1 = \frac{u_1}{R_0} - \frac{i_2^2}{I_0} \quad \checkmark$$

$$u_2 = u_1 + 2R_0 i_2 - U_0 \frac{i_2^2}{I_0^2} \quad \checkmark$$

0
1
2


Assume that the two-port \mathcal{T} is connected to a short circuit at port one and to the current source I_0 at port two.

0 ☐
1 ☐
2 ☐
3 ☐
4 ☐

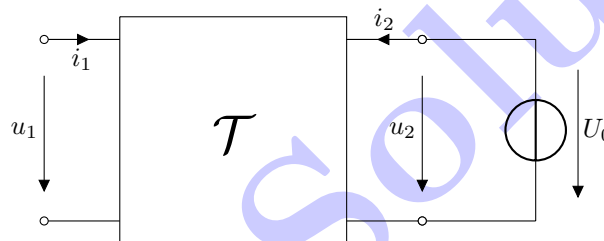g) Determine the corresponding operating point (U_1, U_2, I_1, I_2) .

short circuit: $U_1 = 0$ ✓
current source: $I_2 = I_0$ ✓
 $I_1 = -\frac{I_0^2}{I_0} = -I_0$ ✓
 $U_2 = U_0$ ✓

Now the two-port is connected to the voltage source U_0 at port two as illustrated below.



0 ☐
1 ☐

h)* What is u_2 depending on U_0 ?

$u_2 = U_0$ ✓

0 ☐
1 ☐

i) Express i_2 depending on i_1 and I_0 .
Remember that $R_0 = \frac{U_0}{I_0}$.

$i_2 = -\frac{1}{2} i_1 + \frac{I_0}{2}$ ✓

0 ☐
1 ☐

j) What is the power p_2 at port two?

$p_2 = u_2 i_2 = -\frac{1}{2} U_0 i_1 + \frac{U_0 I_0}{2}$ ✓

Additional space for solutions—clearly mark the (sub)problem your answers are related to and strike out invalid solutions.

A large rectangular area filled with a fine grid of squares, intended for writing solutions. A large, light blue, semi-transparent watermark with the text "Sample Solution" is oriented diagonally from the bottom-left to the top-right across the entire grid.

Sample Solution