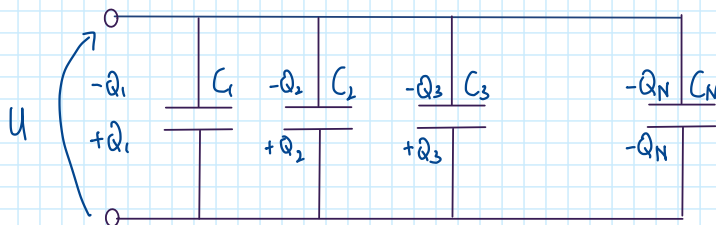


### 1.7.3. Capacitor Aggregations/Configurations

#### (i) Parallel circuit:

N capacitors in parallel  $C_i$  ( $i = 1 \dots N$ )

(Note: they don't have to be necessarily parallel plate capacitors!)



Can we find an equivalent circuit representation, which describes this configuration by a single capacitance? = total capacitance  $C_p$

· Voltage is the same for each capacitor  $C_i$

· For each  $C_i$ :  $C_i = \frac{Q_i}{U} \Rightarrow Q_i = C_i \cdot U$

· total  $Q_{\text{total}}$ :  $Q_{\text{total}} = \sum_{i=1}^N Q_i = \sum_{i=1}^N C_i \cdot U = U \sum_{i=1}^N C_i$

$$Q_{\text{total}} = C_p \cdot U \Rightarrow C_p = \sum_{i=1}^N C_i \quad (1.48)$$


↑  
parallel

equivalent circuit representation:  $U \uparrow \parallel C_p = \sum_{i=1}^N C_i$
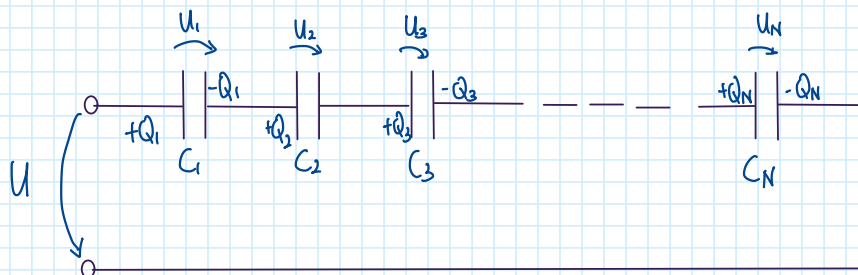
#### (ii) Serial circuit

N capacitors in serial configuration

(Note: they don't have to be necessarily parallel plate capacitors!)



in an Electrostatic equilibrium, if all  $C_i$  are charge ( $\hat{=}$  stable situation)

$$Q_1 = Q_2 = Q_3 = Q_4 = \dots = Q_{N-1} = Q_N \Rightarrow Q_i \text{ are equal} \\ = Q_{\text{total}}$$

$$Q_{\text{total}} = Q_1 = Q_2 = Q_3 = Q_N$$

for one capacitor  $C_i = \frac{Q_i}{U_i} = \frac{Q_{total}}{U_i} \Rightarrow U_i = \frac{1}{C_i} \cdot Q_{total}$

$$U = \sum_{i=1}^N U_i = \sum_{i=1}^N \frac{1}{C_i} Q_{total} = Q_{total} \cdot \sum_{i=1}^N \frac{1}{C_i}$$


$$C_s = \frac{Q_{total}}{U} = U = \frac{1}{C_s} \cdot Q$$

$$\Rightarrow \frac{1}{C_s} = \sum_{i=1}^N \frac{1}{C_i} \quad (1.46)$$

$$C_1 = C_0 \quad C_2 = C_0$$


$$\frac{1}{C_{total}} = \frac{1}{C_0} + \frac{1}{C_0} = \frac{2}{C_0}$$
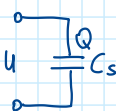
$$\Rightarrow C_{total} = \frac{C_0}{2}$$



### (iii) Dielectric layers in parallel

Plate capacitor is filled with two dielectric layers in arranged side by side in parallel

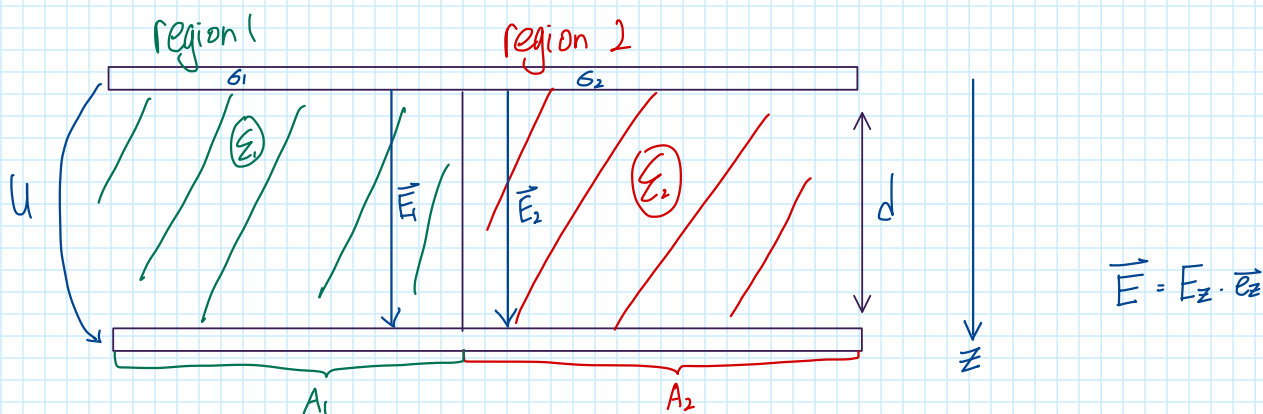

region	permittivity	area	Surface charge	E-field	D-field
1	$\epsilon_1$	$A_1$	$\sigma_1$	$\vec{E}_1$	$\vec{D}_1$
2	$\epsilon_2$	$A_2$	$\sigma_2$	$\vec{E}_2$	$\vec{D}_2$

Calculate total charge Q and voltage U, and hereof the total capacitance of this arrangement:  $C = \frac{Q}{U}$

$$U = \int_0^d E_z \cdot \vec{e}_z \cdot \vec{e}_z \cdot dz = E_z \cdot d$$

Same voltage in both regions  $\Rightarrow U = E_1 d = E_2 d \Rightarrow E = \frac{U}{d} = |\vec{E}|$

$$E_1 = E_2$$

Since  $\epsilon_1 \neq \epsilon_2 \Rightarrow |\vec{D}_1| \neq |\vec{D}_2|$  since  $\vec{D} = \epsilon \vec{E}$

$$D_1 = \epsilon_1 E_1 = \epsilon_1 \frac{U}{d}$$

$$D_2 = \epsilon_2 E_2 = \epsilon_2 \frac{U}{d}$$

$$C = \frac{Q}{U}$$

At surface of a plates:  $|\vec{D}| = \sigma \Rightarrow \sigma_1 \neq \sigma_2$

$$\sigma_1 = D_1 = \epsilon_1 \frac{U}{d}$$

$$\sigma_2 = D_2 = \epsilon_2 \frac{U}{d}$$

Calculate total  $Q$  at the electrodes:


$$\begin{aligned} Q &= \int_A \sigma \cdot da = \sigma \cdot A \\ &= (\sigma \cdot A_1 + \sigma \cdot A_2) \\ &= \frac{\epsilon_1 A_1 U}{d} + \frac{\epsilon_2 A_2 U}{d} \end{aligned}$$

$\sigma = \text{Homogeneous}$

$$C = \frac{Q}{U} = \frac{\epsilon_1 A_1}{d} + \frac{\epsilon_2 A_2}{d} = C_1 + C_2 \quad \triangleq \text{parallel connection of capacitors}$$


$\downarrow$  region 1       $\downarrow$  region 2

Equivalent circuit representation :

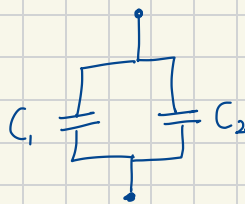

### (iii) Dielectric layers in series

Plate capacitor is filled with two dielectric materials, which are arranged in series

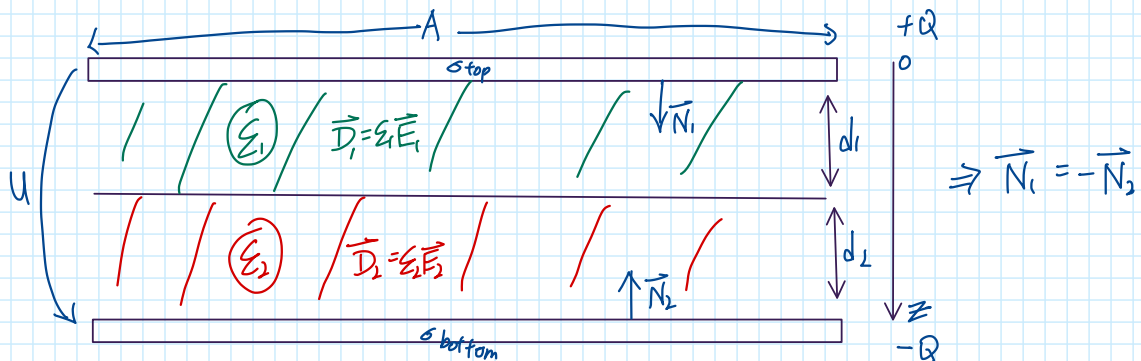

region	permittivity	area	Surface charge	E-field	D-field
1	$\epsilon_1$	$A$	$\sigma_{top} \Rightarrow Q = \sigma_{top} \cdot A$	$\vec{E}_1$	$\vec{D}_1$
2	$\epsilon_2$	$A$	$\sigma_{bot} \Rightarrow Q = \sigma_{bot} \cdot A$	$\vec{E}_2$	$\vec{D}_2$

Calculate total charge Q and voltage U, and hereof the total capacitance of this arrangement:  $C_{tot} = \frac{Q}{U}$

• Calculate Q:  $\sigma_{top} = \frac{+Q}{A}$   
 $\sigma_{bottom} = -\frac{Q}{A}$

• We know at Conductor's surface:  $\vec{D}_1 \cdot \vec{N}_1 = \sigma_{top} = \frac{Q}{A}$   
 $\vec{D}_2 \cdot \vec{N}_2 = \sigma_{bot} = -\frac{Q}{A}$   
 $\vec{N}_1 = -\vec{N}_2$

$-\vec{D}_2 \cdot \vec{N}_1 = \sigma_{bot} = -\frac{Q}{A}$   
 $\Rightarrow \vec{D}_2 \cdot \vec{N}_1 = \frac{Q}{A}$

$\Rightarrow \vec{D}_1 = \vec{D}_2 \Rightarrow \vec{D}$  is continuous  
 $|\vec{D}_1| = |\vec{D}_2| = \frac{Q}{A}$


$\Rightarrow \vec{E}_1 \neq \vec{E}_2$  due to  $\epsilon_1 \neq \epsilon_2$

Calculate Voltage :

$$U = \int_{\text{top}}^{\text{bottom}} \vec{E} d\vec{r} = \int_0^{d_1} E_1 dz + \int_{d_1}^{d_1+d_2} E_2 dz = d_1 \cdot E_1 + d_2 \cdot E_2$$

$$U = d_1 \frac{D_1}{\epsilon_1} + d_2 \frac{D_2}{\epsilon_2} = \left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right) \cdot D_1 = \left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right) \cdot \frac{Q}{A}$$
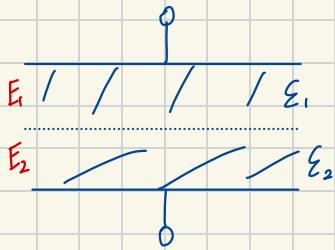
$$\text{Capacitance : } C = \frac{Q}{U} = \frac{\cancel{Q} \cdot A}{\left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right) \cdot \cancel{Q}} = \frac{A}{\left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right)}$$



$$\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$C_1 = \frac{\epsilon_1 A}{d_1}$$

$$C_2 = \frac{\epsilon_2 A}{d_2}$$

$$\frac{1}{C_{\text{tot}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d_1}{\epsilon_1 A} + \frac{d_2}{\epsilon_2 A}$$

$$\Rightarrow C_{\text{total}} = \frac{1}{\left( \frac{d_1}{\epsilon_1 A} + \frac{d_2}{\epsilon_2 A} \right)} = \frac{1}{\frac{1}{A} \left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right)} = \frac{A}{\left( \frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} \right)}$$